



# *Digital Integrated Circuits*


## *A Design Perspective*

Jan M. Rabaey  
Anantha Chandrakasan  
Borivoje Nikolic


# The Inverter

*July 30, 2002*

# *The CMOS Inverter: A First Glance*

 


# CMOS Inverter

 

# Two Inverters



**Share power and ground**

**Abut cells**

 


# CMOS Inverter

## First-Order DC Analysis

  


$$\begin{aligned} V_{OL} &= 0 \\ V_{OH} &= V_{DD} \\ V_M &= f(R_n, R_p) \end{aligned}$$

# CMOS Inverter: Transient Response

 


(a) Low-to-high

 

 
(b) High-to-low

$$t_{pHL} = f(R_{on} \cdot C_L) \\ = 0.69 R_{on} C_L$$




# *Voltage Transfer Characteristic*

# PMOS Load Lines

 





# CMOS Inverter Load Characteristics

 


# CMOS Inverter VTC

 
 
# Switching Threshold as a function of Transistor Ratio



# Determining $V_{IH}$ and $V_{IL}$

 


$$V_{IH} - V_{IL} = -\frac{(V_{OH} - V_{OL})}{g} = \frac{-V_{DD}}{g}$$

$$V_{IH} = V_M - \frac{V_M}{g} \quad V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

$$NM_H = V_{DD} - V_{IH} \quad NM_L = V_{IL}$$



A simplified approach

# Inverter Gain

 


$$g = -\frac{1}{I_D(V_M)} \frac{k_n V_{DSATn} + k_p V_{DSATp}}{\lambda_n - \lambda_p}$$
$$\approx \frac{1 + r}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$


# *Gain as a function of $V_{DD}$*

  

# *Simulated VTC*

 

# Impact of Process Variations

 






# *Propagation Delay*

# CMOS Inverter Propagation Delay

## Approach 1

 


$$t_{pHL} = \frac{C_L V_{swing}/2}{I_{av}}$$


$$\sim \frac{C_L}{k_n V_{DD}}$$

# CMOS Inverter Propagation Delay


## Approach 2

 

 
$$t_{pHL} = f(R_{on} \cdot C_L)$$
$$= 0.69 R_{on} C_L$$



# CMOS Inverters

 


# Transient Response

 


# *Design for Performance*

- ❑ Keep capacitances small
- ❑ Increase transistor sizes
  - watch out for self-loading!
- ❑ Increase  $V_{DD}$  (????)

# Delay as a function of $V_{DD}$

 


# Device Sizing

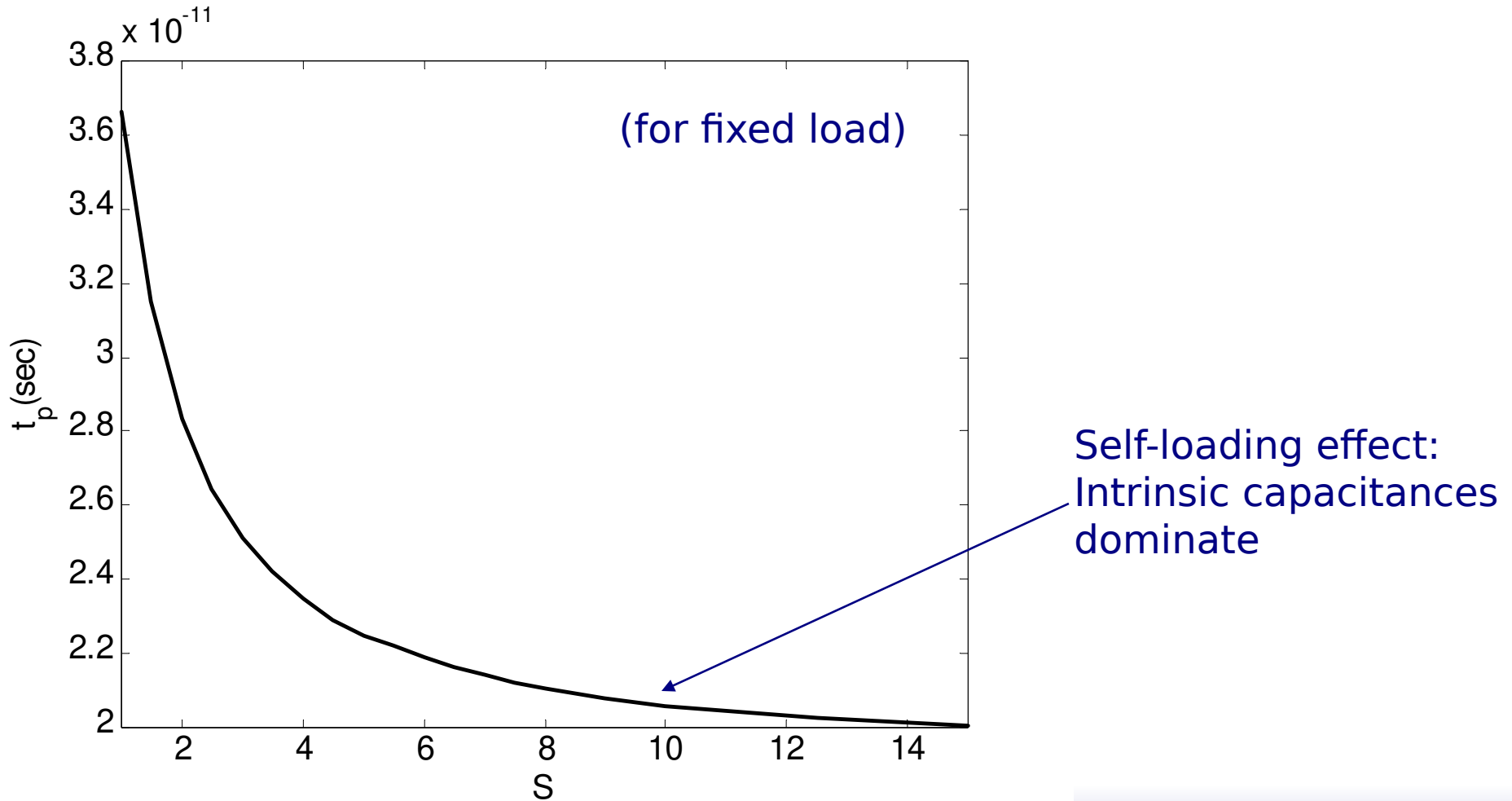




# NMOS/PMOS ratio

 


$$\beta = W_p/W_n$$

# Impact of Rise Time on Delay

 

 
$$t_{pHL} = \sqrt{t_{pHL(step)}^2 + (t_r/2)^2}$$



# *Inverter Sizing*

# Inverter Chain

 


If  $C_L$  is given:

- How many stages are needed to minimize the delay?
- How to size the inverters?

May need some additional constraints.
 
# Inverter Delay

- Minimum length devices,  $L=0.25\mu\text{m}$
- Assume that for  $W_P = 2W_N = 2W$ 
  - same pull-up and pull-down currents
  - approx. equal resistances  $R_N = R_P$
  - approx. equal rise  $t_{pLH}$  and fall  $t_{pHL}$  delays
- Analyze as an RC network





Delay (D):  $t_{pHL} = (\ln 2) R_N C_L$

$$t_{pLH} = (\ln 2) R_P C_L$$

Load for the next stage:

# *Inverter with Load*

  



$$t_p = k R_W C_L$$

$k$  is a constant, equal to 0.69

Assumptions: no load  $\rightarrow$  zero delay

$$W_{unit} = 1$$

# Inverter with Load

 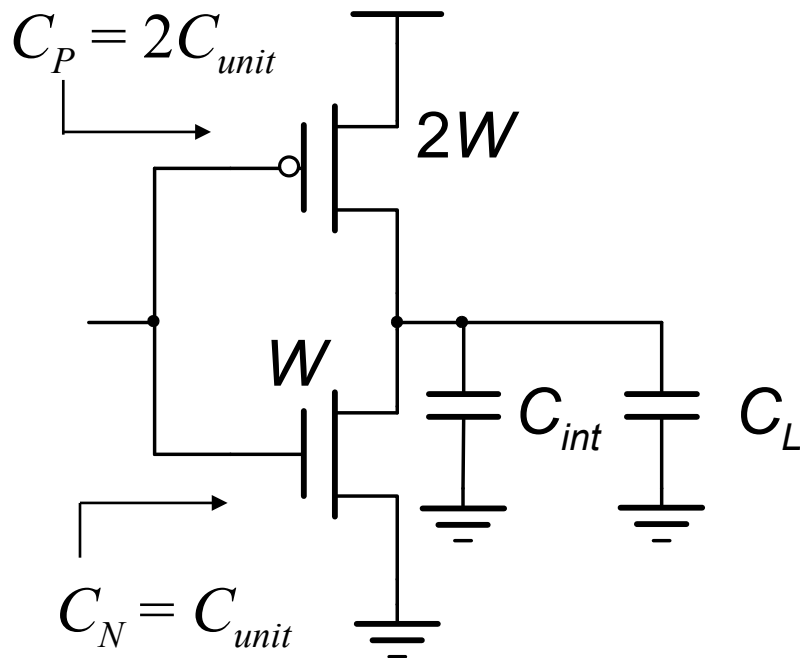

$$\begin{aligned}\text{Delay} &= kR_W(C_{int} + C_L) = kR_W C_{int} + kR_W C_L = kR_W C_{int}(1 + C_L / C_{int}) \\ &= \text{Delay (Internal)} + \text{Delay (Load)}\end{aligned}$$

# Delay Formula



$$C_{int} = \gamma C_{gin} \text{ with } \gamma \approx 1$$


$$f = C_L / C_{gin} - \text{effective fanout}$$

$$R = R_{unit} / W ; C_{int} = W C_{unit}$$

$$t_{p0} = 0.69 R_{unit} C_{unit}$$



# *Apply to Inverter Chain*

 

# Optimal Tapering for Given N

Delay equation has  $N - 1$  unknowns,  $C_{gin,2} - C_{gin,N}$

Minimize the delay, find  $N - 1$  partial derivatives

Result:  $C_{gin,j+1}/C_{gin,j} = C_{gin,j}/C_{gin,j-1}$

Size of each stage is the geometric mean of two neighbors

- each stage has the same effective fanout ( $C_{out}/C_{in}$ )
- each stage has the same delay


# *Optimum Delay and Number of Stages*

When each stage is sized by  $f$  and has same eff. fanout  $f$ :

Effective fanout of each stage:

Minimum path delay

# Example

 

$C_L/C_1$  has to be evenly distributed across  $N = 3$  stages:


# *Optimum Number of Stages*

For a given load,  $C_L$  and given input capacitance  $C_{in}$   
Find optimal sizing  $f$

For  $\gamma = 0$ ,  $f = e$ ,  $N = \ln F$
 
# Optimum Effective Fanout $f$


Optimum  $f$  for given process defined by  $\gamma$




$f_{opt} = 3.6$   
for  $\gamma=1$

# Impact of Self-Loading on $t_p$

No Self-Loading,  $\gamma=0$

 

With Self-Loading  $\gamma=1$

 


# *Normalized delay function of F*


<i>F</i>	Unbuffered	Two Stage	Inverter Chain
10	11	8.3	8.3
100	101	22	16.5
1000	1001	65	24.8
10,000	10,001	202	33.1




# Buffer Design

 


N	f	$t_p$
1	64	65

 

2	8	18
---	---	----

 

3	4	15
---	---	----

 

4	2.8	15.3
---	-----	------



# *Power Dissipation*

# *Where Does Power Go in CMOS?*

- **Dynamic Power Consumption**

Charging and Discharging Capacitors


- **Short Circuit Currents**

Short Circuit Path between Supply Rails during Switching

- **Leakage**

Leaking diodes and transistors

# Dynamic Power Dissipation

 


$$\text{Energy/transition} = C_L * V_{dd}^2$$

$$\text{Power} = \text{Energy/transition} * f = C_L * V_{dd}^2 * f$$

- Not a function of transistor sizes!
- Need to reduce  $C_L$ ,  $V_{dd}$ , and  $f$  to reduce power.
 
# Modification for Circuits with Reduced Swing




$$E_{0 \rightarrow 1} = C_L \cdot V_{dd} \cdot (V_{dd} - V_t)$$

- Can exploit reduced swing to lower power (e.g., reduced bit-line swing in memory)


# Adiabatic Charging

Charging a capacitor

 


$$CV_{dd}^2/2$$

Consider

 

$$v_c = \frac{1}{C} \cdot \int_0^T i dt = \frac{1}{C} \cdot I_{av} \cdot T \quad I_{av} = \frac{C \cdot v_c}{T}$$

 
$$E_{dis} = R \cdot \int_0^T i^2(t) dt \geq R \cdot \int_0^T I_{av}^2 dt = R \cdot I_{av}^2 \cdot T = \frac{RC}{T} \cdot C \cdot V_c^2$$


 
# Adiabatic Charging


$$V_I = RI + V_c = RC \frac{dv_c}{dt} + V_c$$

$V_I = \text{cst} \rightarrow$  Exponential current



$$E_R = CV_c^2 / 2$$

 $I = I_{av} \rightarrow$  Linear ramp on  $V_I$



*wins if  $T > 2RC$*

minimal energy  

$$E_R = RC/T CV_c^2$$

# Node Transition Activity and Power

- Consider switching a CMOS gate for  $N$  clock cycles

$$E_N = C_L \cdot V_{dd}^2 \cdot n(N)$$

$E_N$ : the energy consumed for  $N$  clock cycles

$n(N)$ : the number of 0→1 transition in  $N$  clock cycles


$$P_{avg} = \lim_{N \rightarrow \infty} \frac{E_N}{N} \cdot f_{clk} = \left( \lim_{N \rightarrow \infty} \frac{n(N)}{N} \right) \cdot C_L \cdot V_{dd}^2 \cdot f_{clk}$$

$$\alpha_{0 \rightarrow 1} = \lim_{N \rightarrow \infty} \frac{n(N)}{N}$$

$$P_{avg} = \alpha_{0 \rightarrow 1} \cdot C_L \cdot V_{dd}^2 \cdot f_{clk}$$



# Transistor Sizing for Minimum Energy

 


- Goal: Minimize Energy of whole circuit
  - Design parameters:  $f$  and  $V_{DD}$
  - $tp$  and  $tpref$  of circuit with  $f=1$  and  $V_{DD}=V_{ref}$

# *Transistor Sizing (2)*


- ❑ Performance Constraint ( $\gamma=1$ )
- ❑ Energy for single Transition

# Transistor Sizing (3)



$$V_{DD} = f(f)$$

 



$$\frac{E}{E_{ref}} = f(f)$$

 

# Short Circuit Currents

  

  
# *How to keep Short-Circuit Currents Low?*




Short circuit current goes to zero if  $t_{\text{fall}} \gg t_{\text{rise}}$ ,  
but can't do this for cascade logic, so ...

# Minimizing Short-Circuit Power

 

- Keep the input and output rise/fall times the same  
( $< 10\%$  of Total Consumption)  
from [Veendrick84]  
(*IEEE Journal of Solid-State Circuits*, August 1984)
- If  $V_{\text{dd}} < V_{\text{tn}} + |V_{\text{tp}}|$  then short-circuit power can be *eliminated*!


# Leakage

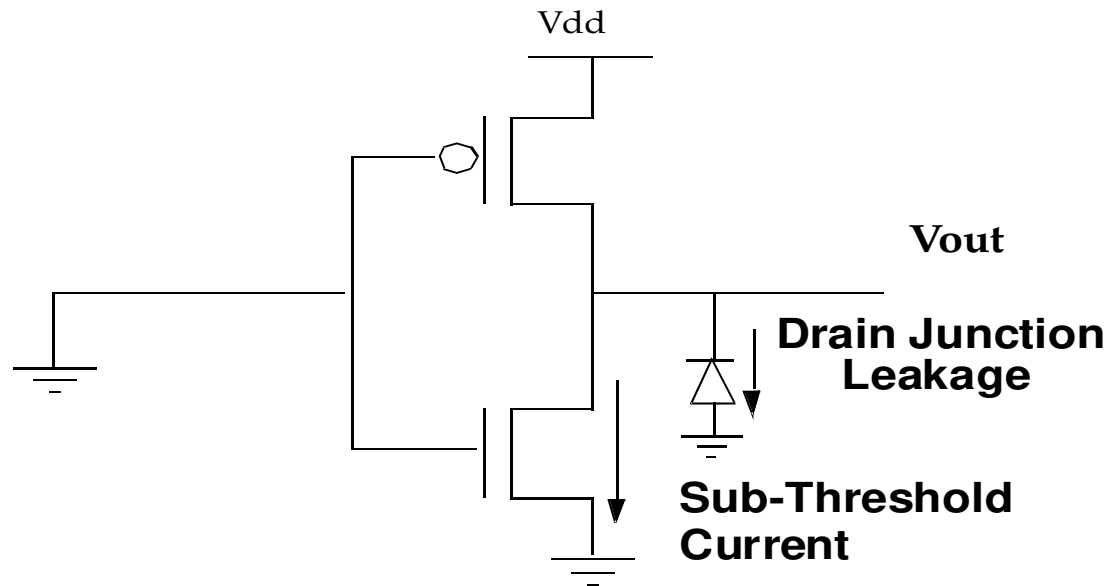

## Sub-Threshold Current Dominant Factor

Sub-threshold current one of most compelling issues in low-energy circuit design!

# Reverse-Biased Diode Leakage

 



$$I_{DL} = J_S \times A$$

- $J_S = 1\text{-}5\text{pA}/\mu\text{m}^2$  for a  $1.2\mu\text{m}$  CMOS technology
- $J_s$  double with every  $9^\circ\text{C}$  increase in temperature

$J_S = 10\text{-}100\text{ pA}/\mu\text{m}^2$  at  $25^\circ\text{C}$  for  $0.25\mu\text{m}$  CMOS  
 $J_S$  doubles for every  $9^\circ\text{C}$ !




# Subthreshold Leakage Component

  

- Leakage control is critical for low-voltage operation

# Static Power Consumption

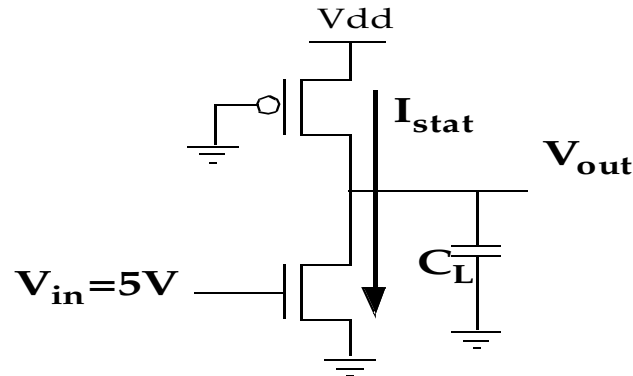

$$P_{\text{stat}} = P_{(I_n=1)} \cdot V_{\text{dd}} \cdot I_{\text{stat}}$$


- **Dominates over dynamic consumption**
- **Not a function of switching frequency**

Wasted energy ...

Should be avoided in almost all cases,  
but could help reducing energy in others (e.g. sense amps)
 
# *Principles for Power Reduction*

- ❑ Prime choice: Reduce voltage!
  - Recent years have seen an acceleration in supply voltage reduction
  - Design at very low voltages still open question (0.6 ... 0.9 V by 2010!)
- ❑ Reduce switching activity
- ❑ Reduce physical capacitance
  - Device Sizing: for  $F=20$ 
    - $f_{opt}(\text{energy})=3.53$ ,  $f_{opt}(\text{performance})=4.47$



# *Impact of Technology Scaling*

# *Goals of Technology Scaling*

- Make things cheaper:
  - Want to sell more functions (transistors) per chip for the same money
  - Build same products cheaper, sell the same part for less money
  - Price of a transistor has to be reduced
- But also want to be faster, smaller, lower power

# *Technology Scaling*

- ❑ Goals of scaling the dimensions by 30%:
  - Reduce gate delay by 30% (increase operating frequency by 43%)
  - Double transistor density
  - Reduce energy per transition by 65% (50% power savings @ 43% increase in frequency)
- ❑ Die size used to increase by 14% per generation
- ❑ Technology generation spans 2-3 years

# Technology Generations

Table 2. Time overlap of semiconductor technology generations.																	
95	96	97	98	99	00	01	02	03	04	05	06	07	08	09	10	11	12
350 nm	1	2	3	4	5												
-2	-1	250 nm	1	2	3	4	5										
-4	-3	-2	-1	180 nm	1	2	3	4	5								
-6	-5	-4	-3	-2	-1	150 nm	1	2	3	4	5						
-8	-7	-6	-5	-4	-3	-2	-1	130 nm	1	2	3	4	5				
-11	-10	-9	-8	-7	-6	-5	-4	-3	-2	-1	100 nm	1	2	3	4	5	
			-11	-10	-9	-8	-7	-6	-5	-4	-3	-2	-1	70 nm	1	2	3
						-11	-10	-9	-8	-7	-6	-5	-4	-3	-2	-1	50 nm

# Technology Evolution (2000 data)

International Technology Roadmap for Semiconductors

Year of Introduction	1999	2000	2001	2004	2008	2011	2014
Technology node [nm]	180		130	90	60	40	30
Supply [V]	1.5-1.8	1.5-1.8	1.2-1.5	0.9-1.2	0.6-0.9	0.5-0.6	0.3-0.6
Wiring levels	6-7	6-7	7	8	9	9-10	10
Max frequency [GHz], Local-Global	1.2	1.6-1.4	2.1-1.6	3.5-2	7.1-2.5	11-3	14.9-3.6
Max $\mu$ P power [W]	90	106	130	160	171	177	186
Bat. power [W]	1.4	1.7	2.0	2.4	2.1	2.3	2.5

Node years: 2007/65nm, 2010/45nm, 2013/33nm, 2016/23nm




# Technology Evolution (1999)

Year of Introduction	1994	1997	2000	2003	2006	2009
Channel length ( $\mu\text{m}$ )	0.4	0.3	0.25	0.18	0.13	0.1
Gate oxide (nm)	12	7	6	4.5	4	4
$V_{DD}$ (V)	3.3	2.2	2.2	1.5	1.5	1.5
$V_T$ (V)	0.7	0.7	0.7	0.6	0.6	0.6
NMOS $I_{Dsat}$ (mA/ $\mu\text{m}$ ) (@ $V_{GS} = V_{DD}$ )	0.35	0.27	0.31	0.21	0.29	0.33
PMOS $I_{Dsat}$ (mA/ $\mu\text{m}$ ) (@ $V_{GS} = V_{DD}$ )	0.16	0.11	0.14	0.09	0.13	0.16


# ITRS Technology Roadmap
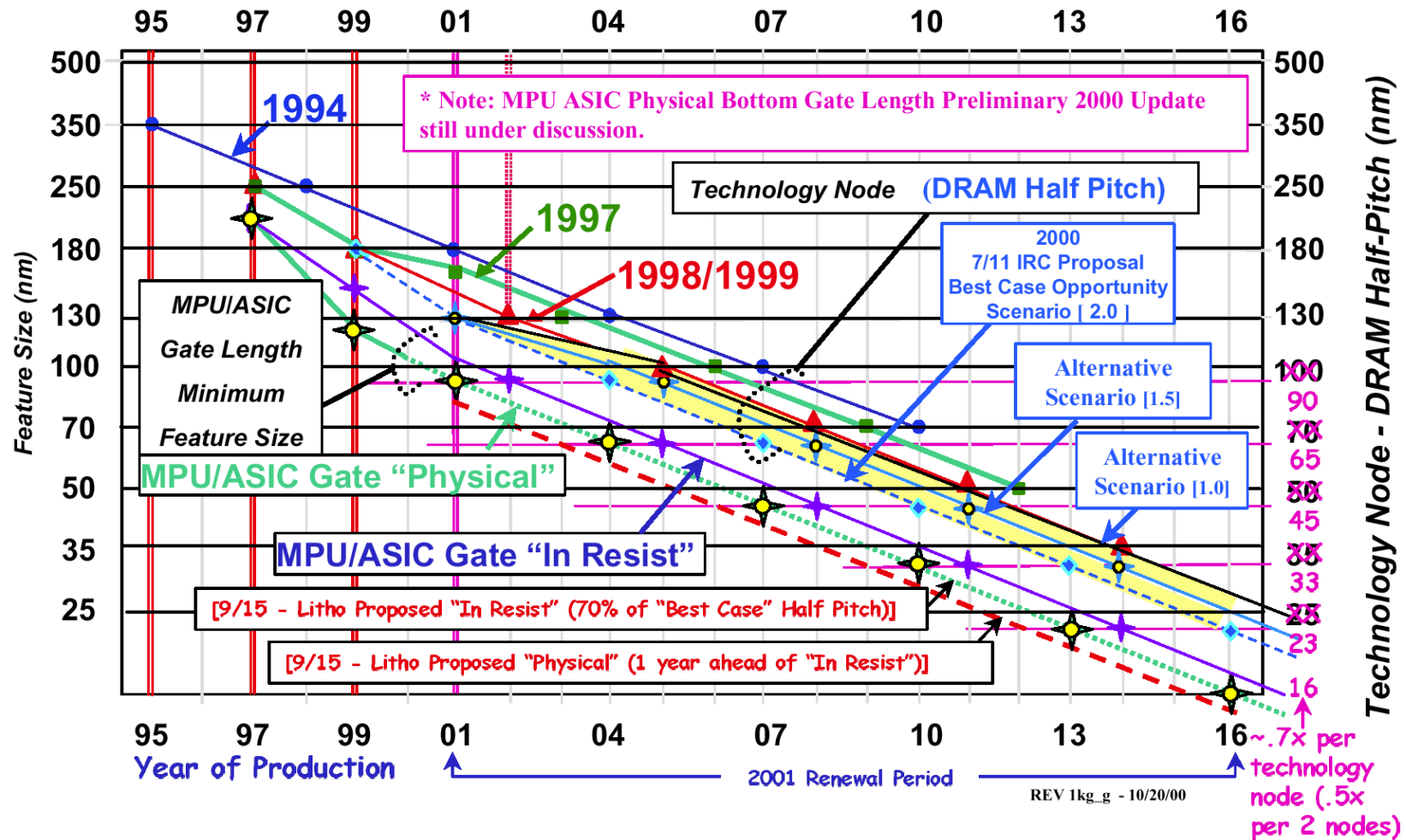
## Acceleration Continues

(Including MPU/ASIC "Physical Gate Length" Proposal)




# Technology Scaling (1)

 


***Minimum Feature Size***

# Technology Scaling (2)

 

***Number of components per chip***


# Technology Scaling (3)

 


$t_p$  decreases by 13%/year  
50% every 5 years!

## Propagation Delay

# Technology Scaling (4)

 

(a) Power dissipation vs. year.

 

(b) Power density vs. scaling factor.

From Kuroda

# *Technology Scaling Models*

- **Full Scaling (Constant Electrical Field)**

ideal model — dimensions and voltage scale together by the same factor  $S$

- **Fixed Voltage Scaling**

most common model until recently —  
only dimensions scale, voltages remain constant

- **General Scaling**

most realistic for today's situation —  
voltages and dimensions scale with different factors

# Scaling Relationships for Long Channel Devices

Parameter	Relation	Full Scaling	General Scaling	Fixed Voltage Scaling
$W, L, t_{ox}$		$1/S$	$1/S$	$1/S$
$V_{DD}, V_T$		$1/S$	$1/U$	$1$
$N_{SUB}$	$V/W_{depl}^2$	$S$	$S^2/U$	$S^2$
Area/Device	$WL$	$1/S^2$	$1/S^2$	$1/S^2$
$C_{ox}$	$1/t_{ox}$	$S$	$S$	$S$
$C_L$	$C_{ox}WL$	$1/S$	$1/S$	$1/S$
$k_n, k_p$	$C_{ox}W/L$	$S$	$S$	$S$
$I_{av}$	$k_{n,p} V^2$	$1/S$	$S/U^2$	$S$
$t_p$ (intrinsic)	$C_L V / I_{av}$	$1/S$	$U/S^2$	$1/S^2$
$P_{av}$	$C_L V^2 / t_p$	$1/S^2$	$S/U^3$	$S$
PDP	$C_L V^2$	$1/S^3$	$1/SU^2$	$1/S$




# Transistor Scaling

## (velocity-saturated devices)


Parameter	Relation	Full Scaling	General Scaling	Fixed-Voltage Scaling
$W, L, t_{ox}$		$1/S$	$1/S$	$1/S$
$V_{DD}, V_T$		$1/S$	$1/U$	1
$N_{SUB}$	$V/W_{depl}^2$	$S$	$S^2/U$	$S^2$
Area/Device	$WL$	$1/S^2$	$1/S^2$	$1/S^2$
$C_{ox}$	$1/t_{ox}$	$S$	$S$	$S$
$C_{gate}$	$C_{ox}WL$	$1/S$	$1/S$	$1/S$
$k_n, k_p$	$C_{ox}W/L$	$S$	$S$	$S$
$I_{sat}$	$C_{ox}WV$	$1/S$	$1/U$	1
Current Density	$I_{sat}/Area$	$S$	$S^2/U$	$S^2$
$R_{on}$	$V/I_{sat}$	1	1	1
Intrinsic Delay	$R_{on}C_{gate}$	$1/S$	$1/S$	$1/S$
$P$	$I_{sat}V$	$1/S^2$	$1/U^2$	1
Power Density	$P/Area$	1	$S^2/U^2$	$S^2$

# *$\mu$ Processor Scaling*

 


P.Gelsinger:  $\mu$ Processors for the New Millenium, ISSCC 2001

# $\mu$ Processor Power

 

P.Gelsinger:  $\mu$ Processors for the New Millenium, ISSCC 2001

# *$\mu$ Processor Performance*

 

P.Gelsinger:  $\mu$ Processors for the New Millenium, ISSCC 2001

# 2010 Outlook

## ❑ Performance 2X/16 months

- 1 TIP (terra instructions/s)
- 30 GHz clock

## ❑ Size

- No of transistors: 2 Billion
- Die: 40\*40 mm

## ❑ Power

- 10kW!!
- Leakage: 1/3 active Power

P.Gelsinger:  $\mu$ Processors for the New Millenium, ISSCC 2001

# *Some interesting questions*

- ❑ What will cause this model to break?
- ❑ When will it break?
- ❑ Will the model gradually slow down?
  - Power and power density
  - Leakage
  - Process Variation