



Digital Integrated Circuits


A Design Perspective

Jan M. Rabaey
Anantha Chandrakasan
Borivoje Nikolic

Designing Sequential Logic Circuits

November 2002

Sequential Logic

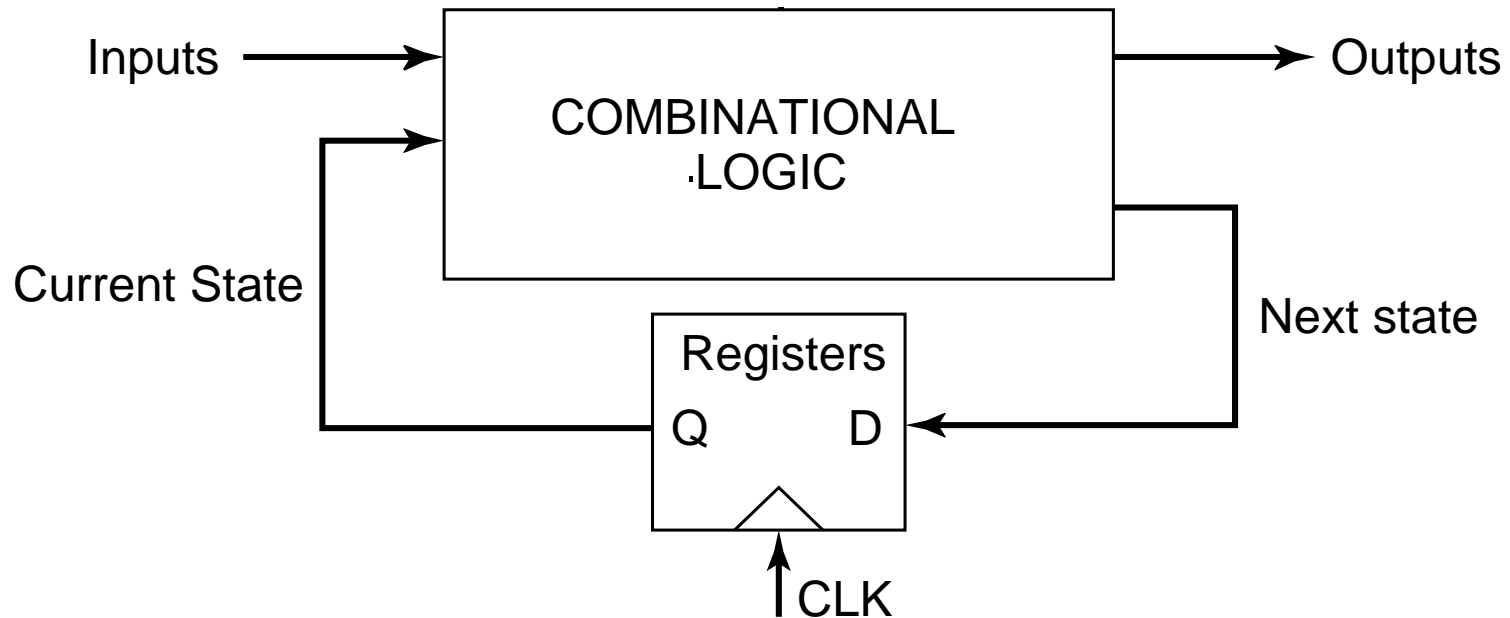

2 storage mechanisms

- positive feedback
- charge-based



Naming Conventions

- ❑ In our text:
 - a latch is level sensitive
 - a register is edge-triggered
- ❑ There are many different naming conventions
 - For instance, many books call edge-triggered elements flip-flops
 - This leads to confusion however

Latch versus Register



❑ Latch

stores data when
clock is low

  


❑ Register

stores data when
clock rises

  


Latches

Positive Latch

 


Negative Latch

 



Latch-Based Design

- N latch is transparent when $\phi = 0$


- P latch is transparent when $\phi = 1$

 


Timing Definitions

 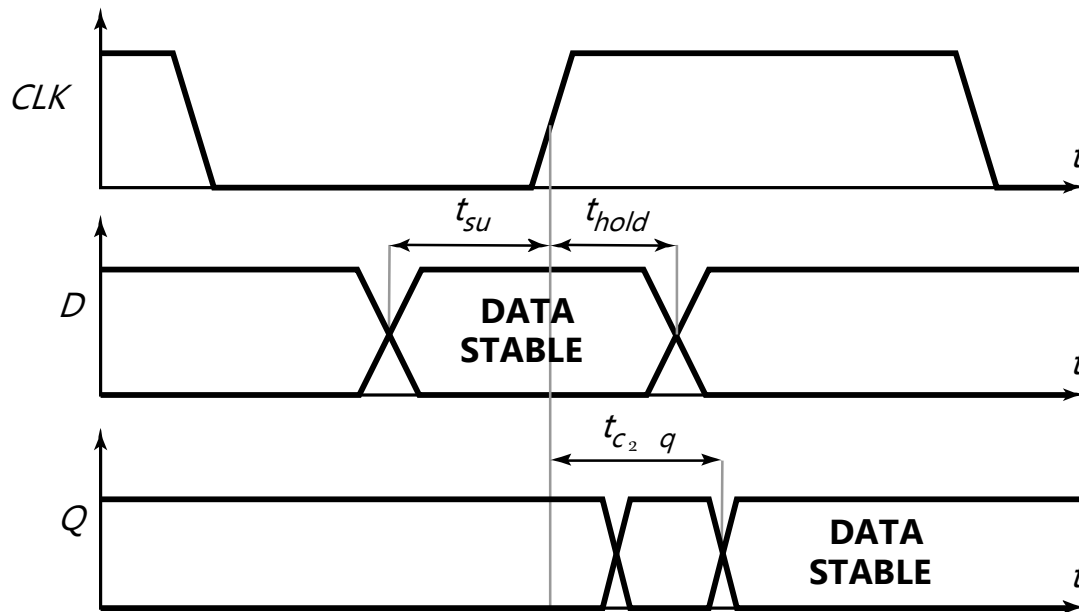

Characterizing Timing

 


Register

 

Latch

Maximum Clock Frequency

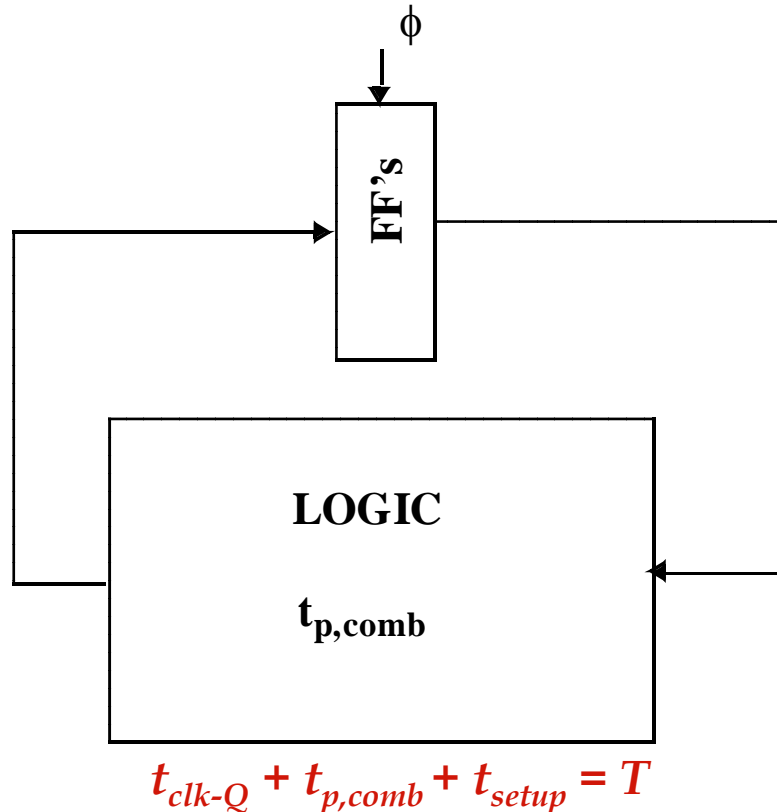


Also:



$$t_{cdreg} + t_{cdlogic} > t_{hold}$$

t_{cd} : contamination delay =
minimum delay

Positive Feedback: Bi-Stability

 


Meta-Stability

  


Gain should be larger than 1 in the transition region

Writing into a Static Latch

 Use the clock as a decoupling signal,
that distinguishes between the transparent and opaque states




Converting into a MUX

 

Forcing the state
(can implement as NMOS-only)


Mux-Based Latches

Negative latch
(transparent when CLK= 0)

 


$$Q = \overline{Clk} \cdot Q + Clk \cdot In$$

Positive latch
(transparent when CLK= 1)

 


$$Q = Clk \cdot Q + \overline{Clk} \cdot In$$


Mux-Based Latch

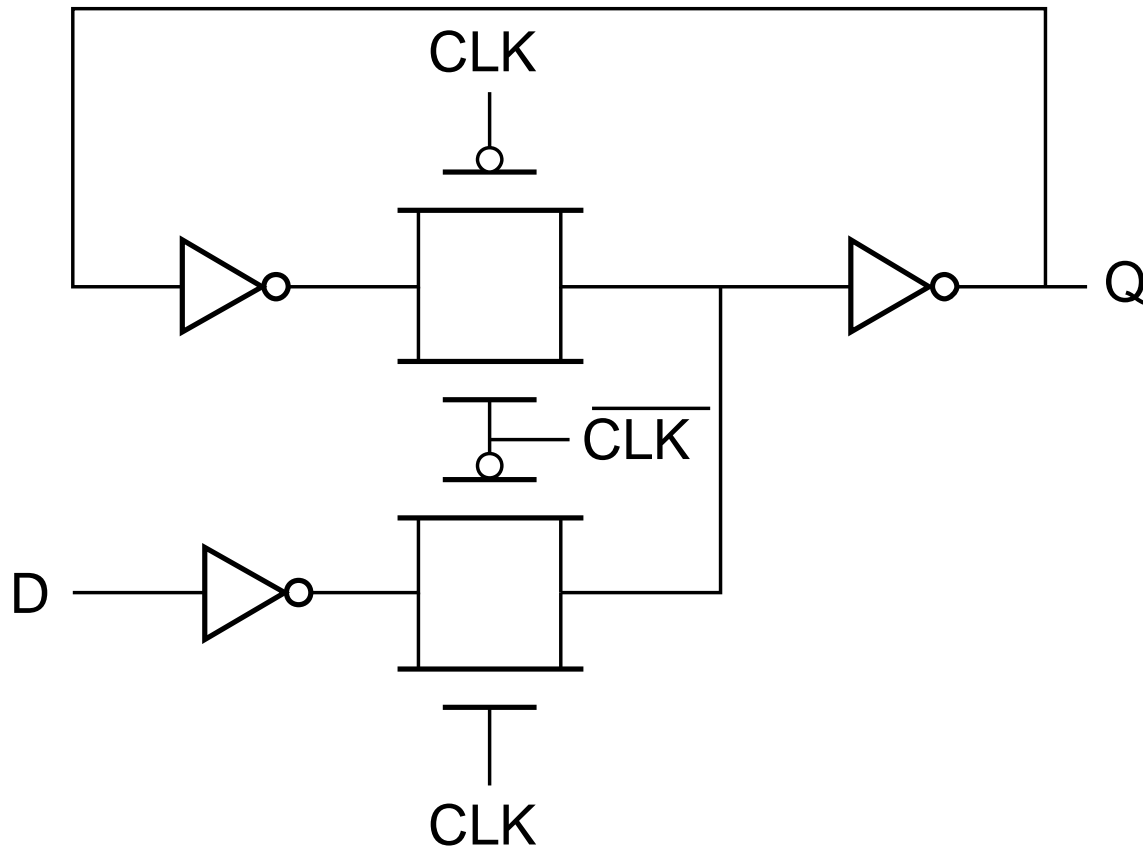

Mux-Based Latch

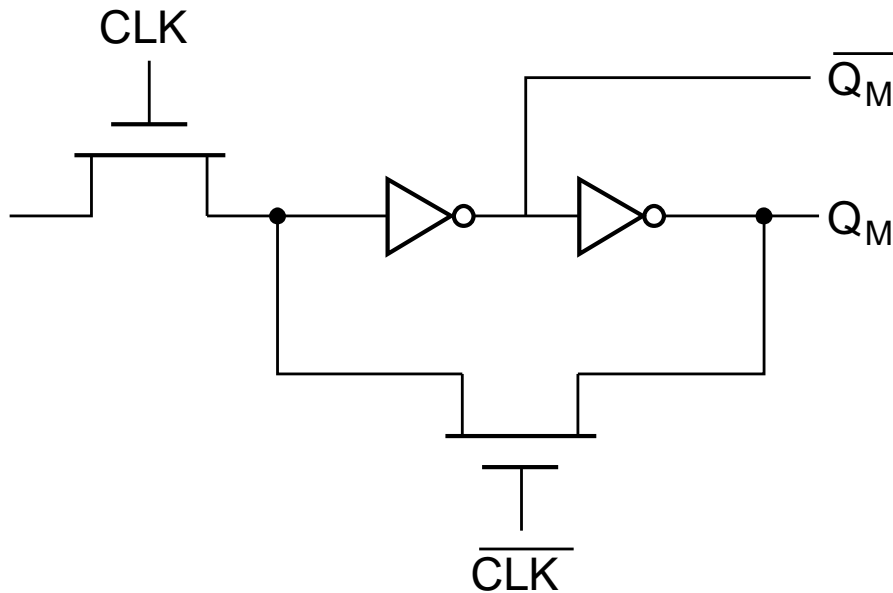


NMOS only

 

Non-overlapping clocks


Master-Slave (Edge-Triggered) Register

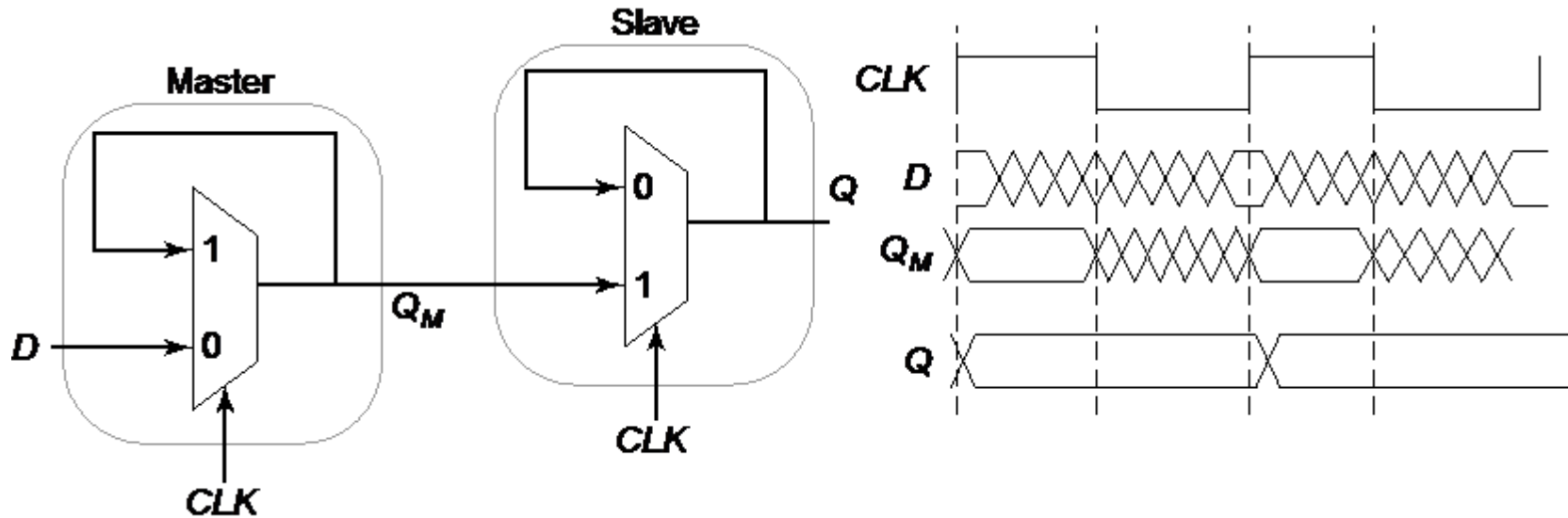


Two opposite latches trigger on edge
Also called master-slave latch pair

Master-Slave Register


Multiplexer-based latch pair

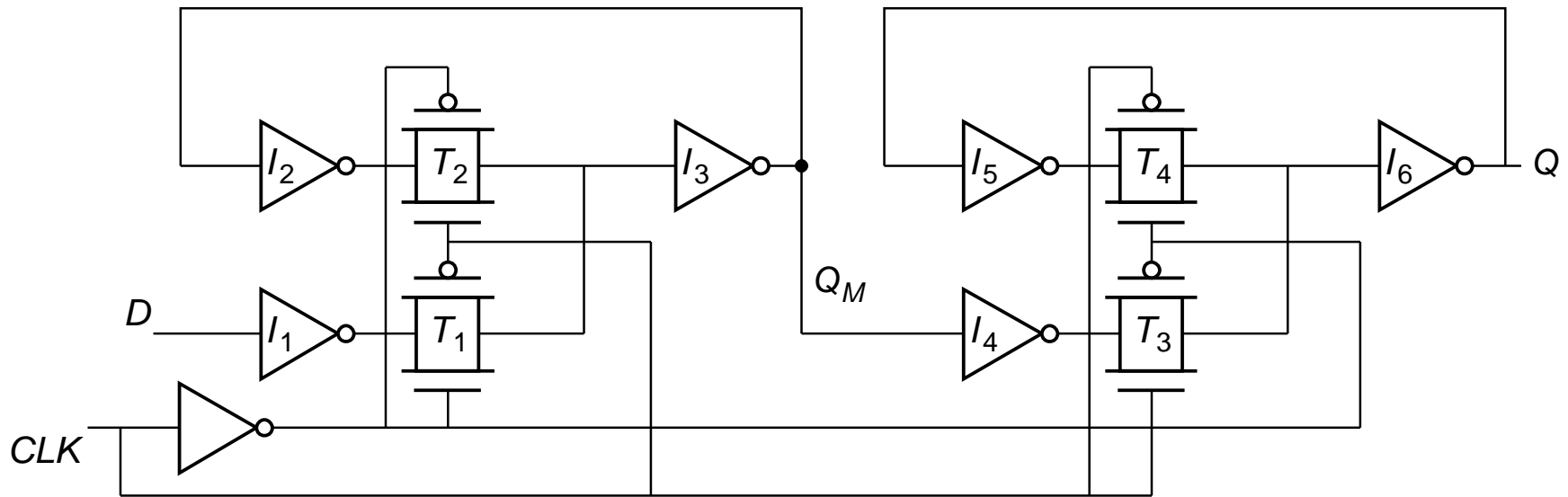


Clk-Q Delay

 

Setup Time

 


(a) $T_{setup} 5 0.21 \text{ nsec}$

 


(b) $T_{setup} 5 0.20 \text{ nsec}$


Reduced Clock Load Master-Slave Register

 

Avoiding Clock Overlap

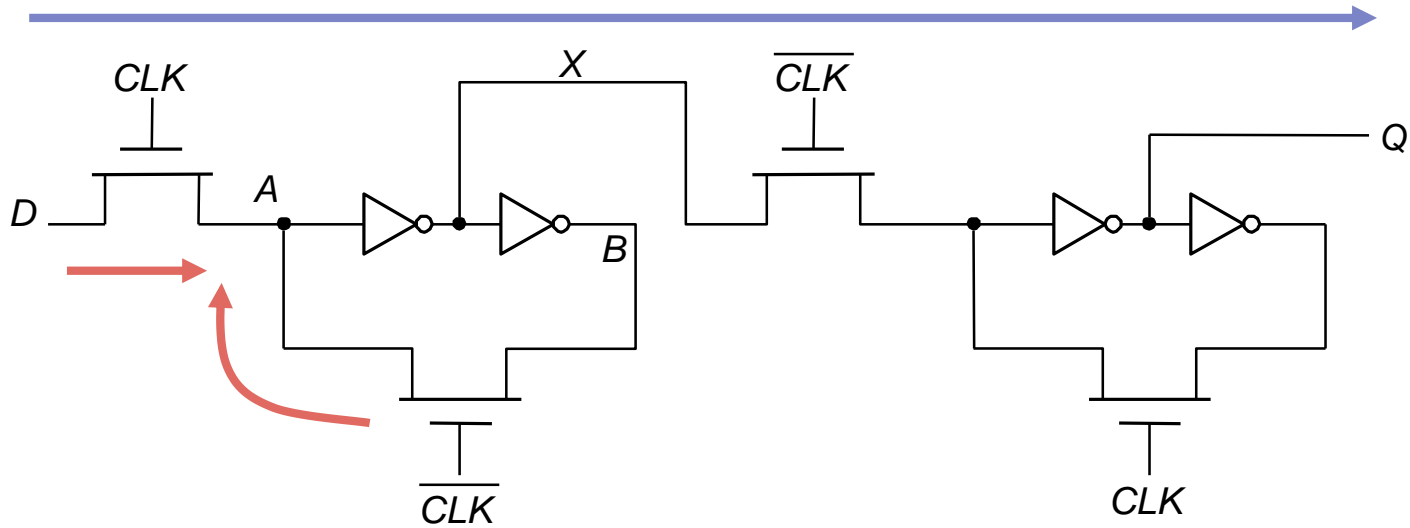



(a) Schematic diagram

 

(b) Overlapping clock pairs

Overpowering the Feedback Loop — Cross-Coupled Pairs

NOR-based set-reset

 
 


S	R	Q	\bar{Q}
0	0	Q	\bar{Q}
1	0	1	0
0	1	0	1
1	1	0	0

Forbidden State


Cross-Coupled NAND

Cross-coupled NANDs

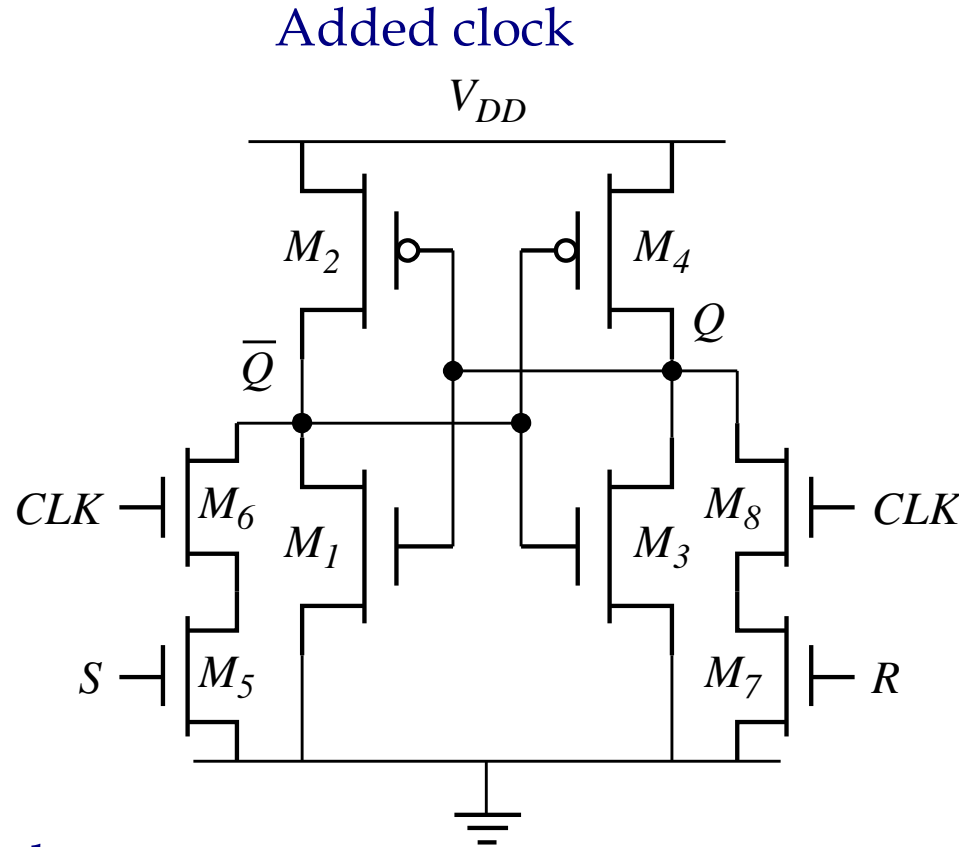 


This is not used in datapaths any more,
but is a basic building memory cell

Sizing Issues

 

 
Output voltage dependence
on transistor width




Transient response

Storage Mechanisms


Static

 



Dynamic (charge-based)

 

Making a Dynamic Latch Pseudo-Static

 


More Precise Setup Time

  


Setup/Hold Time Illustrations

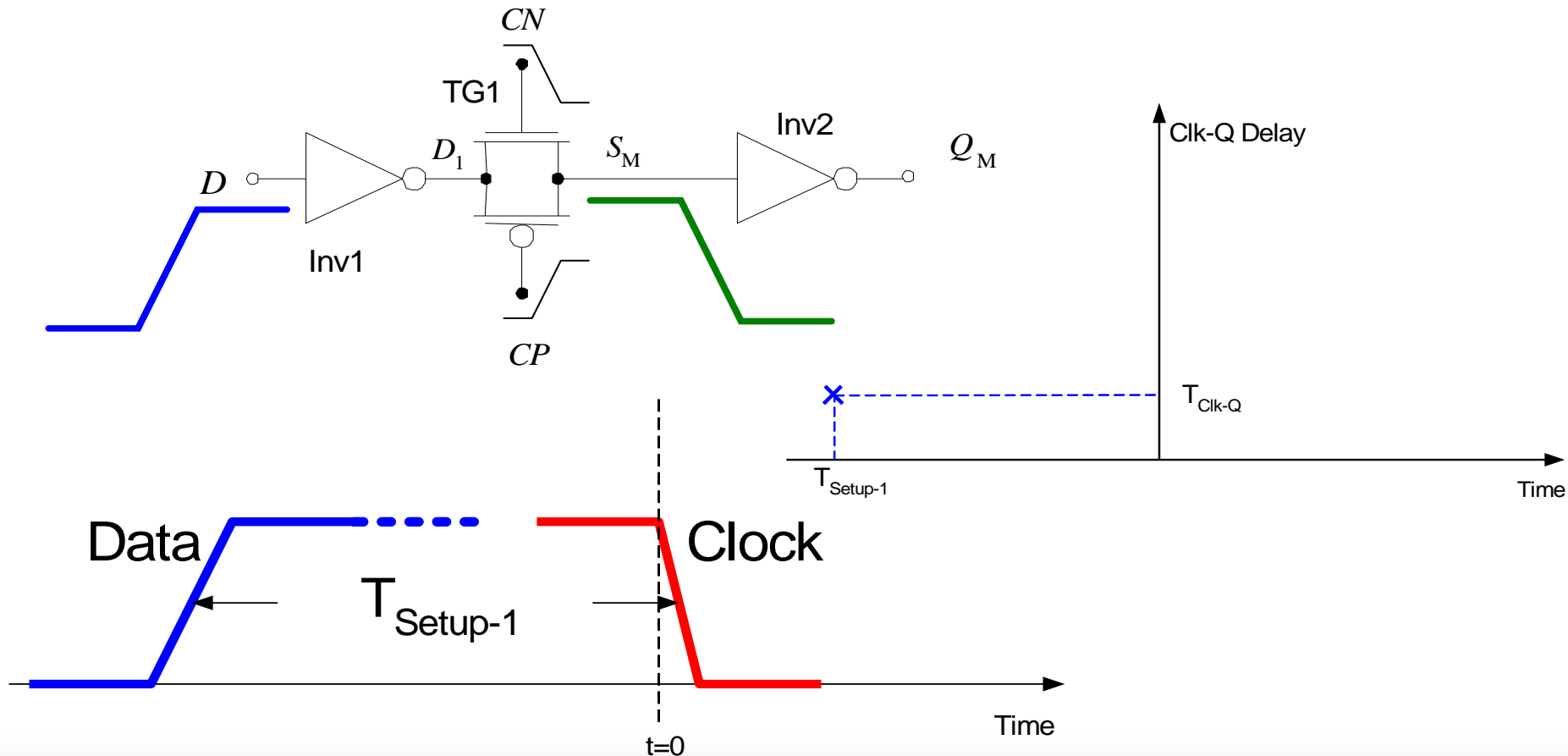Circuit before clock arrival (Setup-1 case)




Setup/Hold Time Illustrations

 Circuit before clock arrival (Setup-1 case)




Setup/Hold Time Illustrations

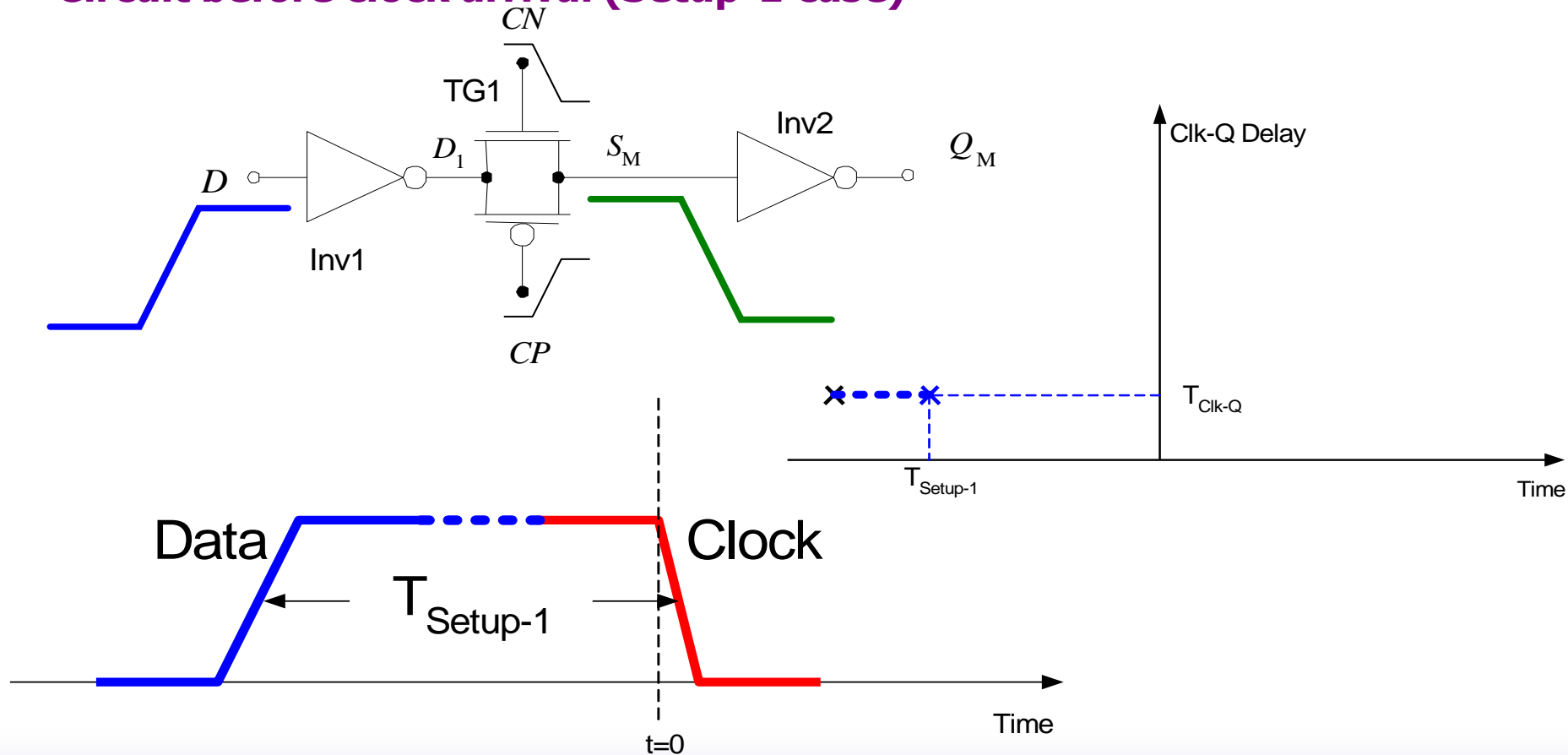Circuit before clock arrival (Setup-1 case)




Setup/Hold Time Illustrations

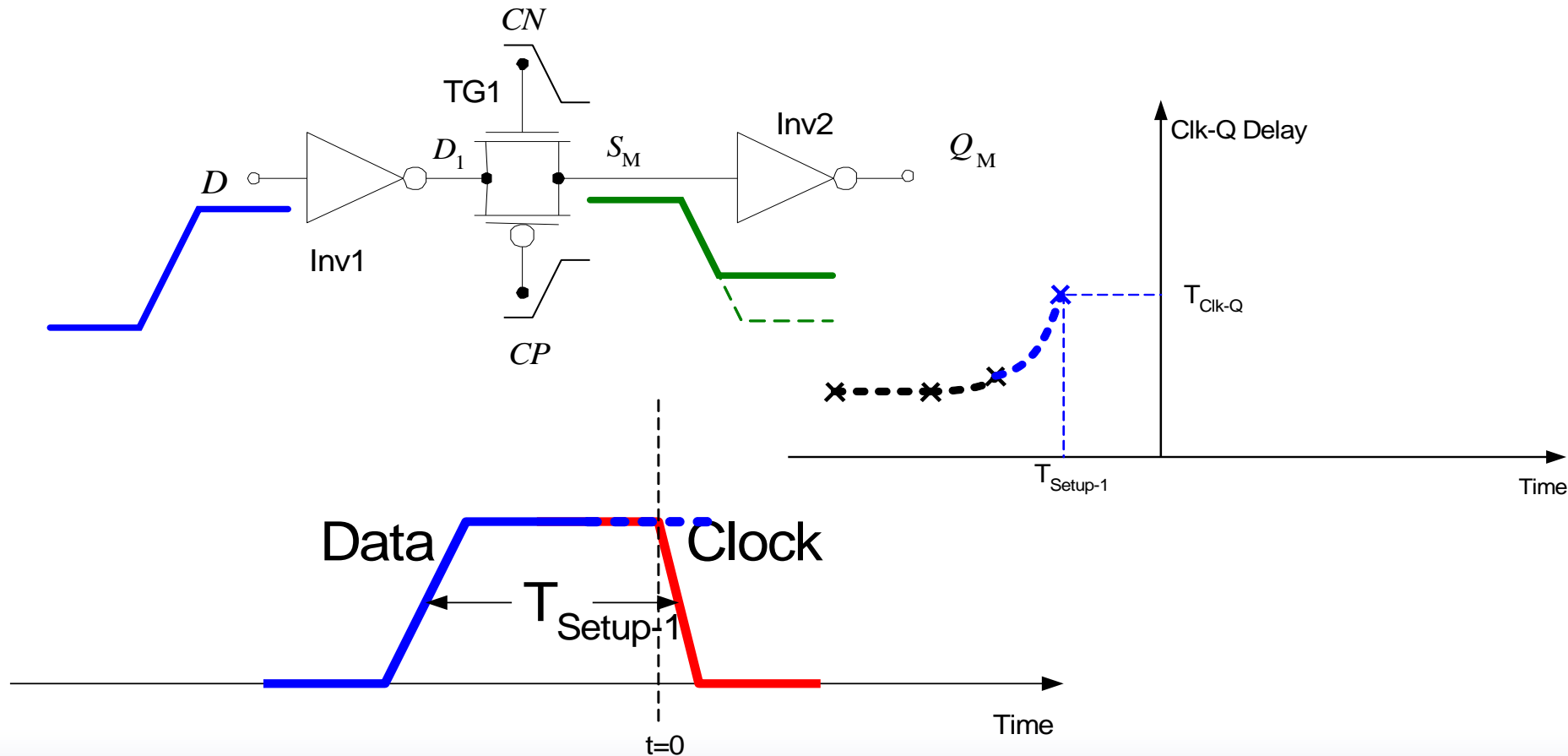Circuit before clock arrival (Setup-1 case)




Setup/Hold Time Illustrations

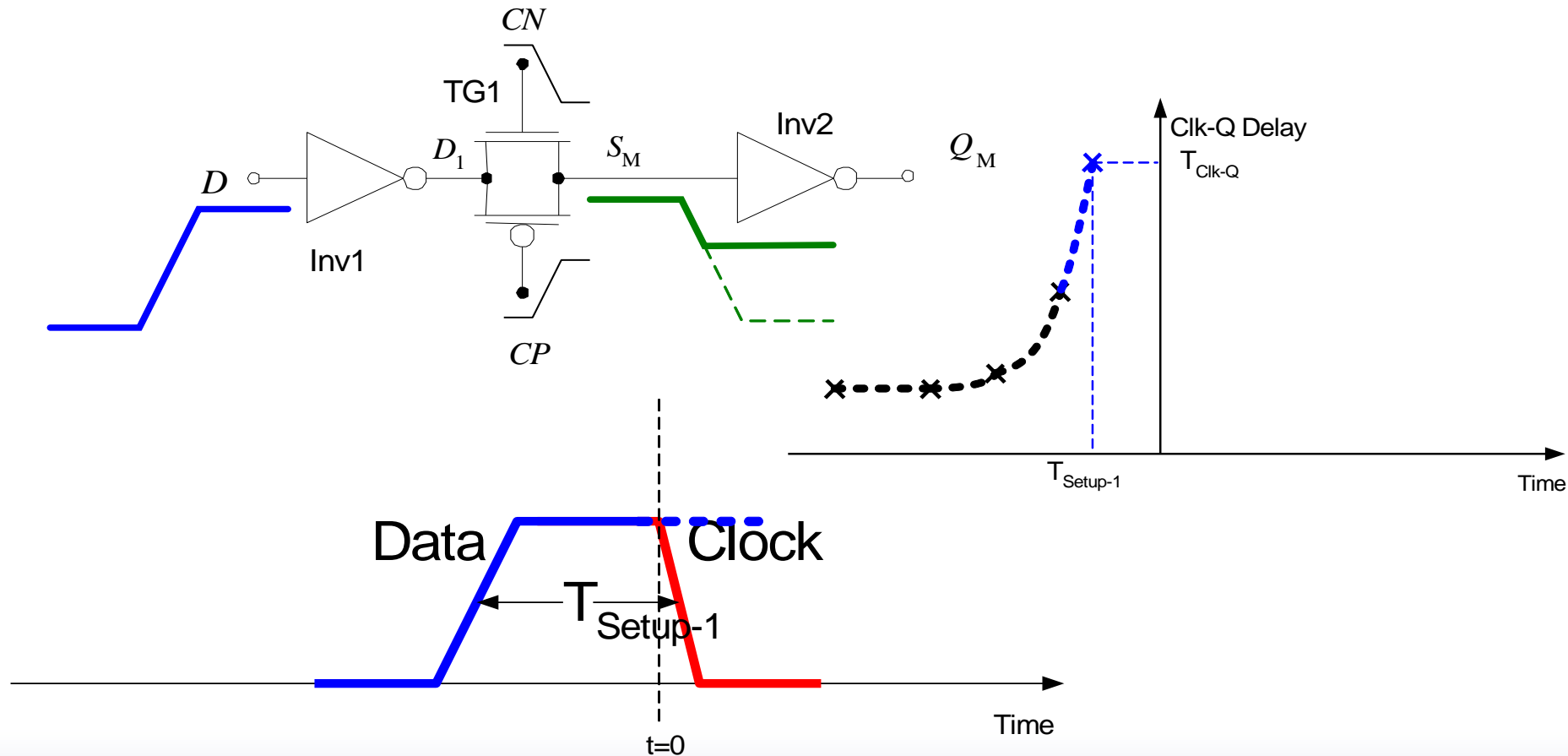Circuit before clock arrival (Setup-1 case)




Setup/Hold Time Illustrations

Hold-1 case

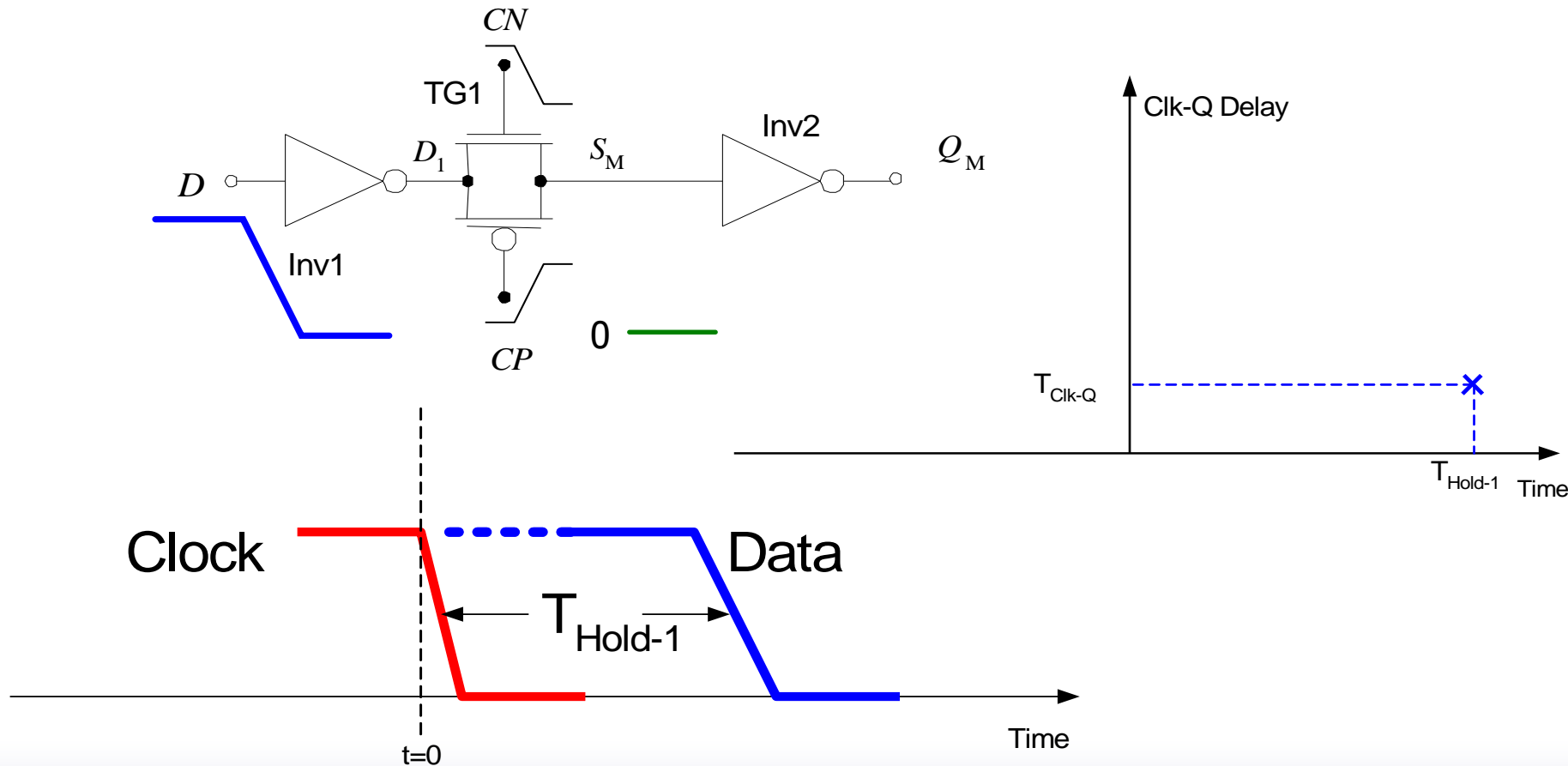


Setup/Hold Time Illustrations

Hold-1 case

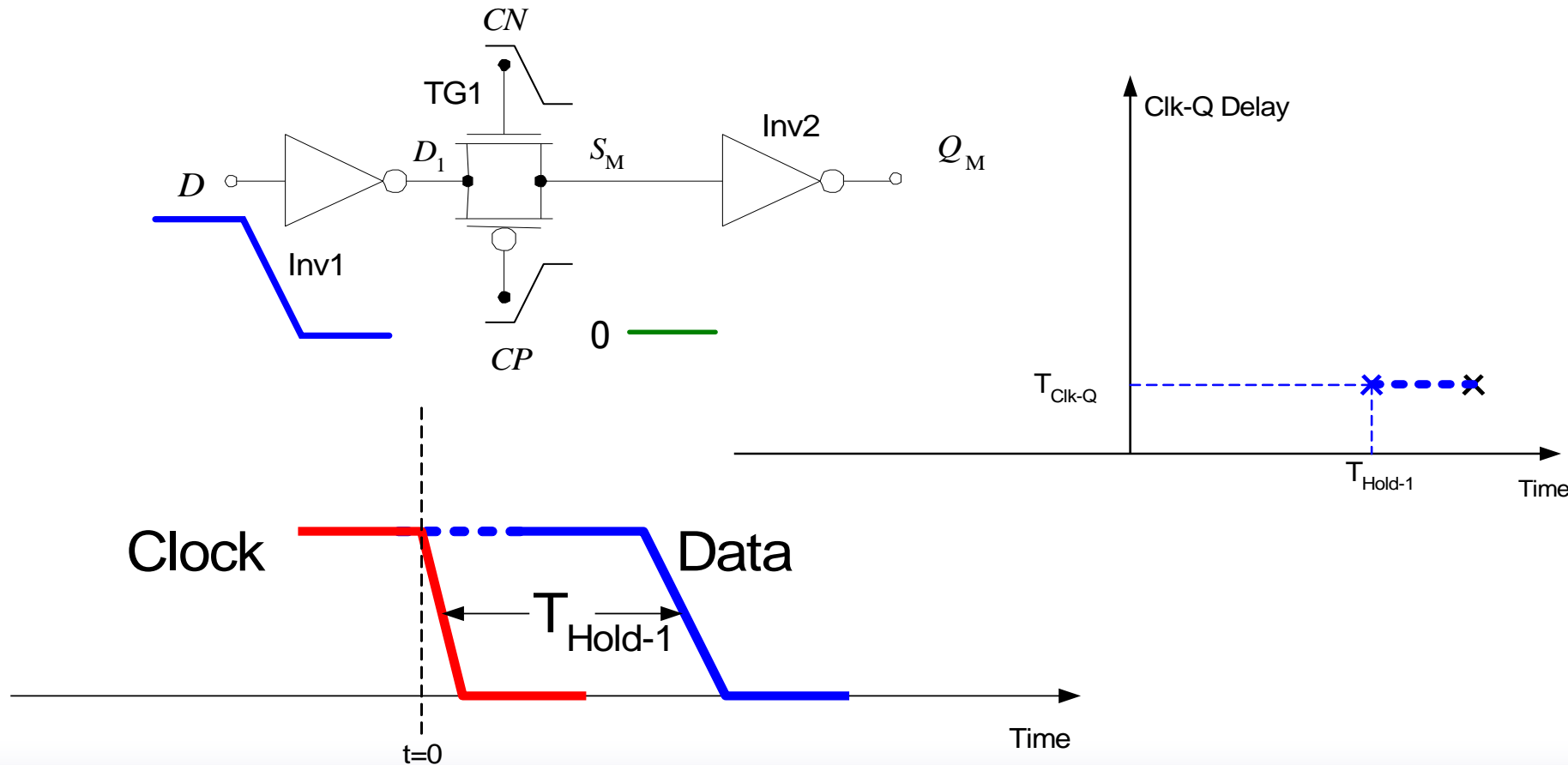


Setup/Hold Time Illustrations

Hold-1 case

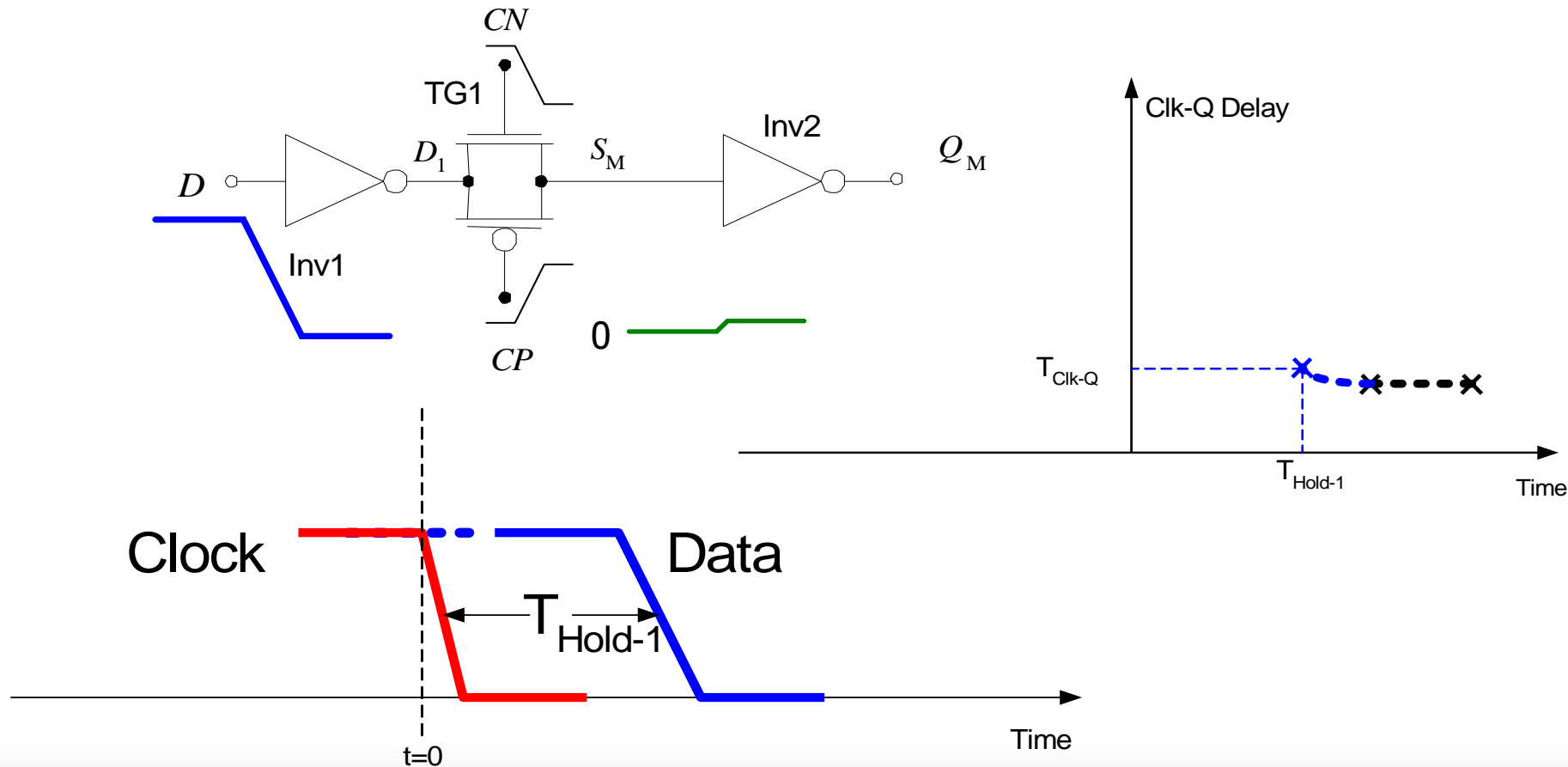


Setup/Hold Time Illustrations

Hold-1 case

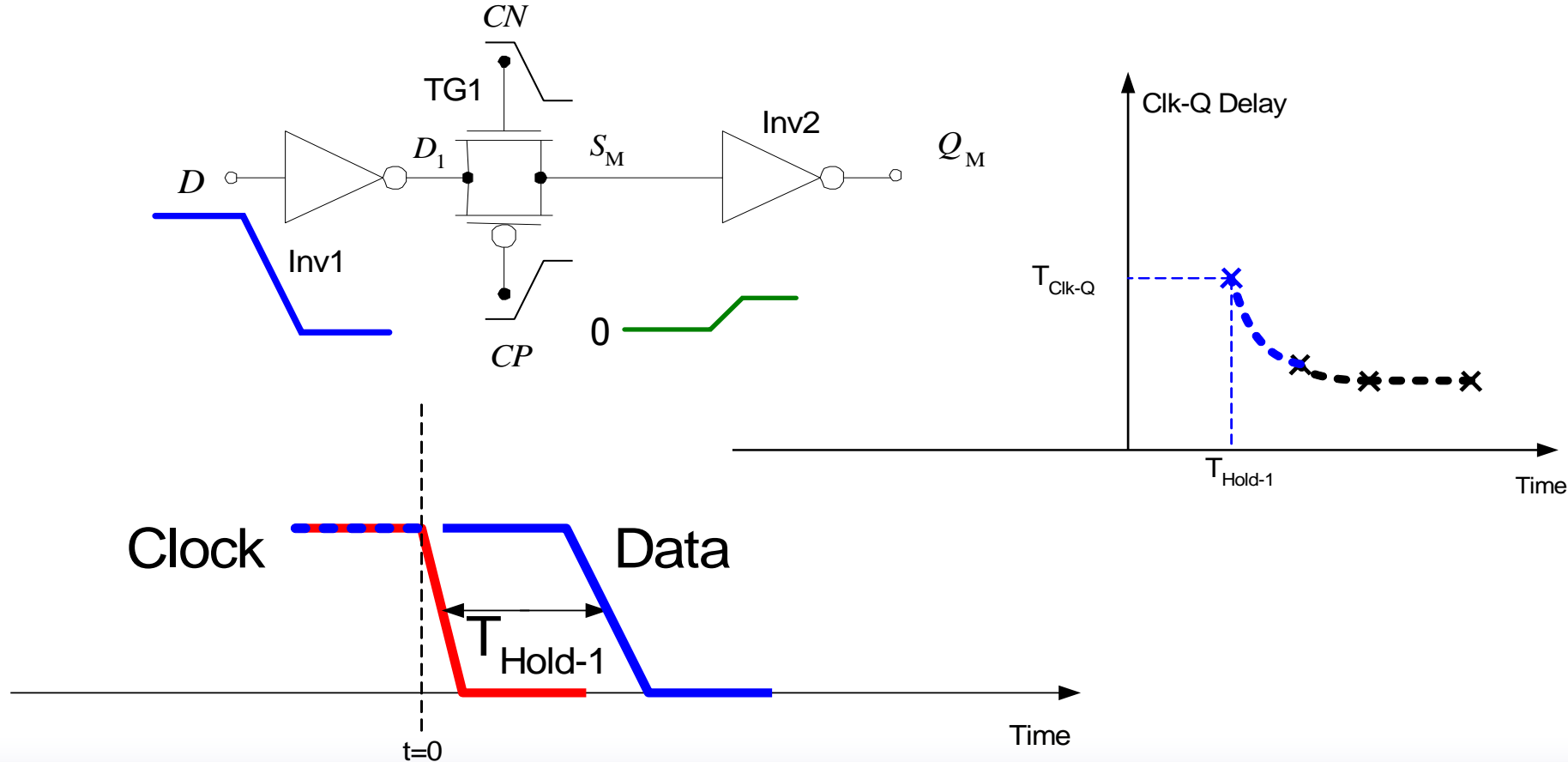


Setup/Hold Time Illustrations

Hold-1 case

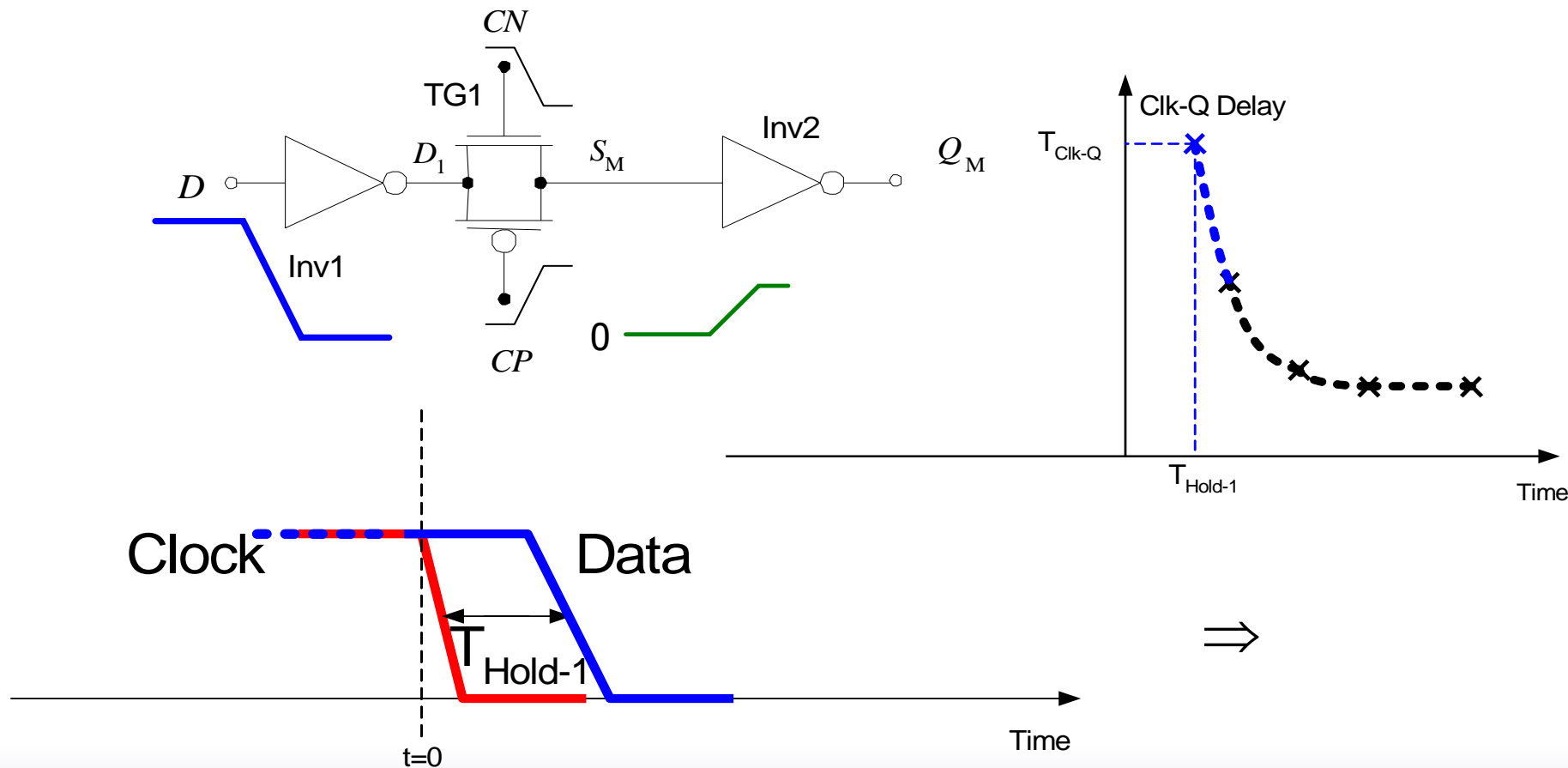


Other Latches/Registers: C²MOS

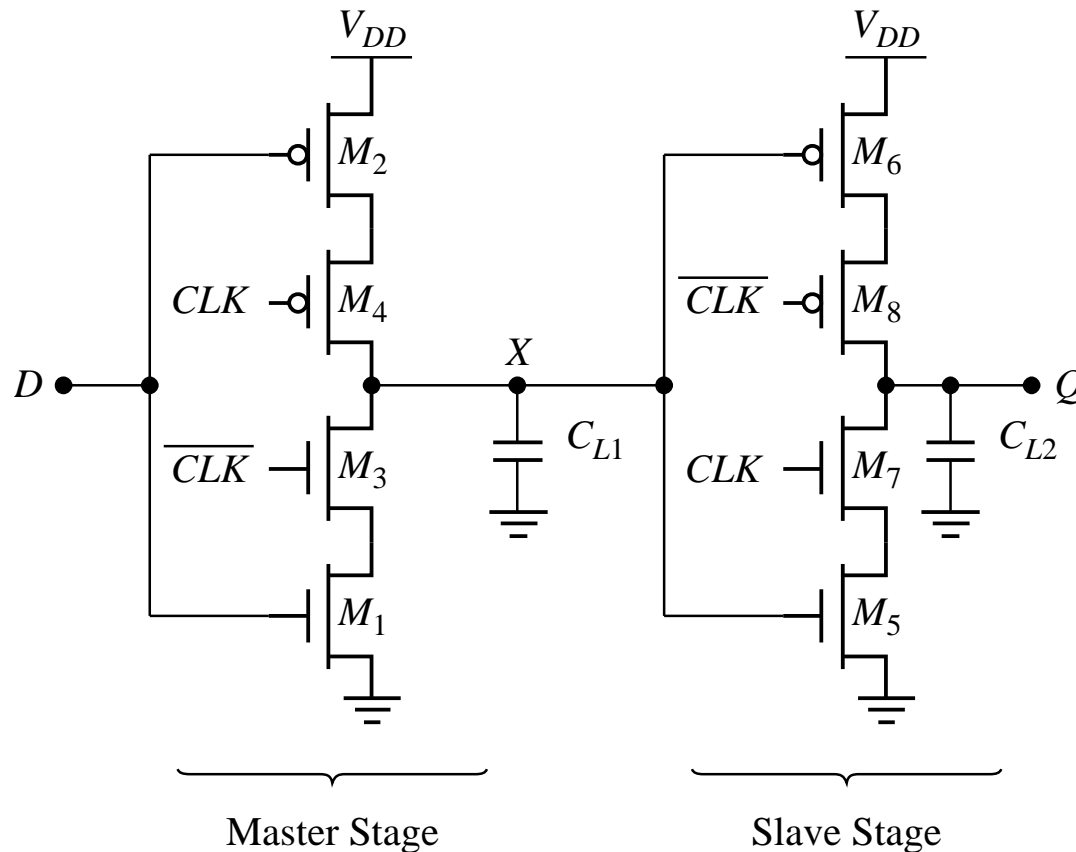


“Keepers” can be added to make circuit pseudo-static

Insensitive to Clock-Overlap

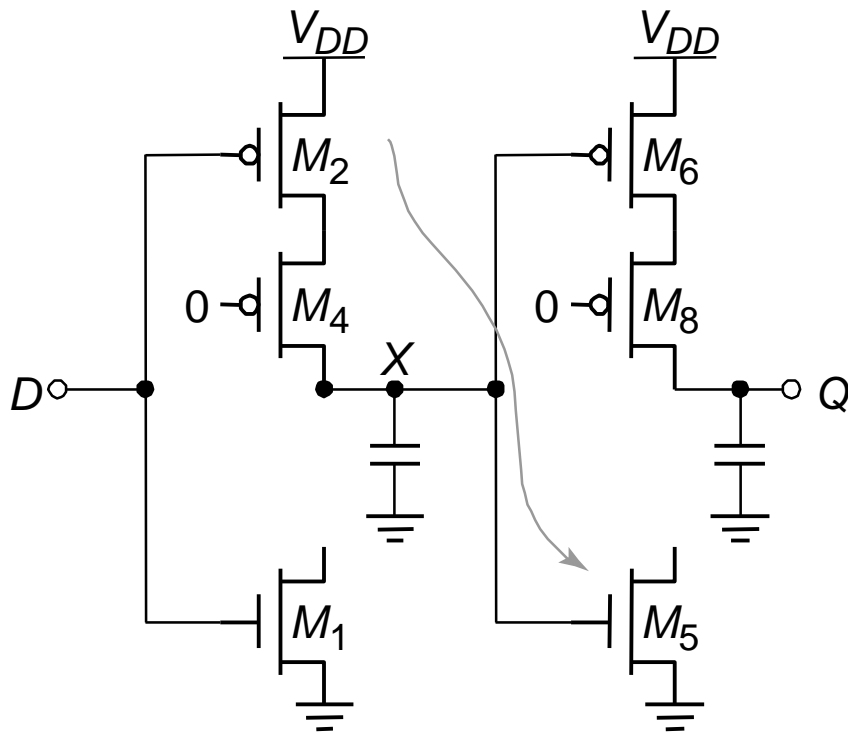


(a) (0-0) overlap

 


(b) (1-1) overlap

Pipelining

 


Reference

 

Pipelined


Clock Period	Adder	Absolute Value	Logarithm
1	$a_1 + b_1$		
2	$a_2 + b_2$	$ a_1 + b_1 $	
3	$a_3 + b_3$	$ a_2 + b_2 $	$\log(a_1 + b_1)$
4	$a_4 + b_4$	$ a_3 + b_3 $	$\log(a_2 + b_2)$
5	$a_5 + b_5$	$ a_4 + b_4 $	$\log(a_3 + b_3)$

Other Latches/Registers: TSPC

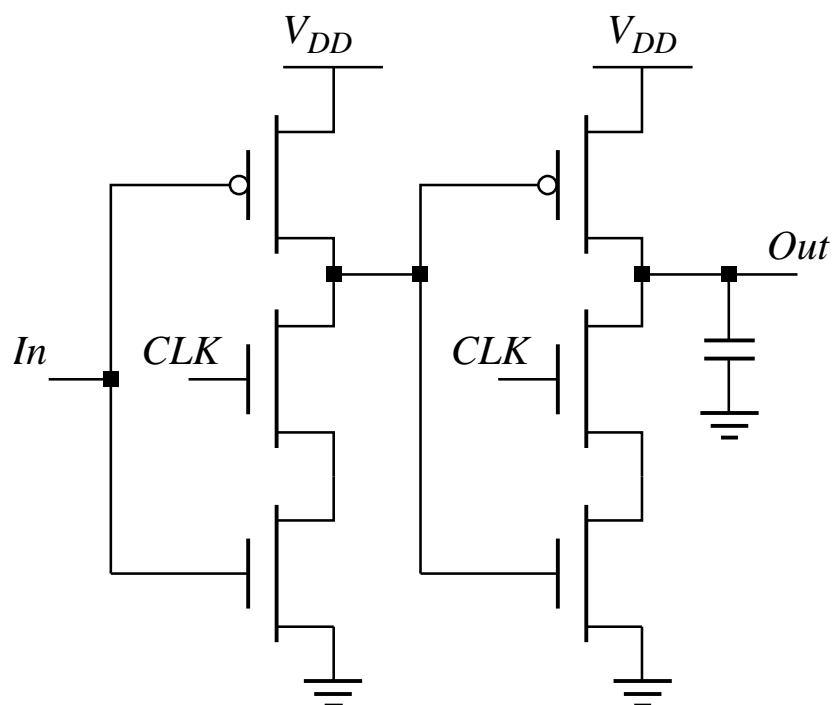

Positive latch


(transparent when $CLK = 1$)

 


Negative latch

(transparent when $CLK = 0$)

Including Logic in TSPC

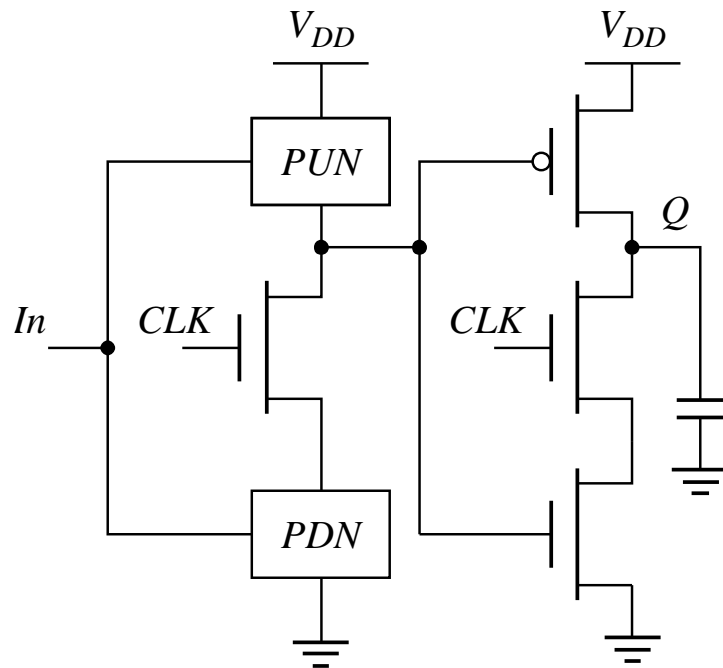


Example: logic inside the latch

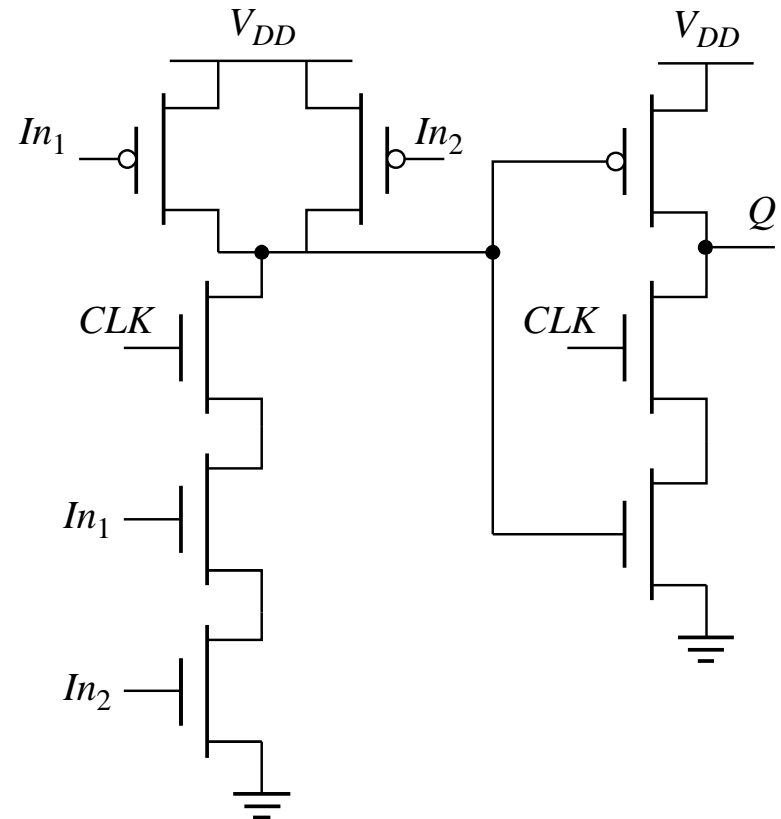

AND latch

TSPC Register

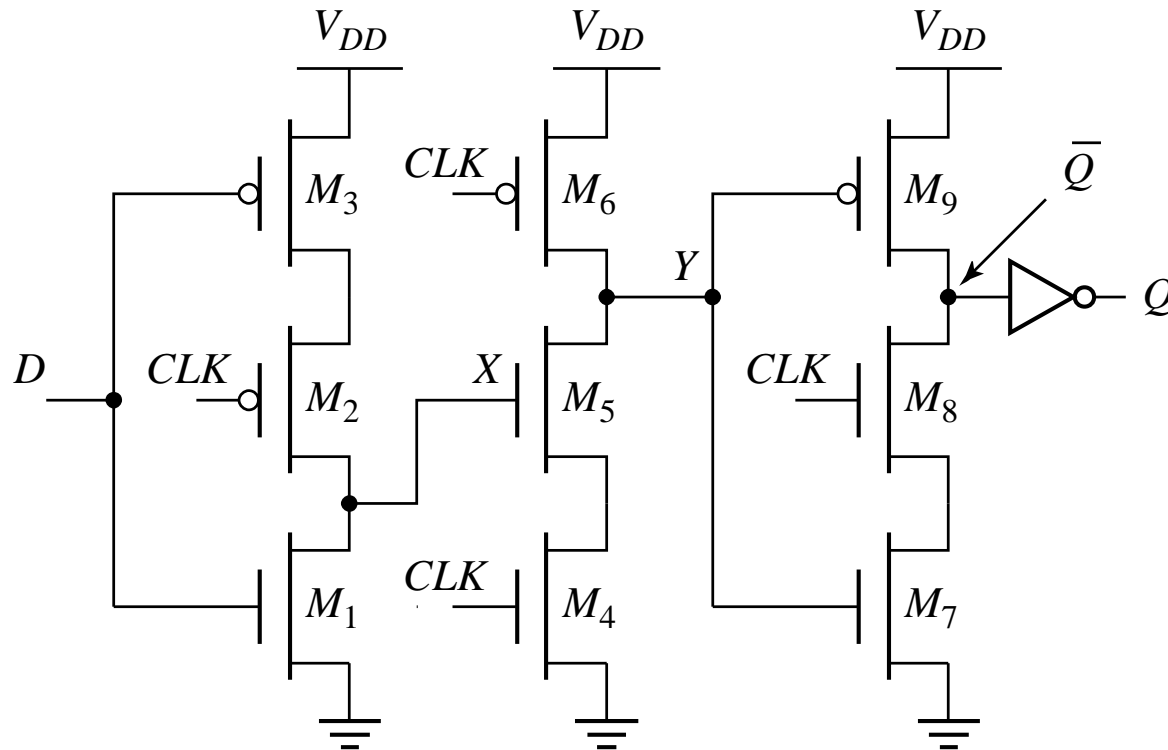


Pulse-Triggered Latches


An Alternative Approach

Ways to design an edge-triggered sequential cell:


Master-Slave
Latches

 


Pulse-Triggered
Latch

 


Pulsed Latches

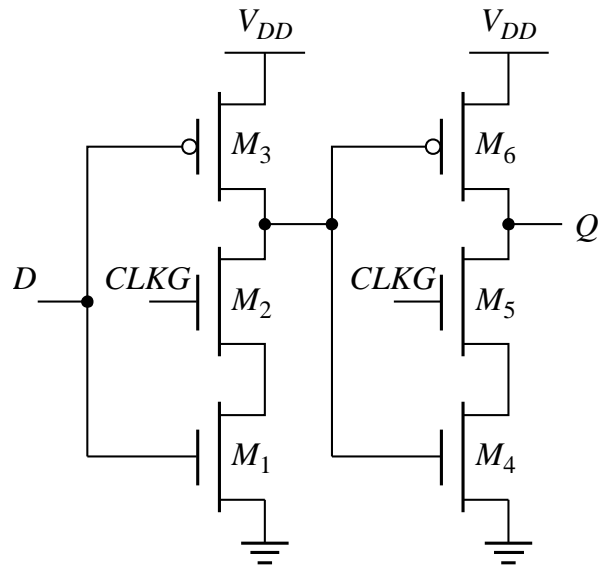

(a) register

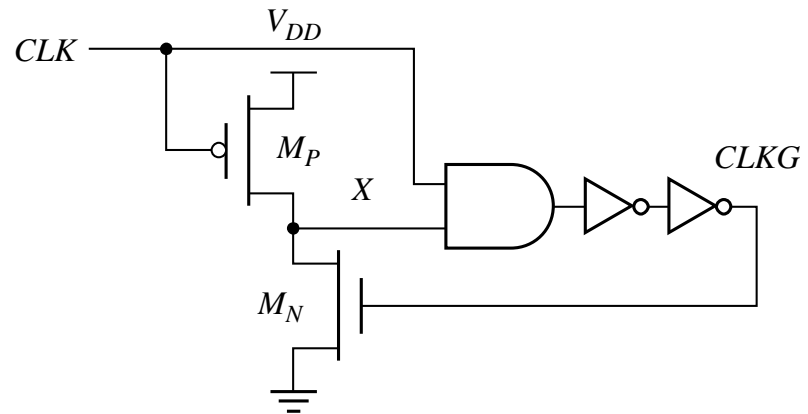


(b) glitch generation

 

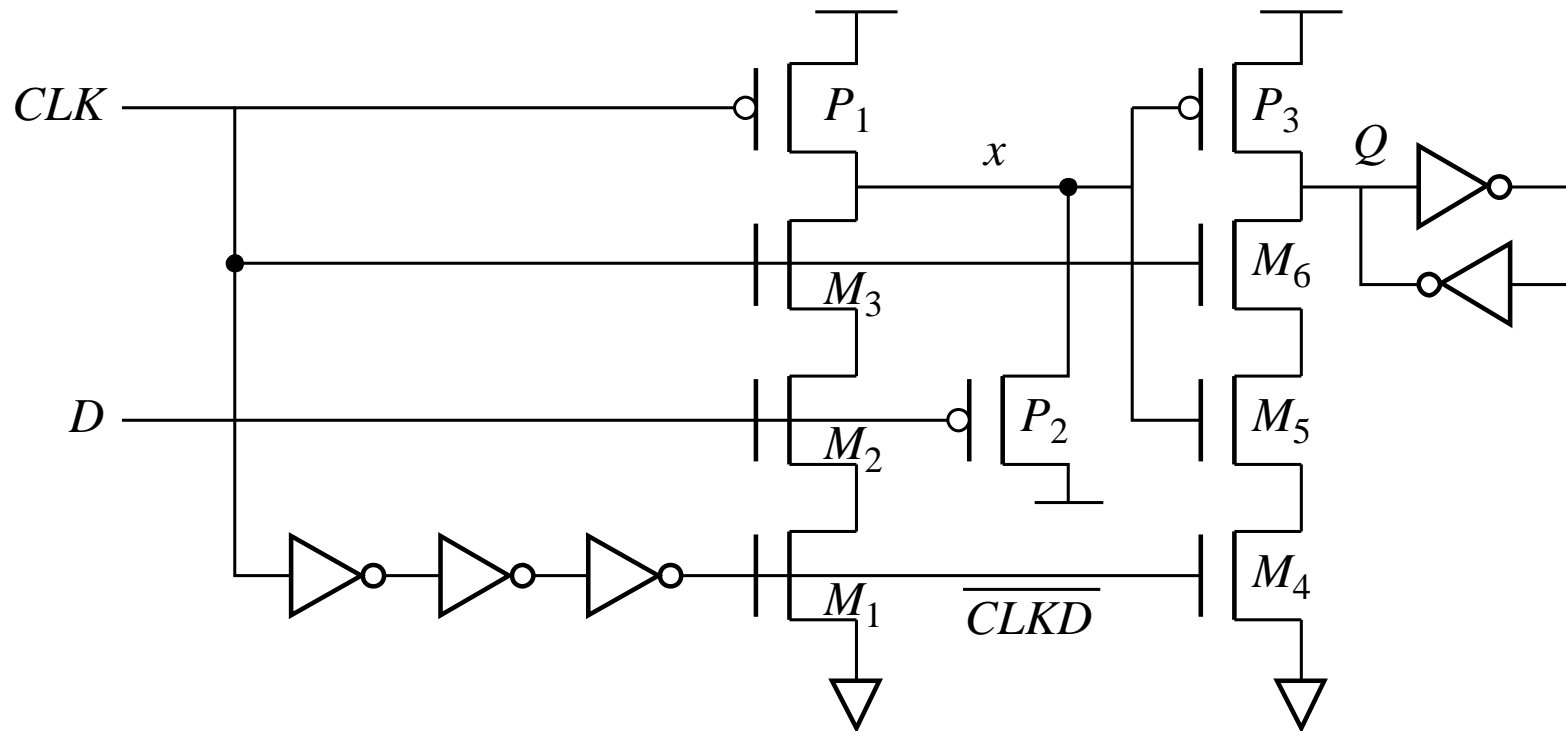
(c) glitch clock

Pulsed Latches



Hybrid Latch – Flip-flop (HLFF), AMD K-6 and K-7 :




Hybrid Latch-FF Timing

 


Latch-Based Pipeline

  

 
Non-Bistable Sequential Circuits— Schmitt Trigger



 
- VTC with hysteresis
- Restores signal slopes



Noise Suppression using Schmitt Trigger

 


CMOS Schmitt Trigger

 


**Moves switching threshold
of the first inverter**

Schmitt Trigger Simulated VTC

 


 Voltage-transfer characteristics with hysteresis.




The effect of varying the ratio of the PMOS device M_4 . The width is $k \cdot 0.5 \mu m$.


CMOS Schmitt Trigger (2)

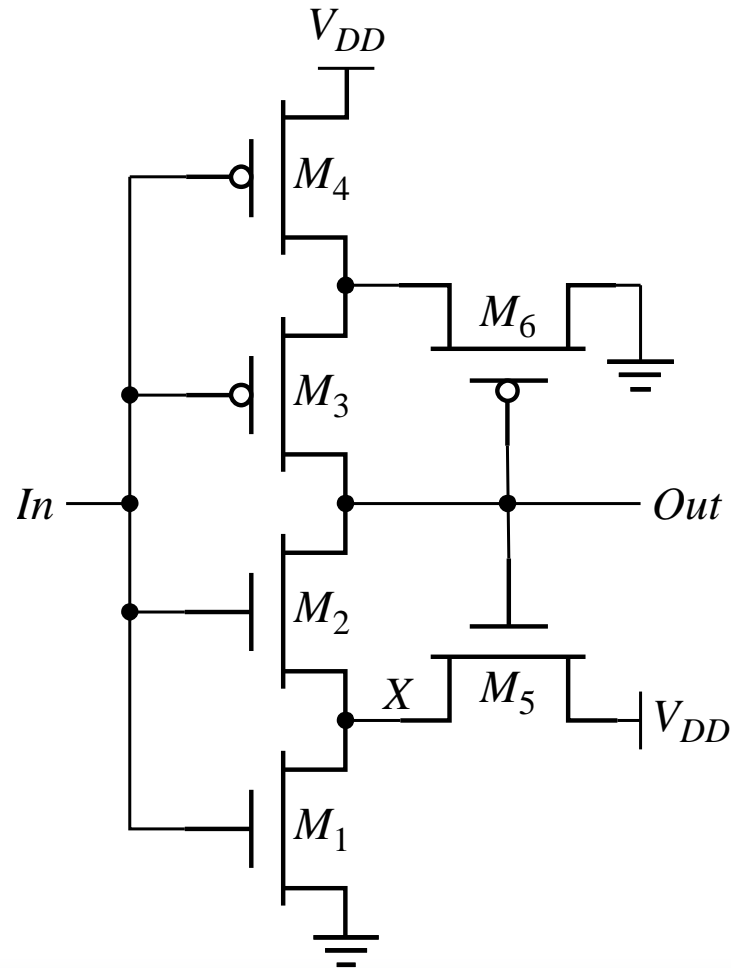


Multivibrator Circuits

 

 Bistable Multivibrator
flip-flop, Schmitt Trigger




Monostable Multivibrator
one-shot

 


Astable Multivibrator
oscillator


Transition-Triggered Monostable

 

Monostable Trigger (RC-based)


 


(a) Trigger circuit.

 


(b) Waveforms.

Astable Multivibrators (Oscillators)

  



simulated response of 5-stage oscillator

Relaxation Oscillator

 


$$T = 2 (\log 3) RC$$

Voltage Controller Oscillator (VCO)

 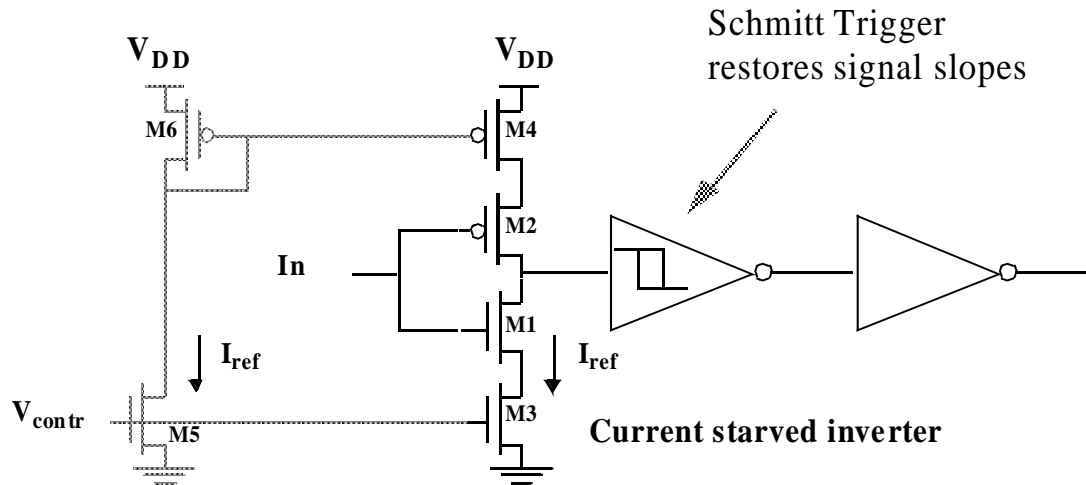


propagation delay as a function of control voltage


Differential Delay Element and VCO

 

delay cell

 

two stage VCO

 

simulated waveforms of 2-stage VCO