



# *Digital Integrated Circuits*


## *A Design Perspective*

Jan M. Rabaey  
Anantha Chandrakasan  
Borivoje Nikolić

# Timing Issues

*January 2003*


# Synchronous Timing

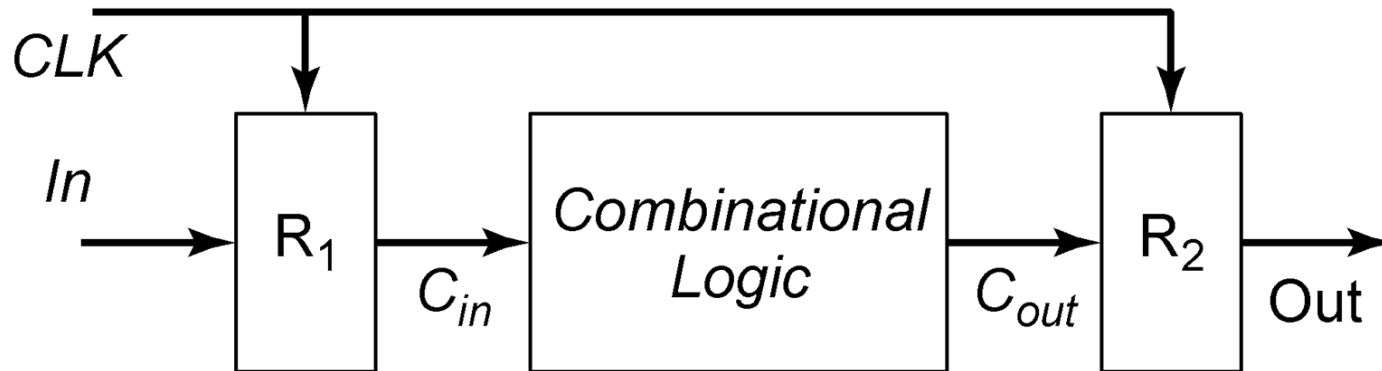




# *Timing Definitions*

# Latch Parameters

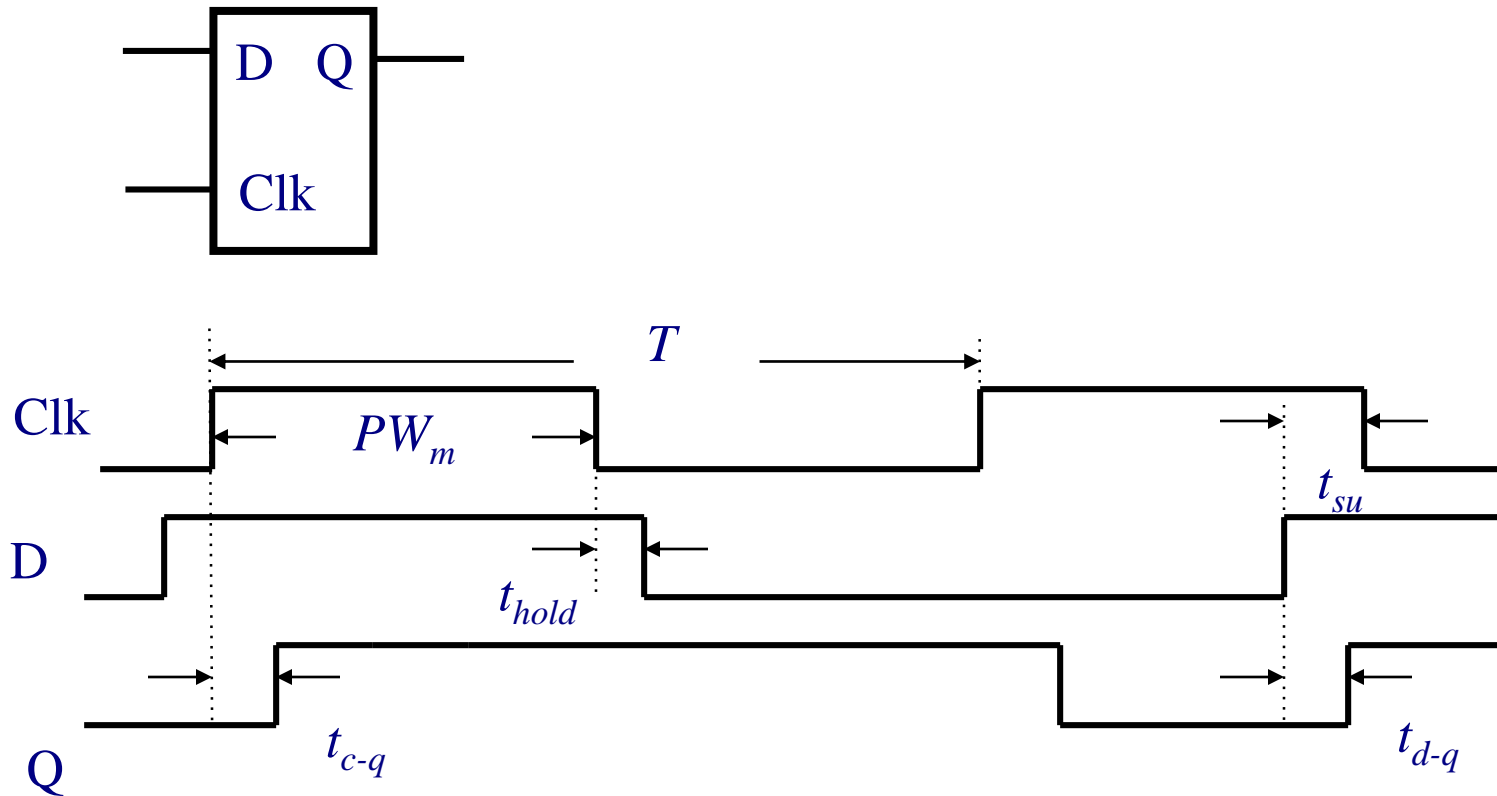


*Delays can be different for rising and falling data transitions*

# Register Parameters

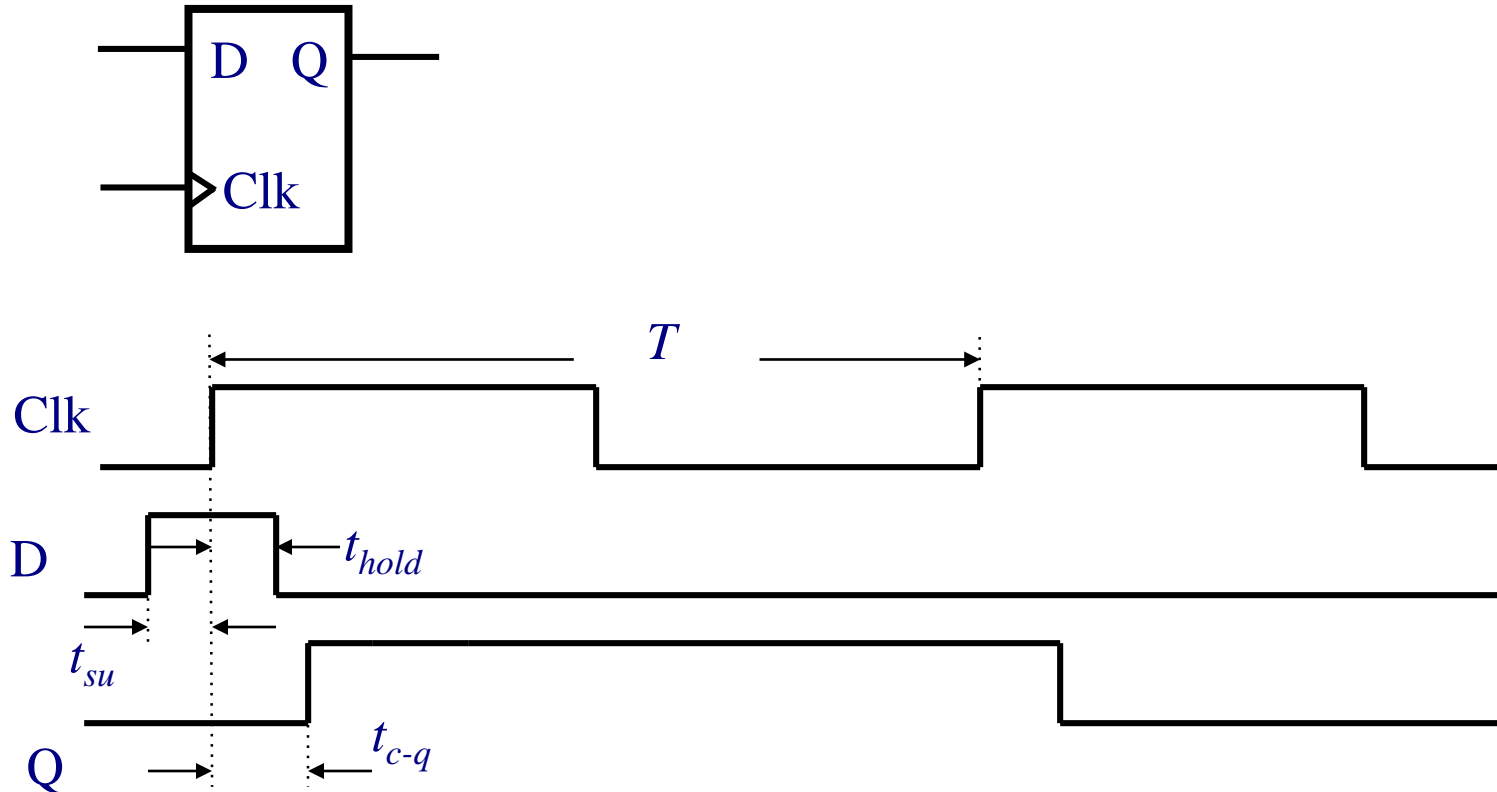

*Delays can be different for rising and falling data transitions*

# Clock Uncertainties

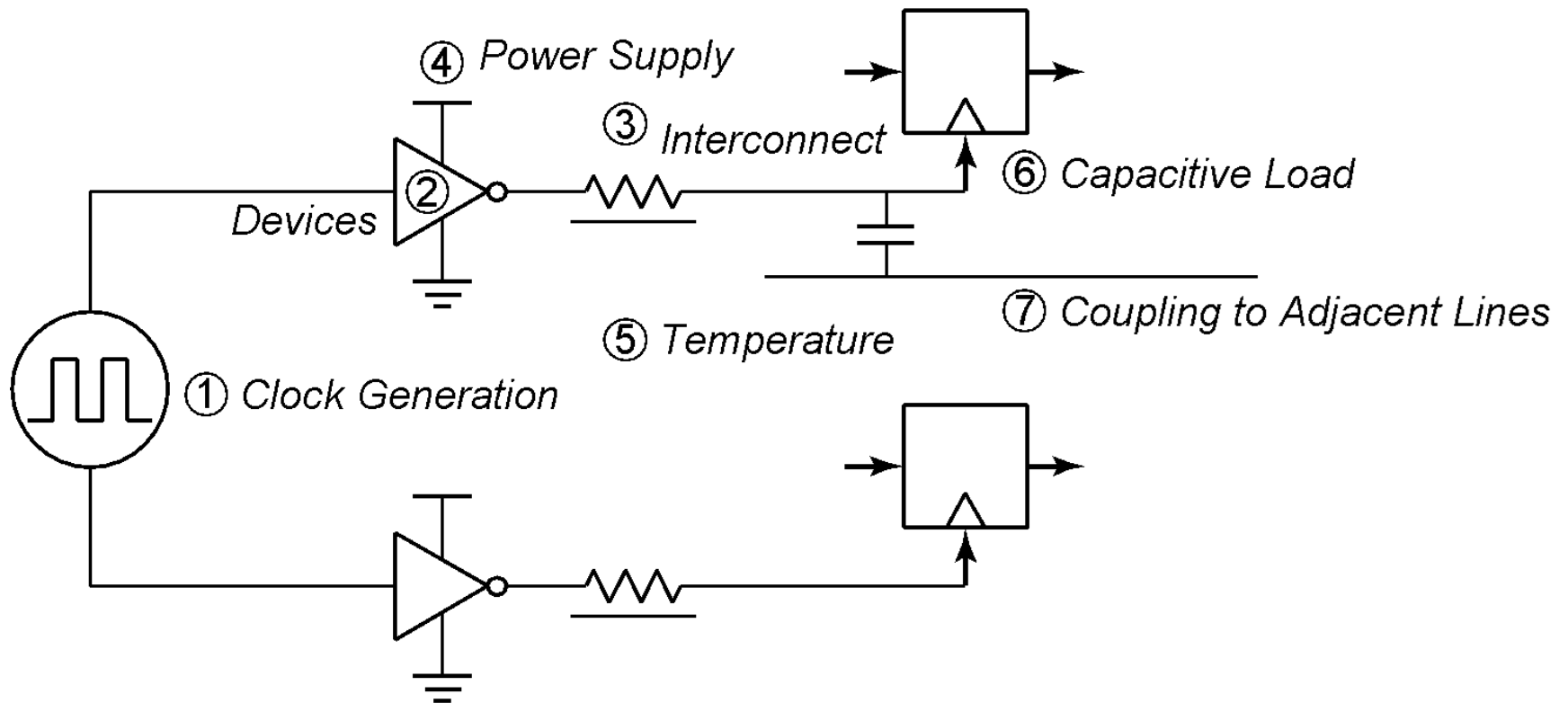

*Sources of clock uncertainty*

# Clock Nonidealities

## ❑ Clock skew

- Spatial variation in temporally equivalent clock edges; deterministic + random,  $t_{SK}$


## ❑ Clock jitter

- Temporal variations in consecutive edges of the clock signal; modulation + random noise
- Cycle-to-cycle (short-term)  $t_{JS}$
- Long term  $t_{JL}$

## ❑ Variation of the pulse width

- Important for level sensitive clocking


# Clock Skew and Jitter

 


- ❑ Both skew and jitter affect the effective cycle time
- ❑ Only skew affects the race margin




# Clock Skew

 

# Positive and Negative Skew

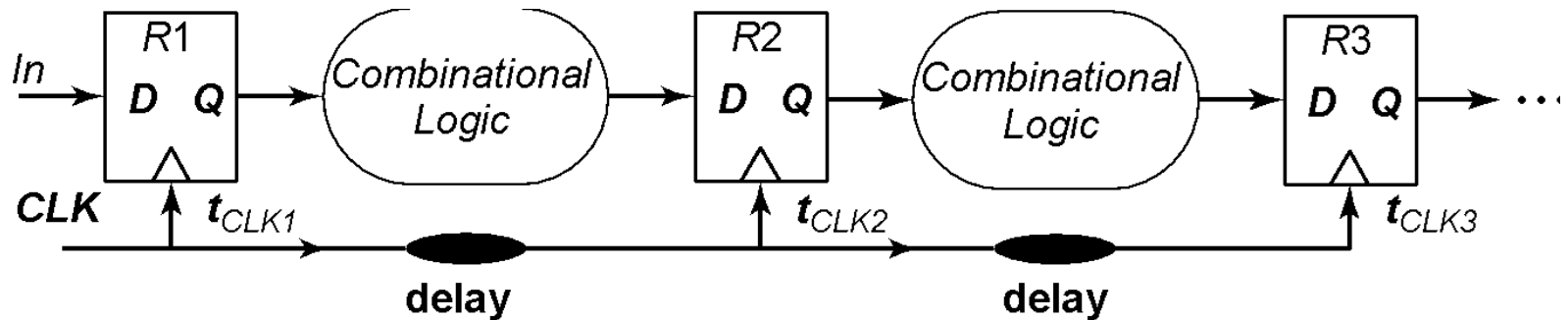


(a) Positive skew

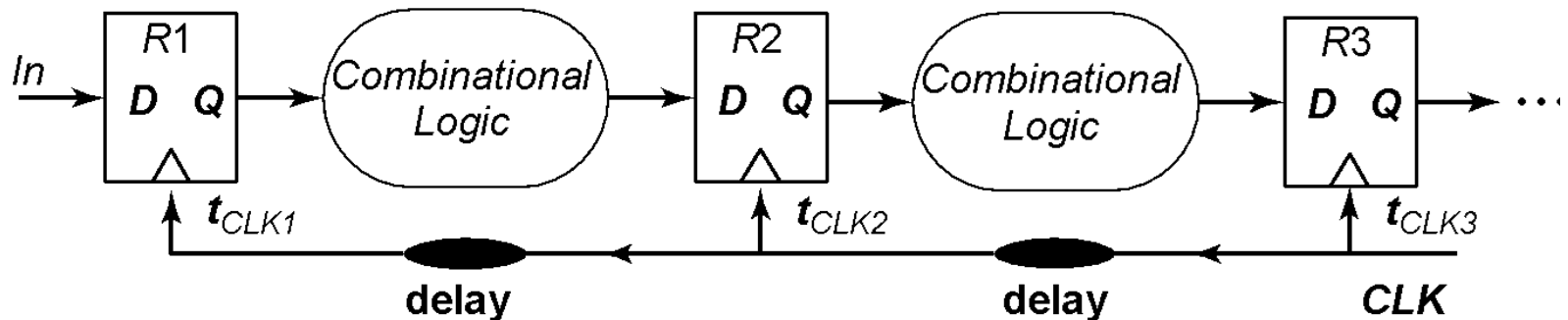


(b) Negative skew

# Positive Skew

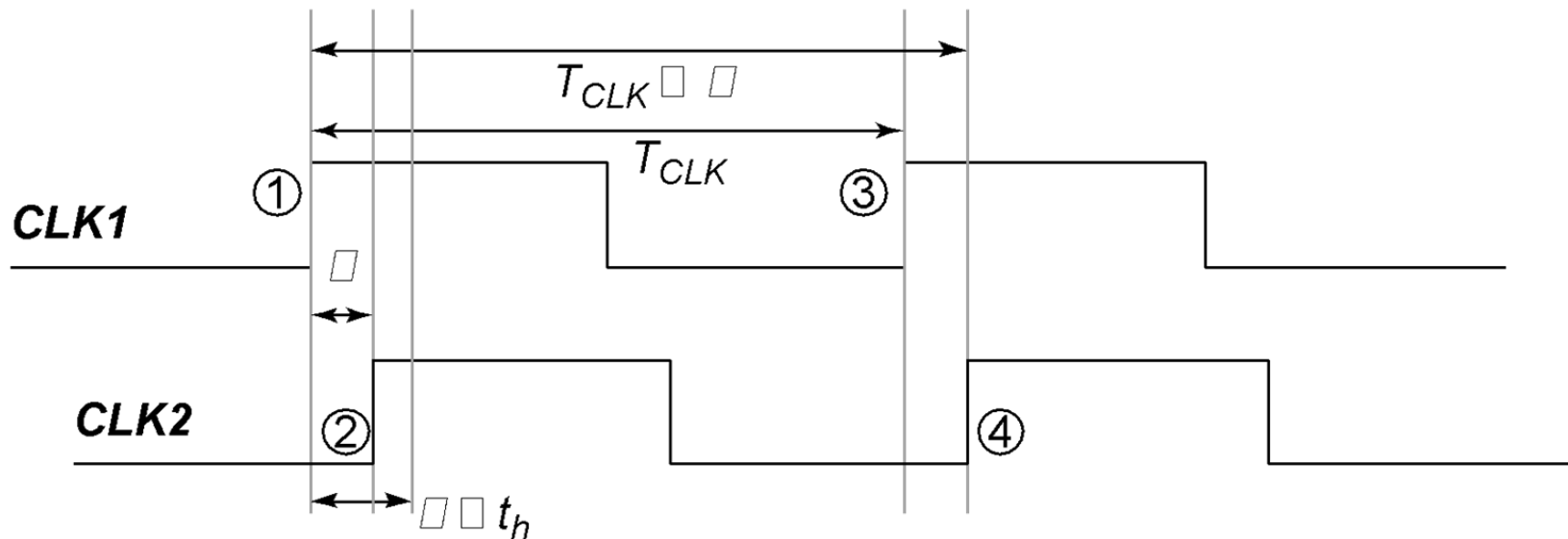


*Launching edge arrives before the receiving edge*

# Negative Skew

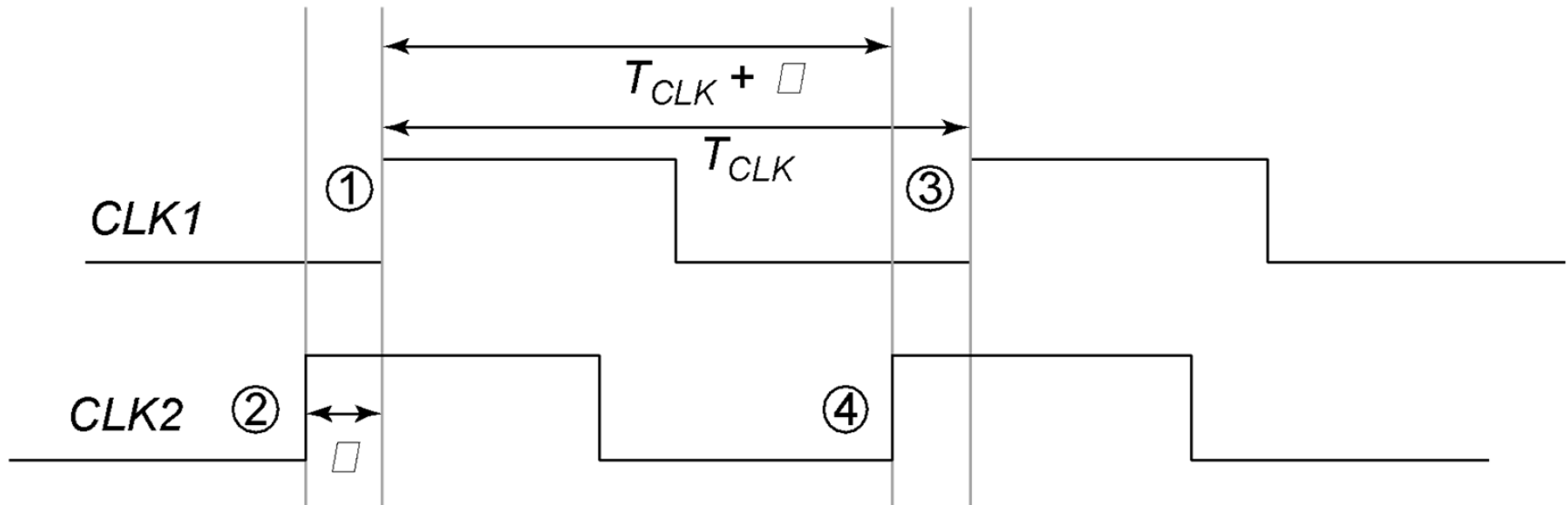

*Receiving edge arrives before the launching edge*

# Timing Constraints

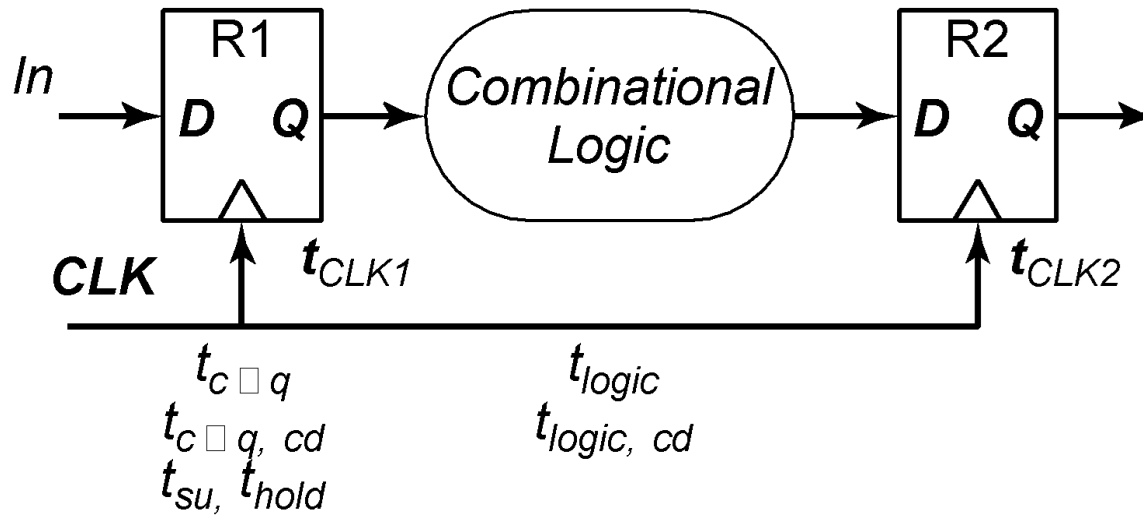


*Minimum cycle time:*

$$T - \delta = t_{c \rightarrow q} + t_{su} +$$

$t_{logic}$

*Worst case is when receiving edge arrives early (positive  $\delta$ )*

# Timing Constraints

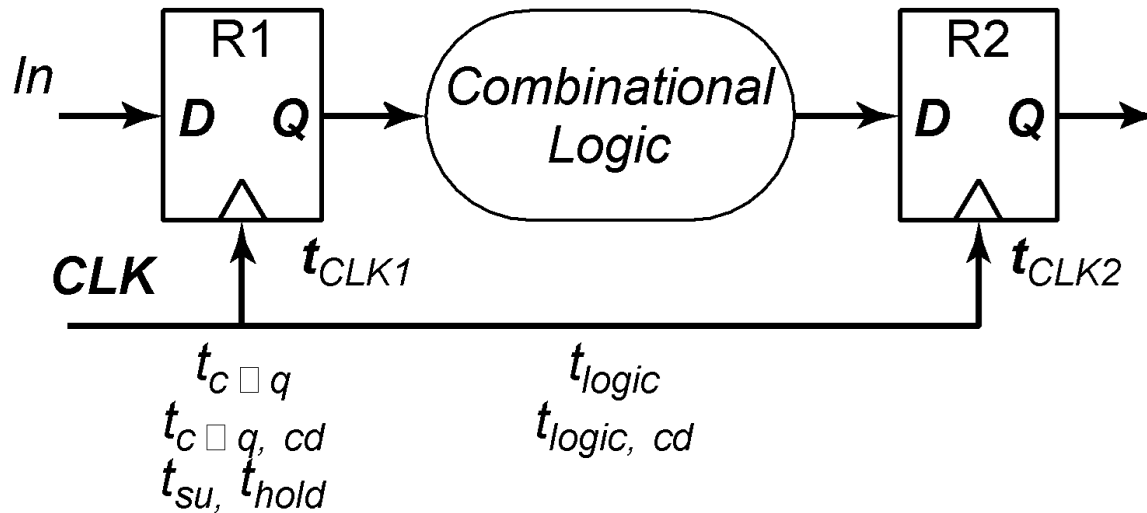


*Hold time constraint:*


$$t_{(c-q, cd)} + t_{(logic, cd)} > t_{hold} + \delta$$

*Worst case is when receiving edge arrives late  
Race between data and clock*

# Impact of Jitter

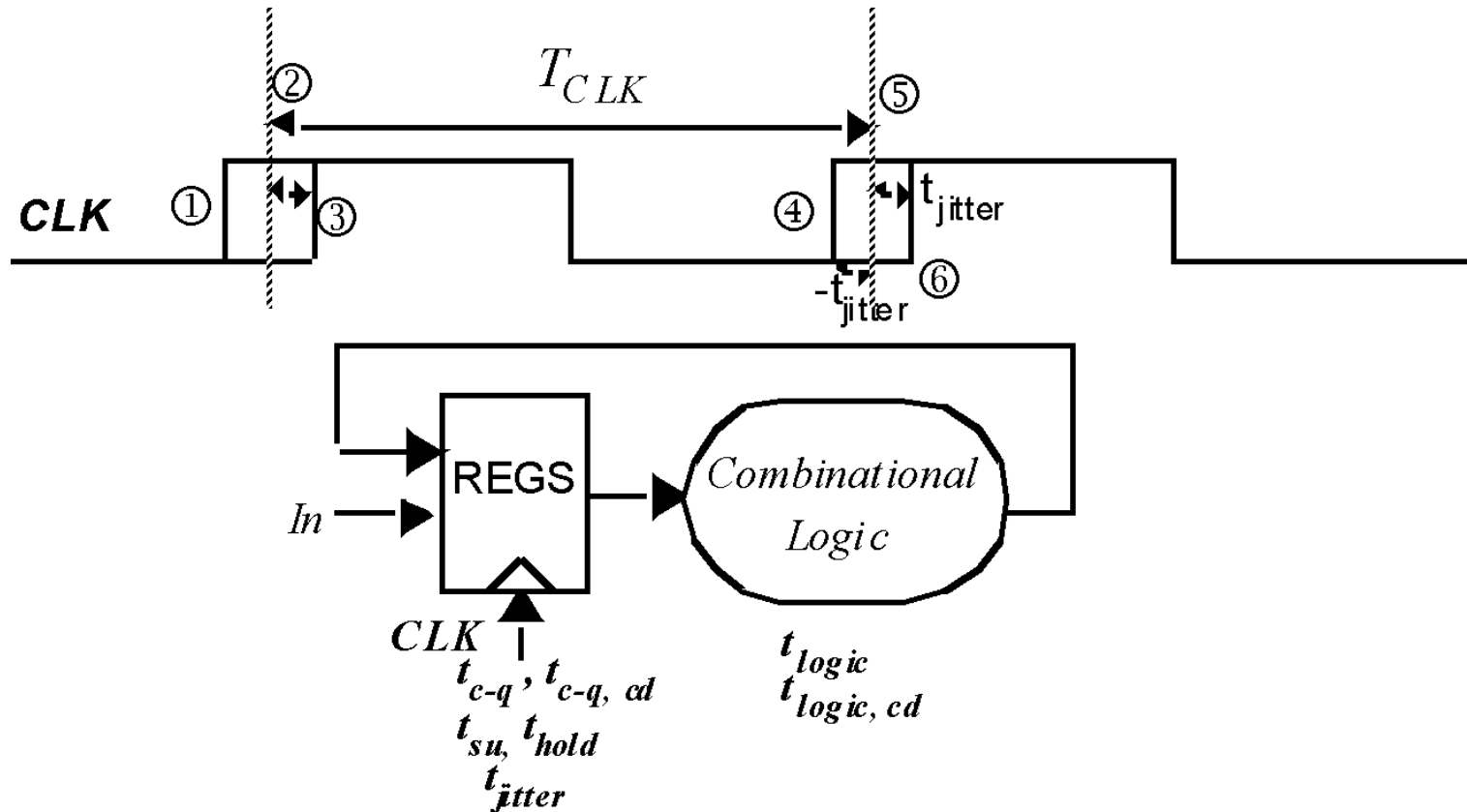
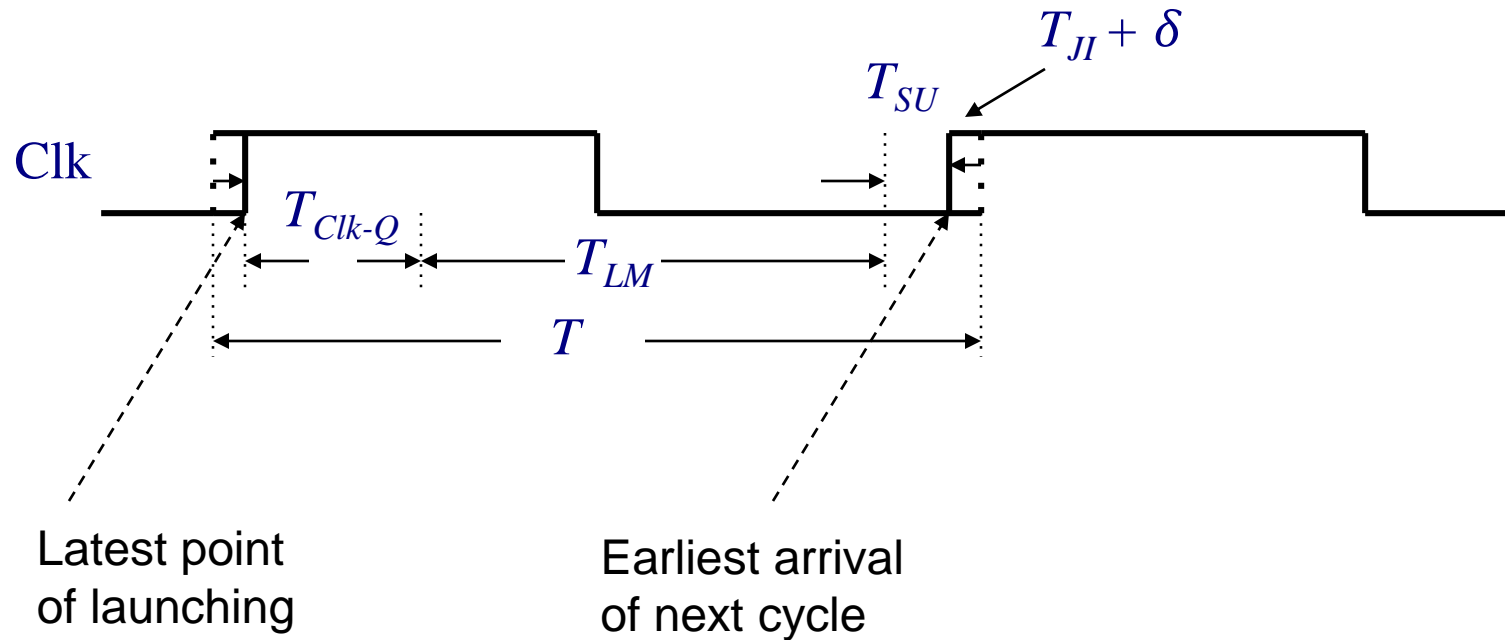
# Longest Logic Path in Edge-Triggered Systems





# Clock Constraints in Edge-Triggered Systems

If launching edge is late and receiving edge is early, the data will not be too late if:


$$T_{c-q} + T_{LM} + T_{SU} < T - T_{JI,1} - T_{JI,2} - \delta$$

Minimum cycle time is determined by the maximum delays through the logic

$$T_{c-q} + T_{LM} + T_{SU} + \delta + 2 T_{JI} < T$$

**Skew can be either positive or negative**

# Shortest Path

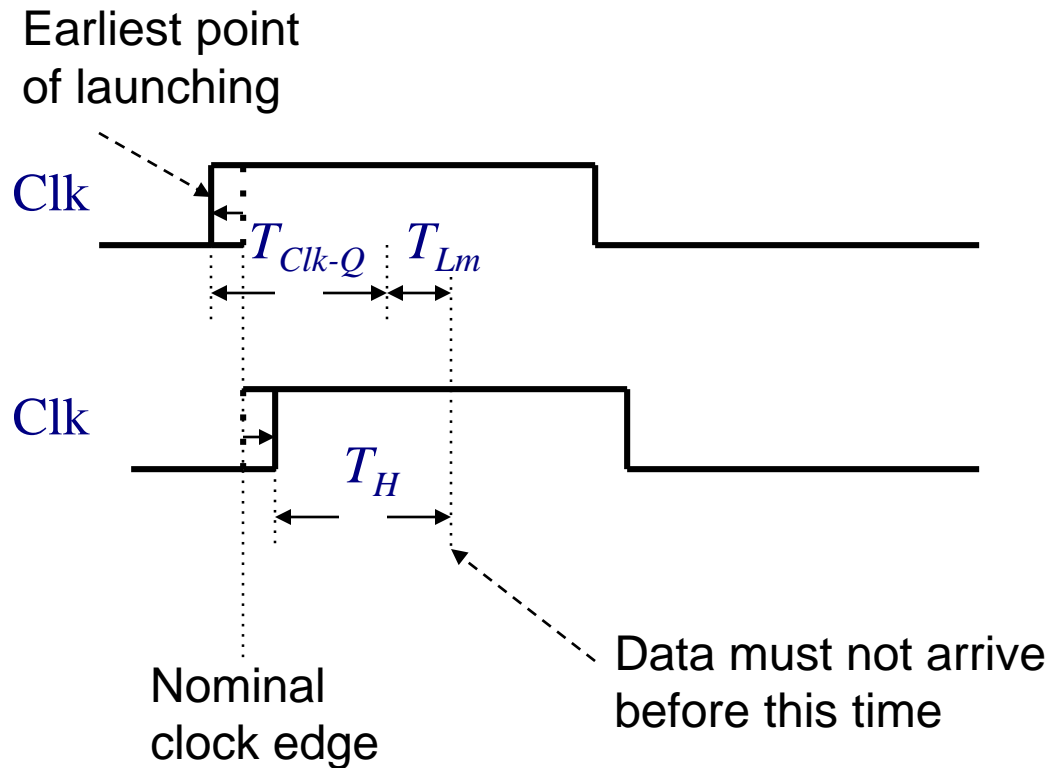

# *Clock Constraints in Edge-Triggered Systems*


**If launching edge is early and receiving edge is late:**

$$T_{c-q} + T_{LM} - T_{JI,1} < T_H + T_{JI,2} + \delta$$

**Minimum logic delay**



$$T_{c-q} + T_{LM} < T_H + 2T_{JI} + \delta$$

## How to counter Clock Skew?

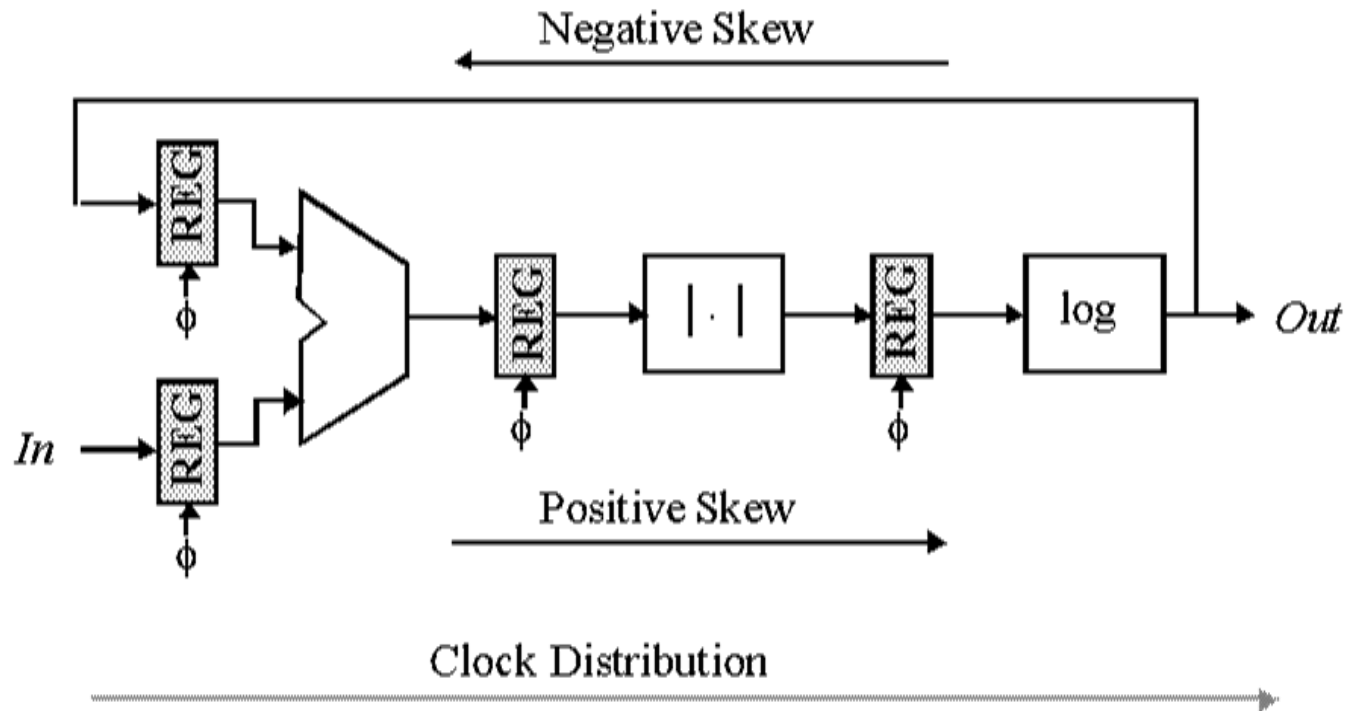


## Data and Clock Routing

# Flip-Flop – Based Timing

  


Representation after  
M. Horowitz, VLSI Circuits 1996.

# Flip-Flops and Dynamic Logic

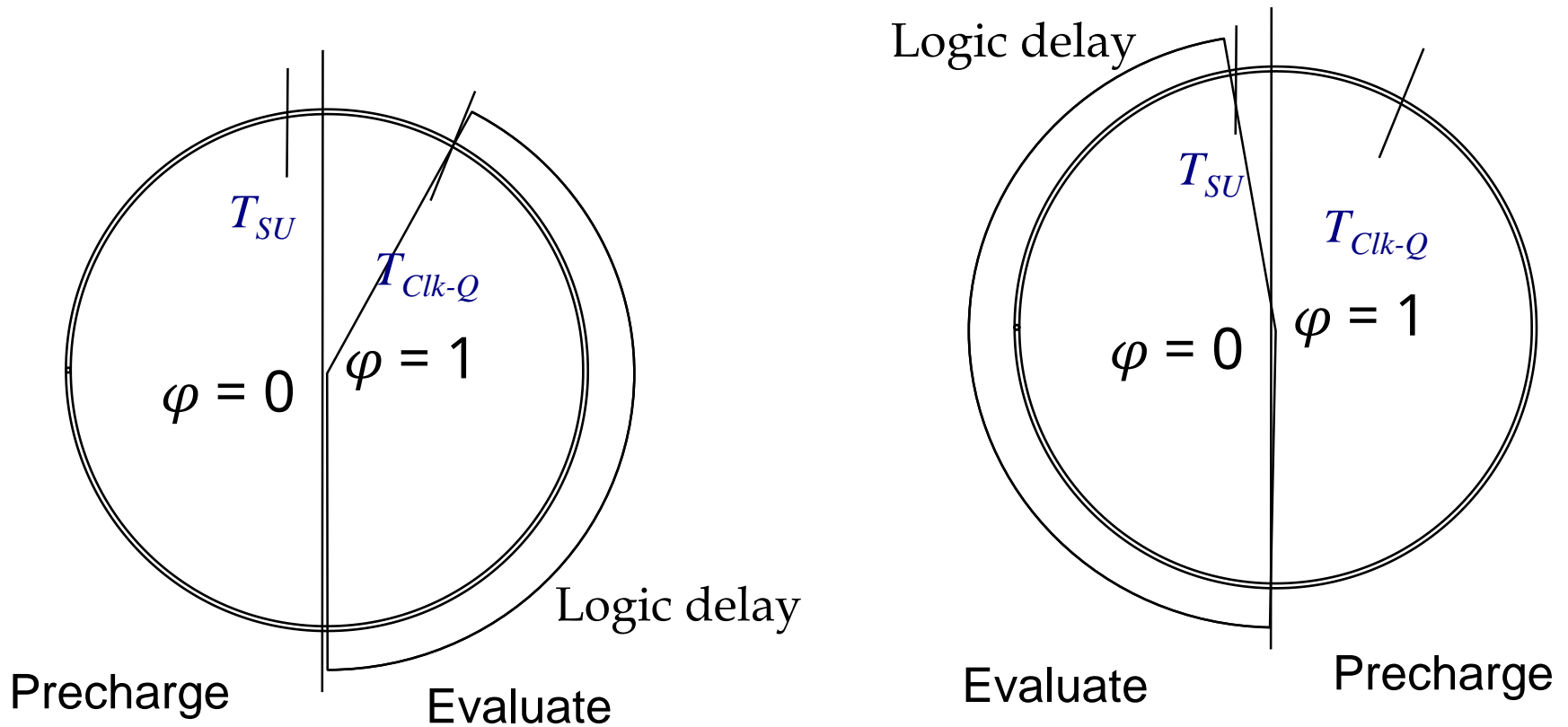

Flip-flops are used only with static logic

# Latch timing

 



When data arrives  
to transparent latch

Latch is a 'soft' barrier

When data arrives  
to closed latch

Data has to be 're-launched'

# Single-Phase Clock with Latches

  




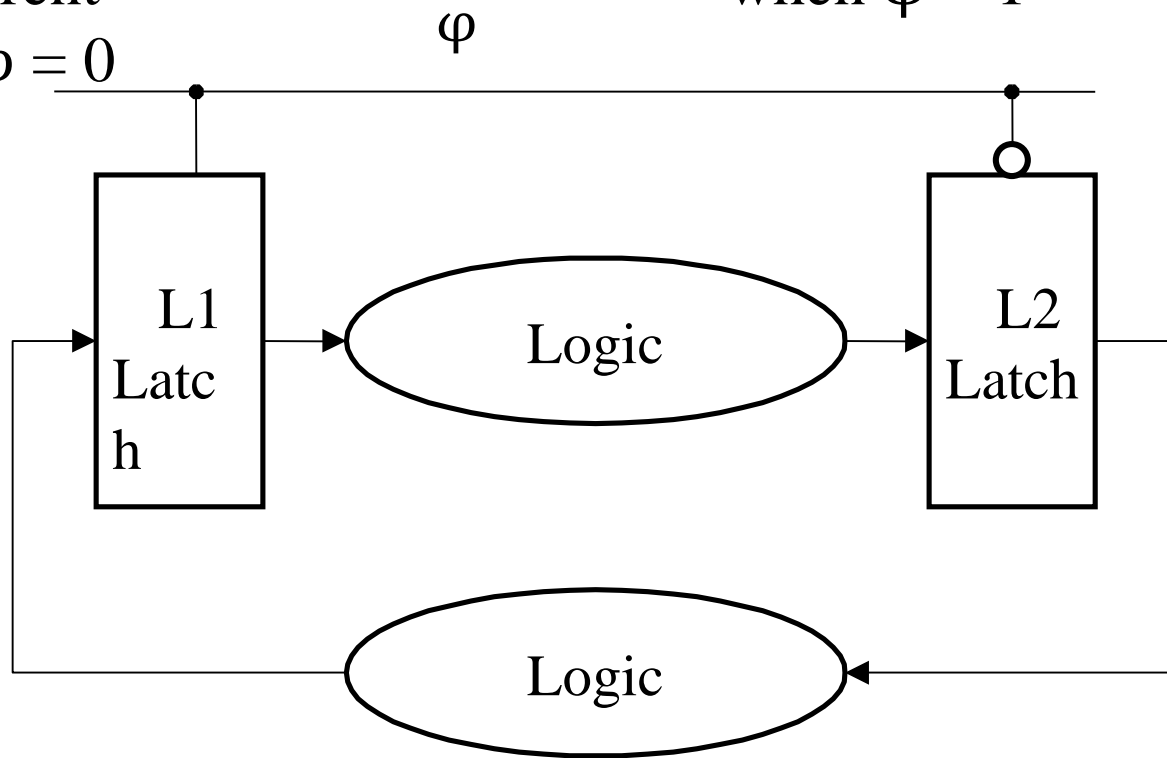
# Latch-Based Design

L1 latch is transparent when  $\varphi = 0$


L2 latch is transparent when  $\varphi = 1$




# Slack-borrowing

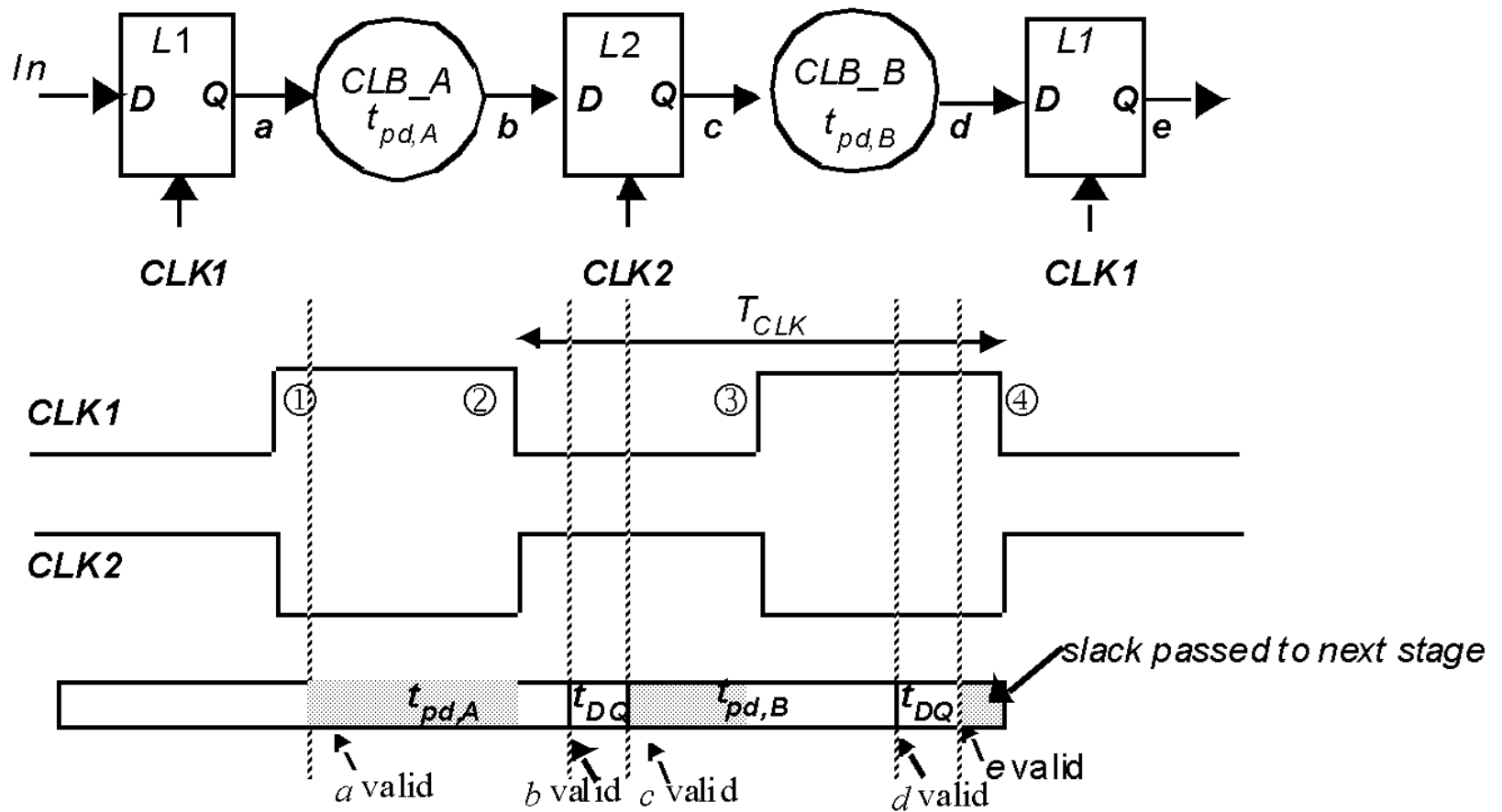

# Latch-Based Timing

 


**Can tolerate skew!**

 


# Clock Distribution

## H-tree

 


## Clock is distributed in a tree-like fashion

# More realistic H-tree

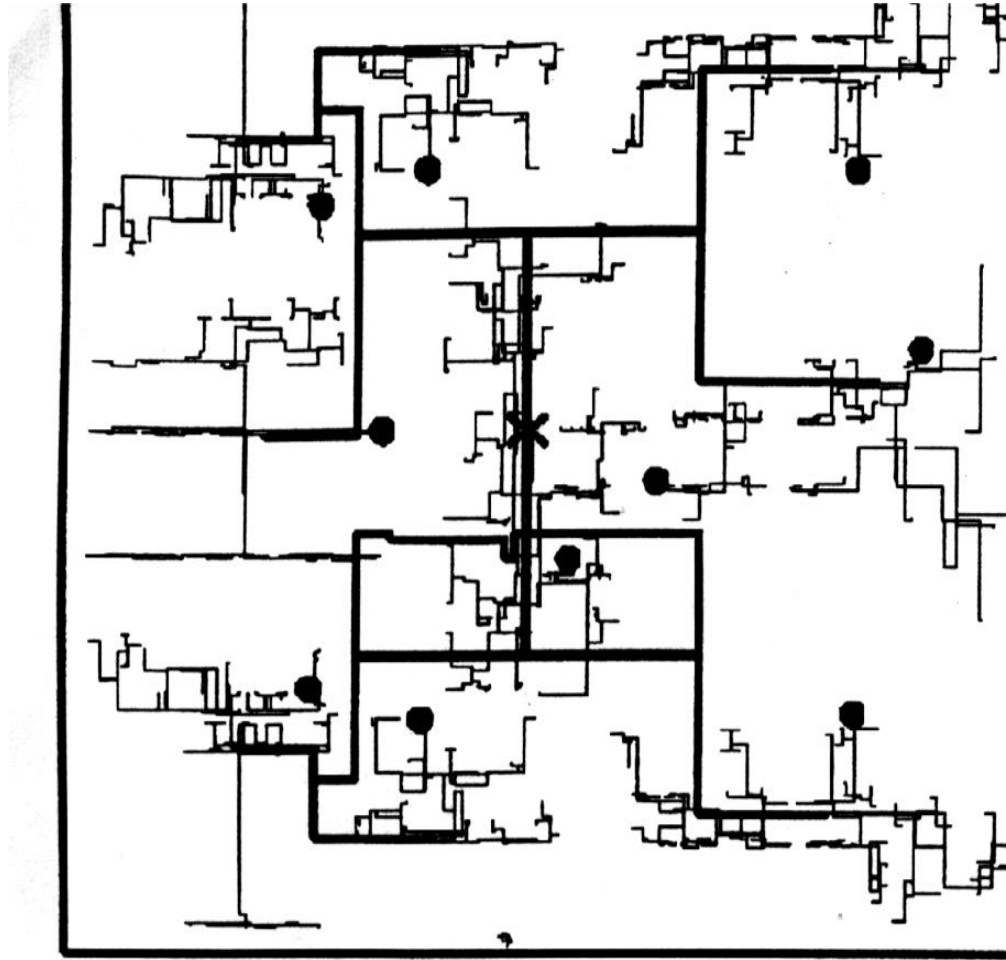

*[Restle98]*

# The Grid System

 

- *No rc-matching*
- *Large power*

# ***Example: DEC Alpha 21164***

**Clock Frequency: 300 MHz - 9.3 Million Transistors**

**Total Clock Load: 3.75 nF**


**Power in Clock Distribution network : 20 W (out of 50)**

**Uses Two Level Clock Distribution:**


- **Single 6-stage driver at center of chip**
- **Secondary buffers drive left and right side clock grid in Metal3 and Metal4**

**Total driver size: 58 cm!**

# 21164 Clocking

 


**Clock waveform**

 

 **Location of clock driver on die**

- ❑ 2 phase single wire clock, distributed globally
- ❑ 2 distributed driver channels
  - Reduced RC delay/skew
  - Improved thermal distribution
  - 3.75nF clock load
  - 58 cm final driver width
- ❑ Local inverters for latching
- ❑ Conditional clocks in caches to reduce power
- ❑ More complex race checking
- ❑ Device variation






Clock Drivers





# *Clock Skew in Alpha Processor*

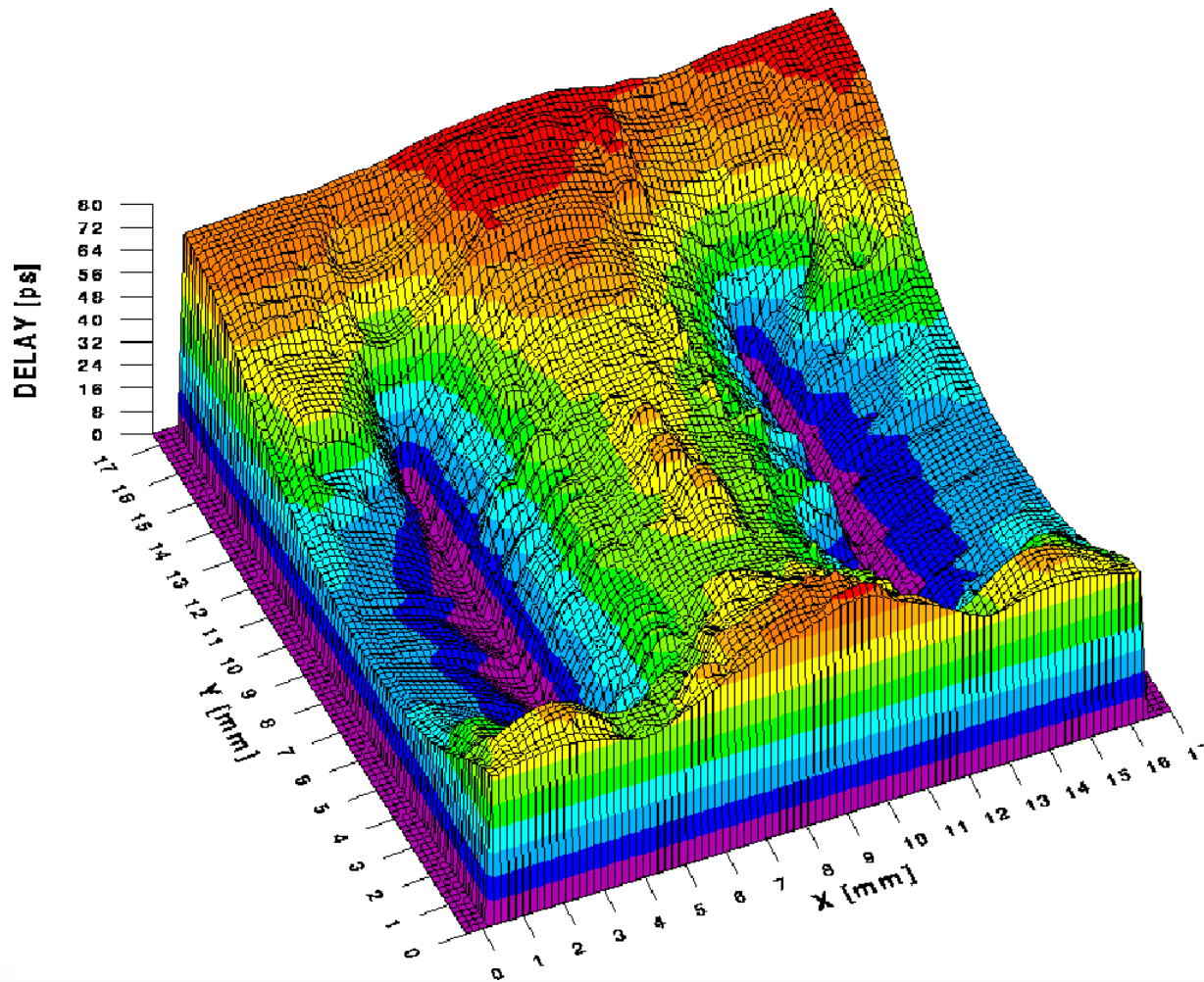


# EV6 (Alpha 21264) Clocking

## 600 MHz – 0.35 micron CMOS

  


- ❑ 2 Phase, with multiple conditional buffered clocks
  - 2.8 nF clock load
  - 40 cm final driver width
- ❑ Local clocks can be gated “off” to save power
- ❑ Reduced load/skew
- ❑ Reduced thermal issues
- ❑ Multiple clocks complicate race checking

# 21264 Clocking

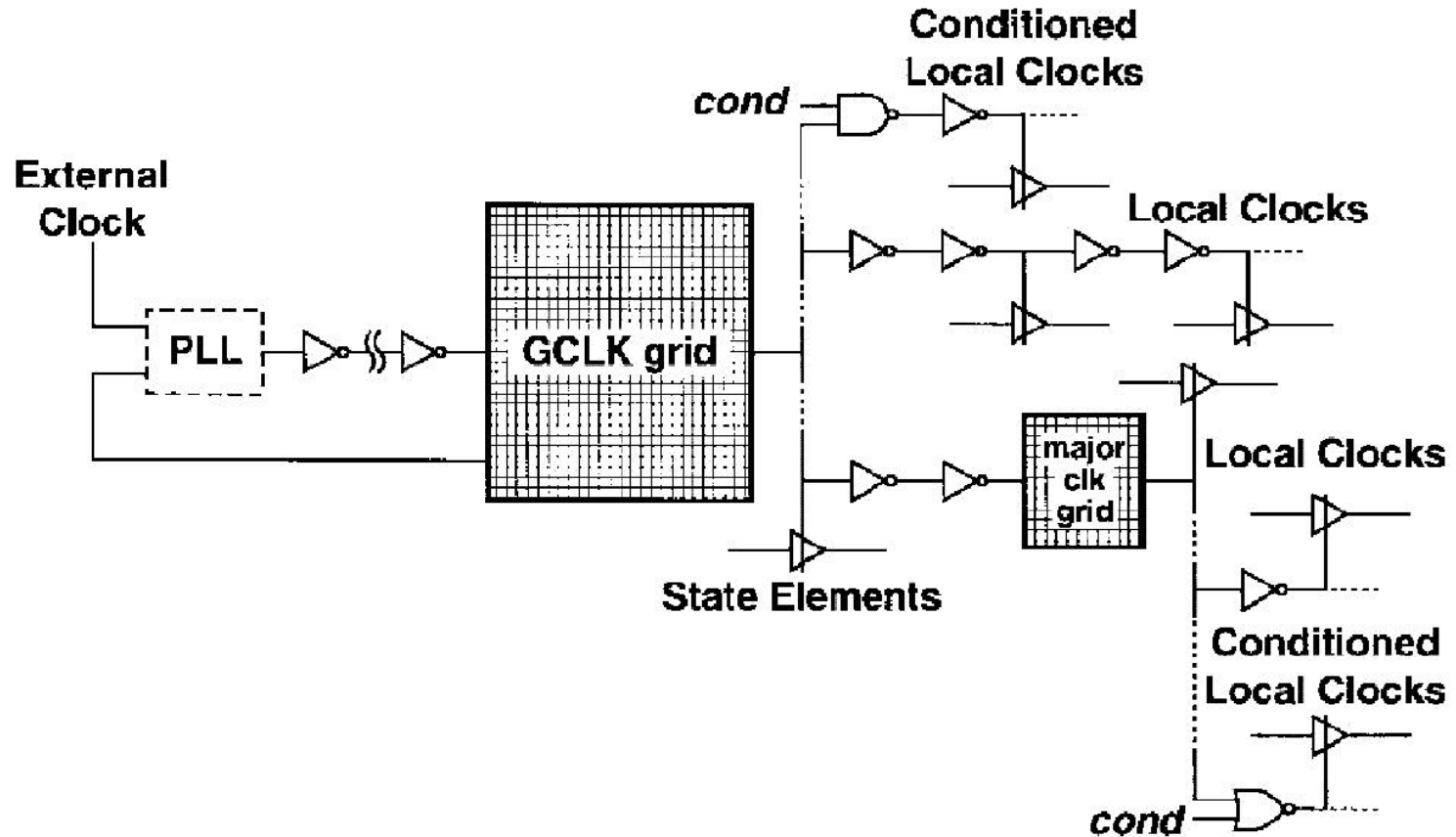


# EV6 Clock Results

 

50

**GCLK Skew**  
(at Vdd/2 Crossings)

 


345

**GCLK Rise Times**  
(20% to 80% Extrapolated to 0% to 100%)

# EV7 Clock Hierarchy
 
## Active Skew Management and Multiple Clock Domains



- + widely dispersed drivers
- + DLLs compensate static and low-frequency variation
- + divides design and verification effort
- DLL design and verification is added work
- + tailored clocks

# *Self-timed and Asynchronous Design*

## **Functions of clock in synchronous design**

- 1) Acts as completion signal**
- 2) Ensures the correct ordering of events**


## **Truly asynchronous design**

- 1) Completion is ensured by careful timing analysis**
- 2) Ordering of events is implicit in logic**

## **Self-timed design**


- 1) Completion ensured by completion signal**
- 2) Ordering imposed by handshaking protocol**

# Synchronous Pipelined Datapath

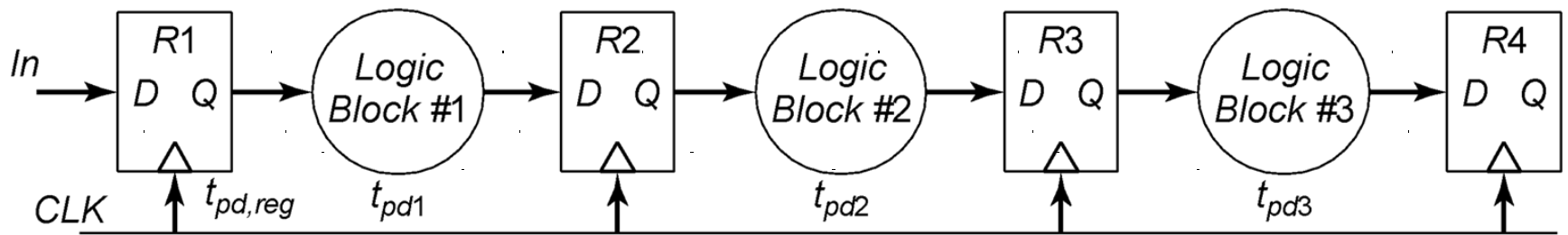




# Self-Timed Pipelined Datapath

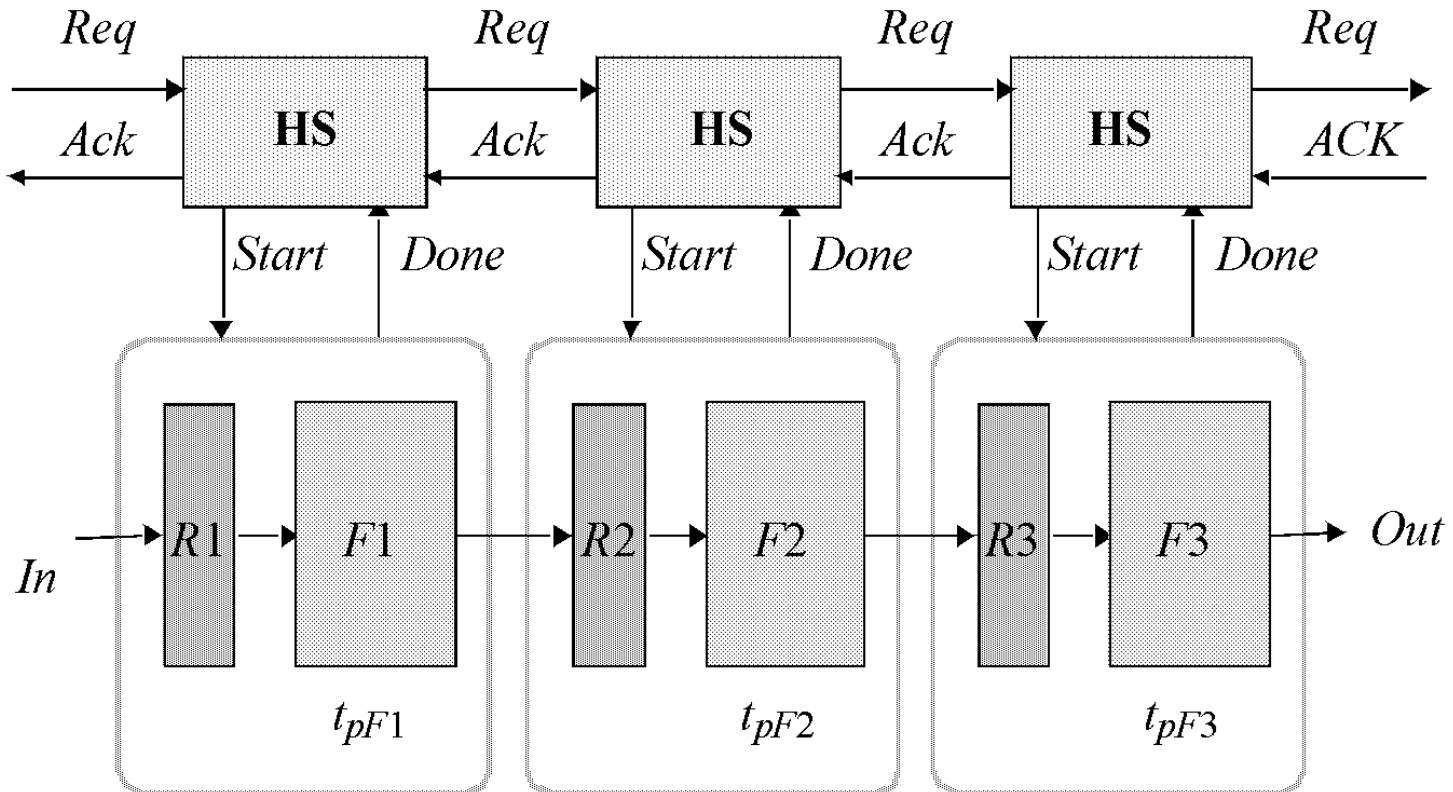

# Completion Signal Generation

 


Using Delay Element (e.g. in memories)

# Completion Signal Generation


B	B0	B1
in transition (or reset)	0	0
0	0	1
1	1	0
illegal	1	1

**Using Redundant Signal Encoding**


# Completion Signal in DCVSL

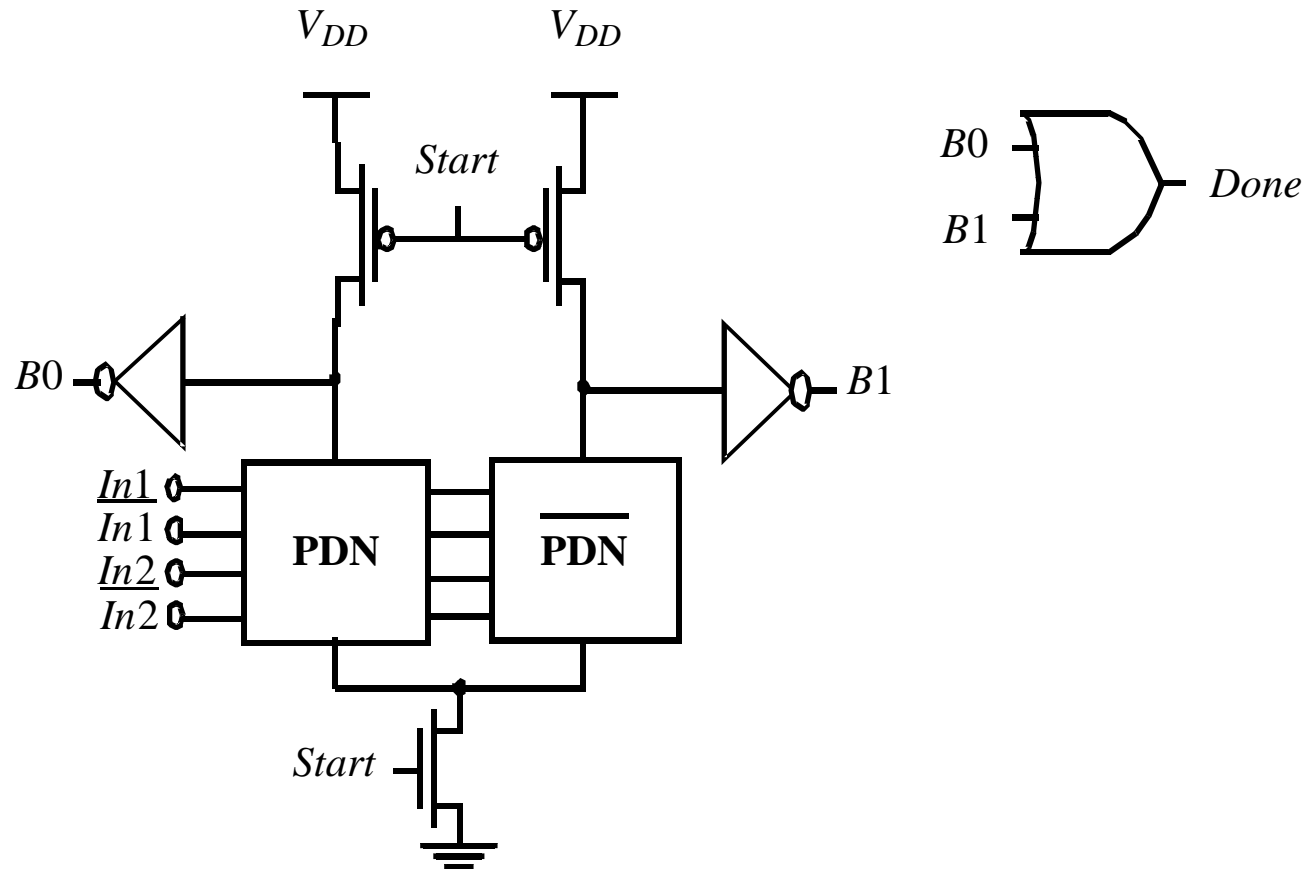

# Self-Timed Adder


 


(a) Differential carry generation

 


(b) Completion signal

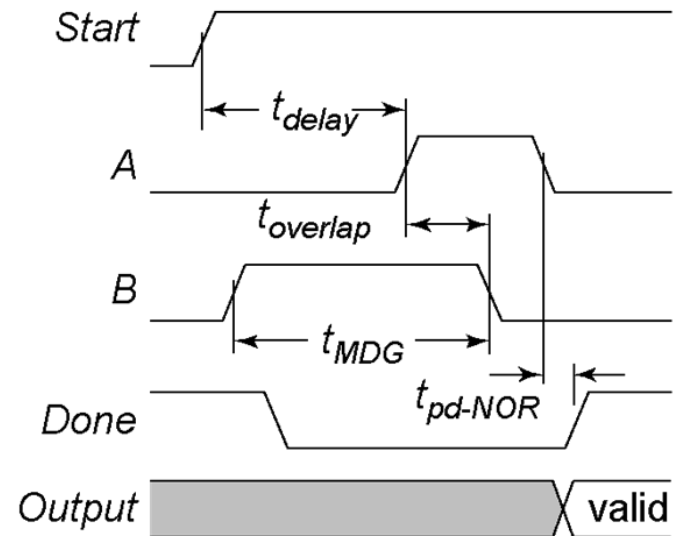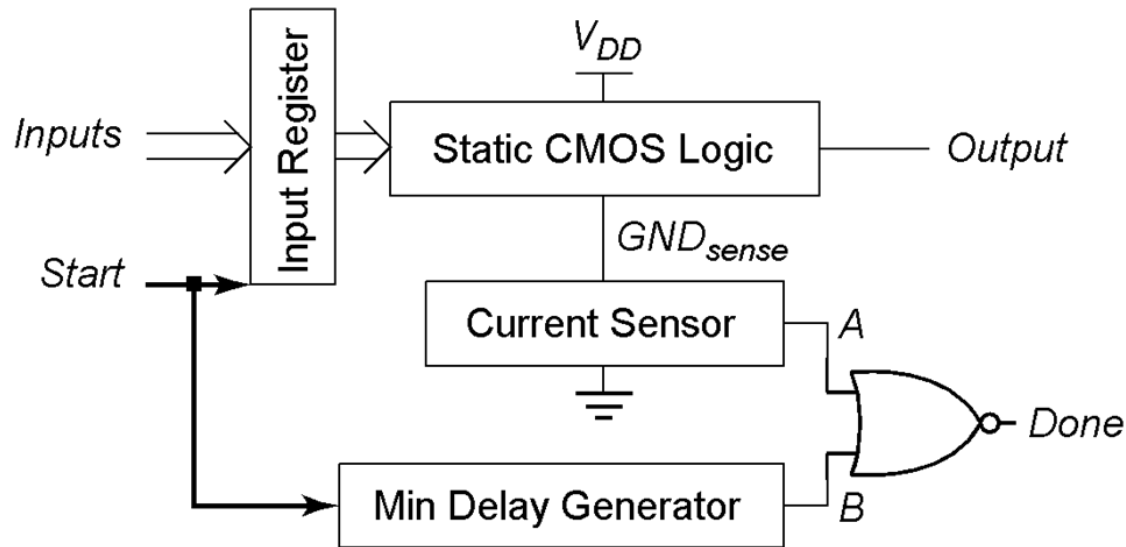
# Completion Signal Using Current Sensing



# Hand-Shaking Protocol

 


(a) Sender-receiver configuration

 

(b) Timing diagram

## Two Phase Handshake


# Event Logic – The Muller-C Element

 


(a) Schematic

$A$	$B$	$F_{n+1}$
0	0	0
0	1	$F_n$
1	0	$F_n$
1	1	1


(b) Truth table

 

(a) Logic

 


(b) Majority Function

 

(c) Dynamic




# 2-Phase Handshake Protocol

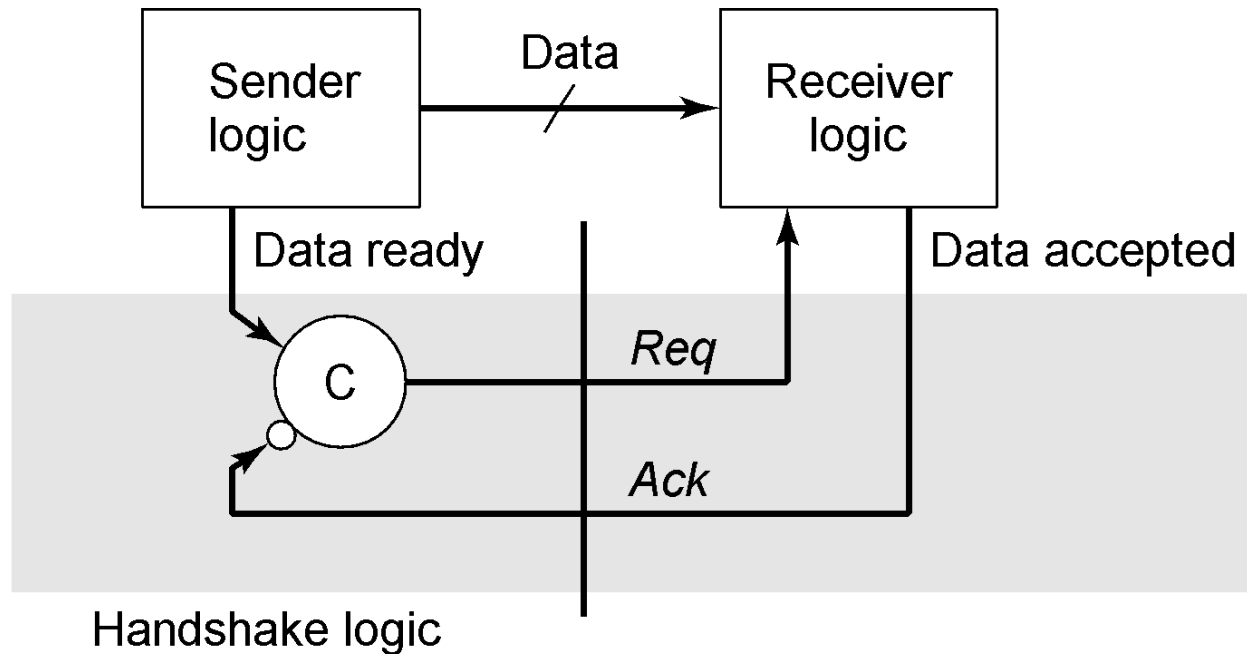

Advantage : FAST - minimal # of signaling events (important for global interconnect)

Disadvantage : edge - sensitive, has state


# Example: Self-timed FIFO

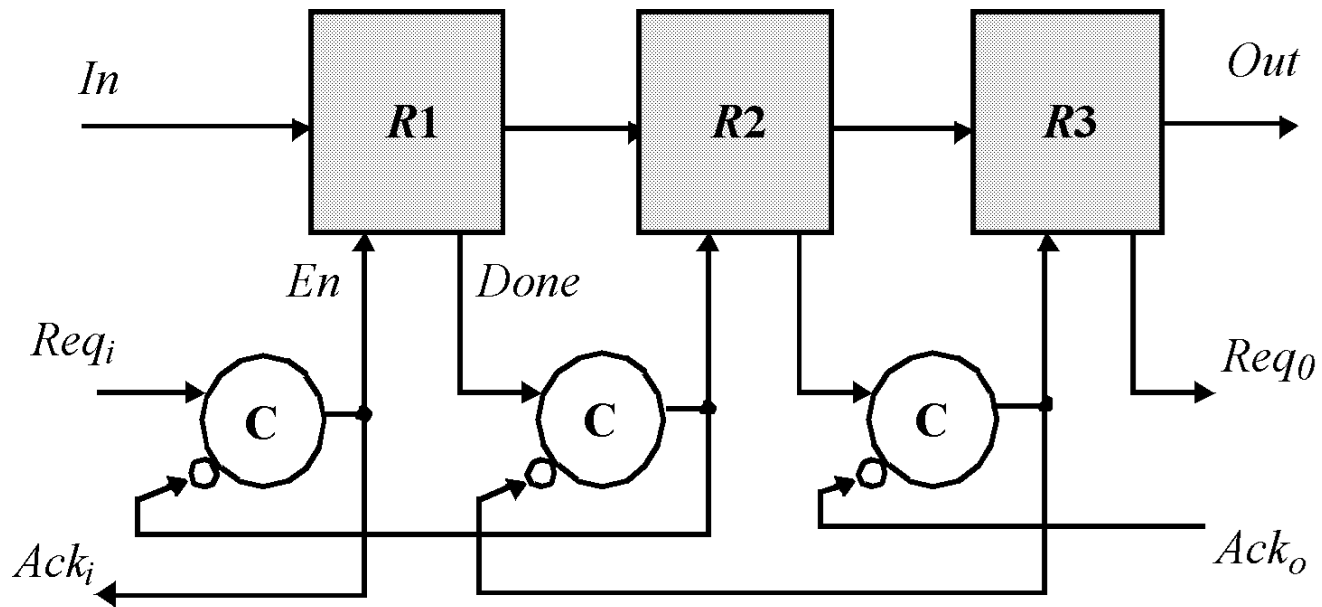


All 1s or 0s -> pipeline empty

Alternating 1s and 0s -> pipeline full

## 2-Phase Protocol

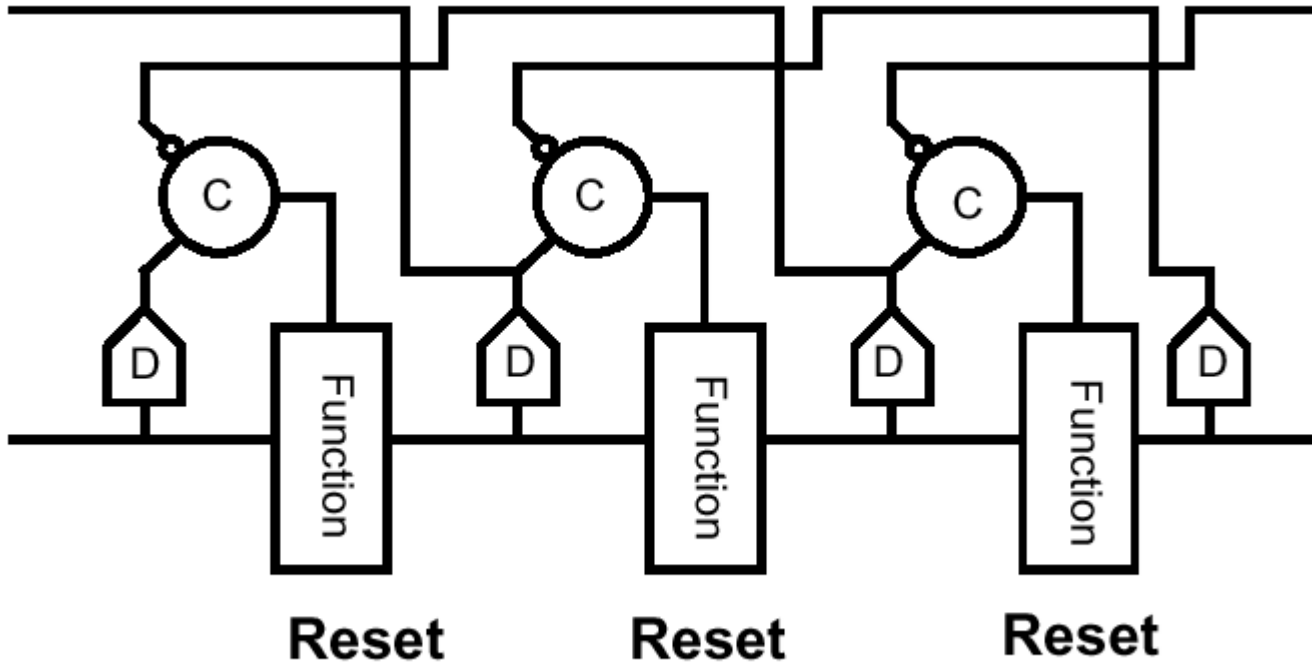


# Example

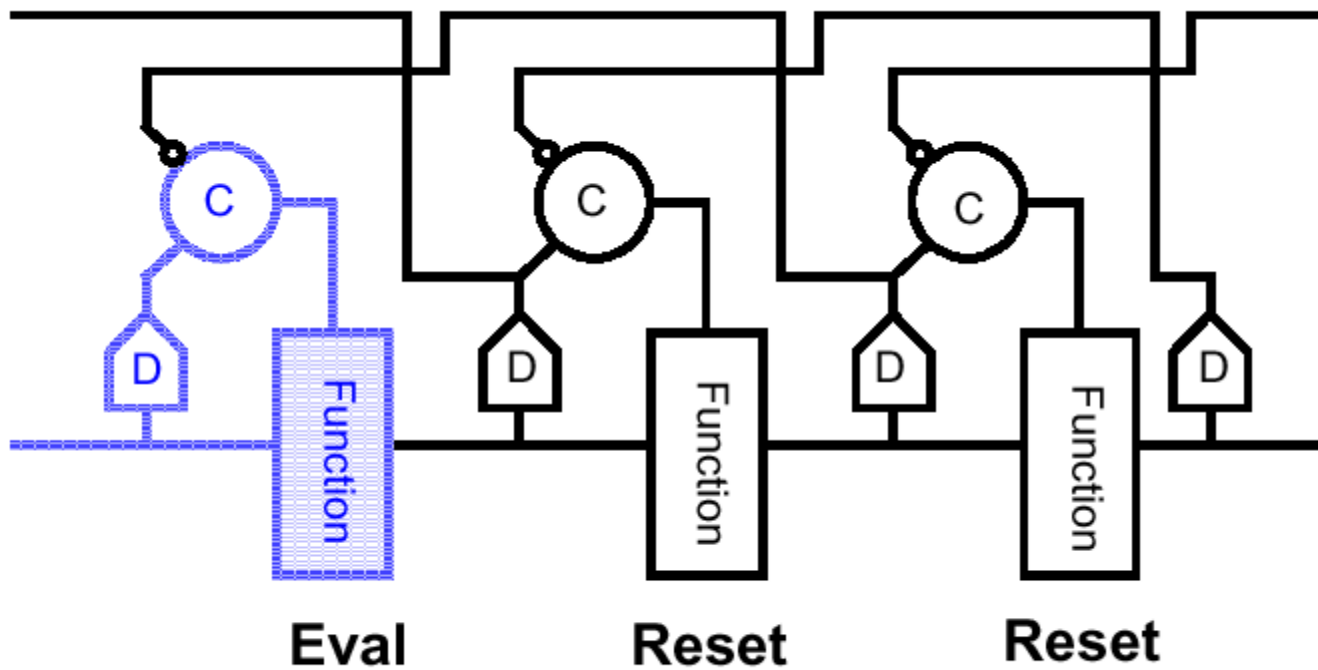


From [Horowitz]


# Example

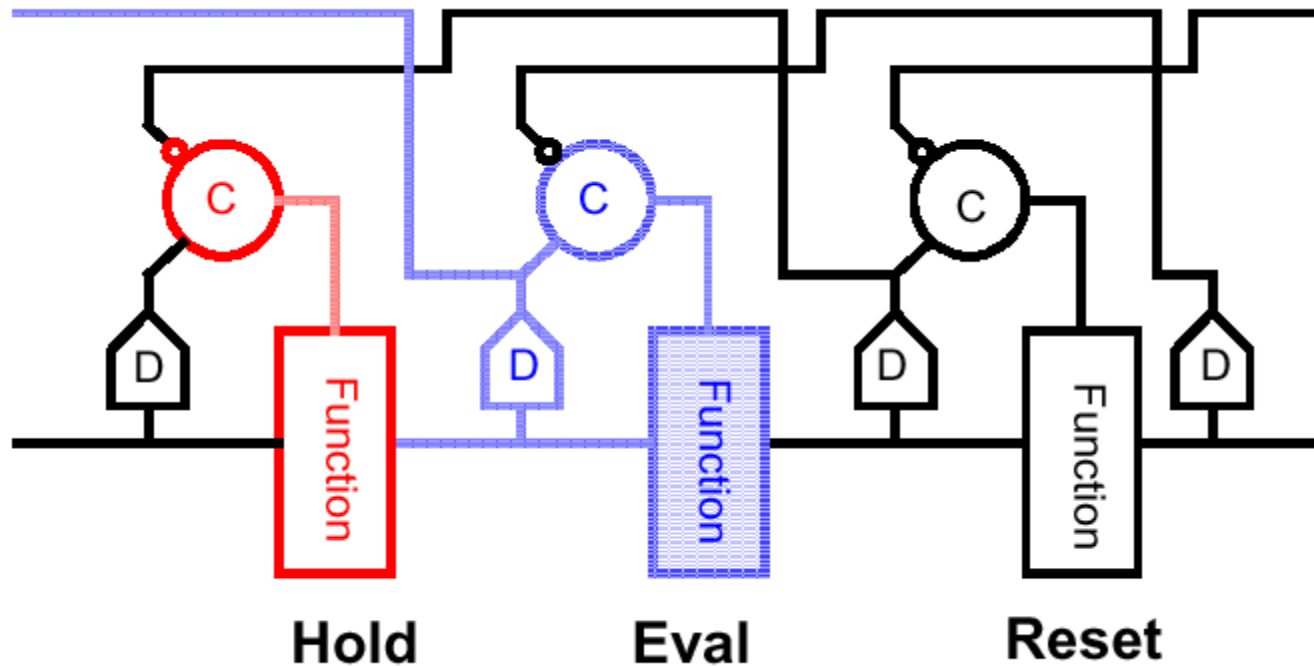


# Example

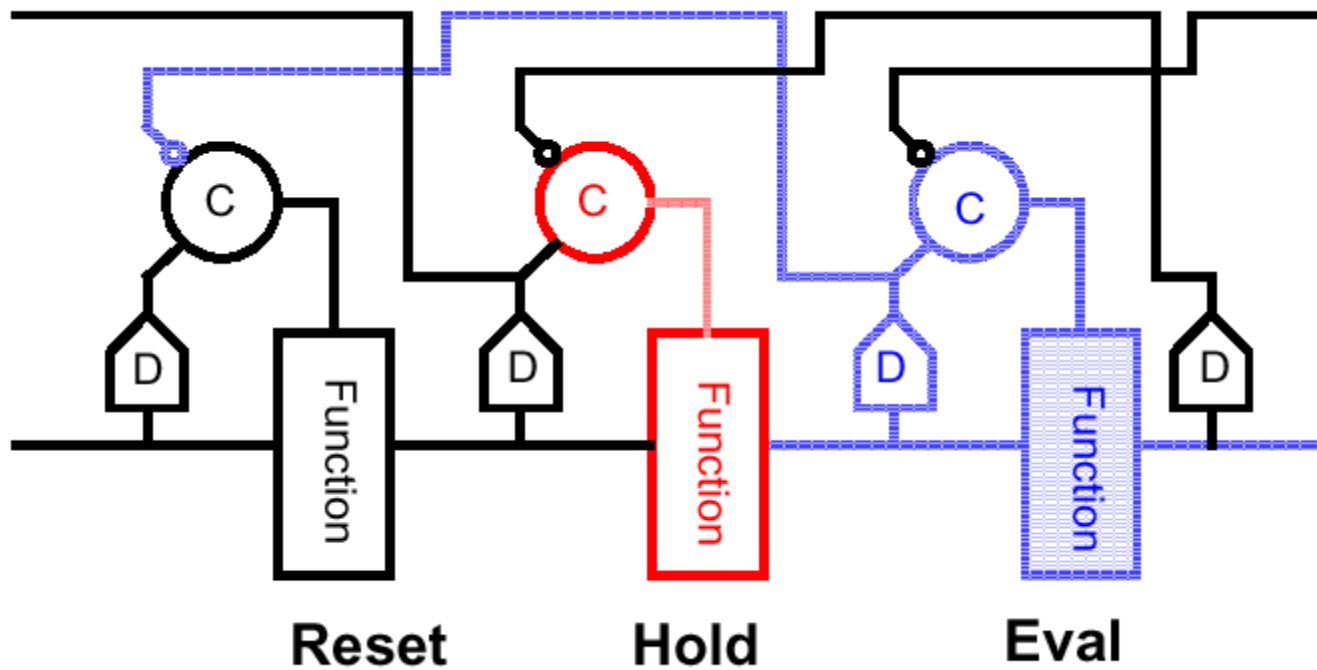

# Example

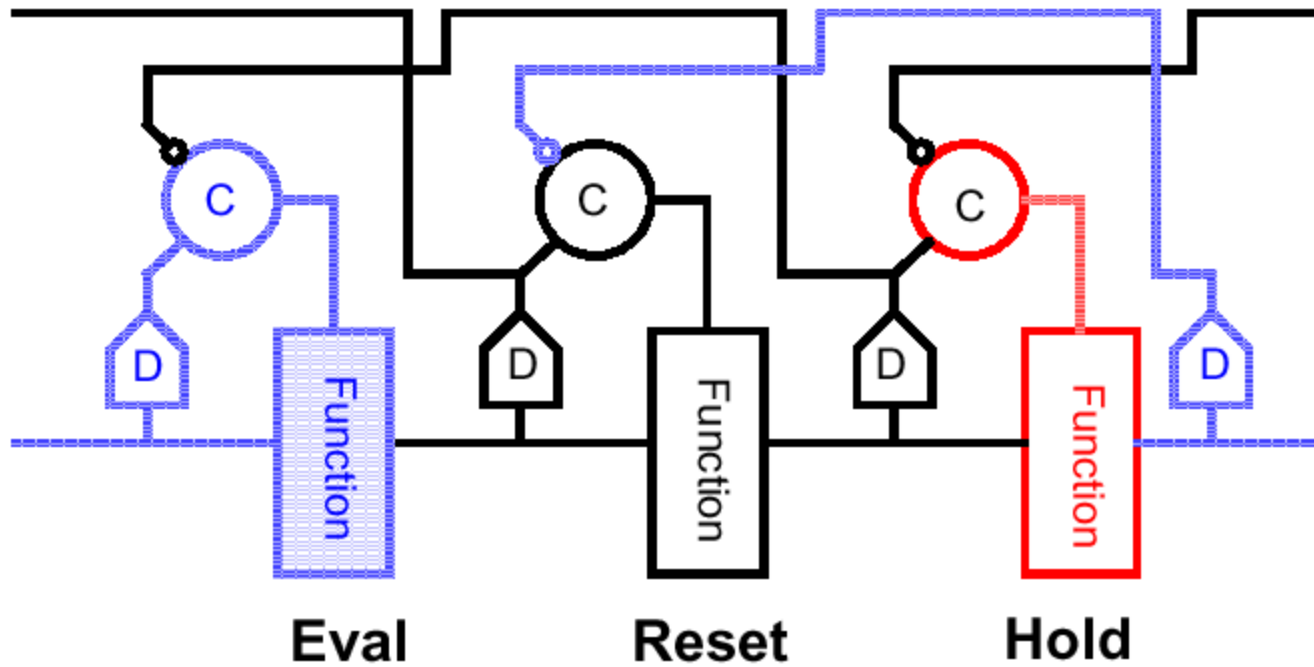

# 4-Phase Handshake Protocol

 


*Also known as RTZ*

Slower, but  
unambiguous





# 4-Phase Handshake Protocol

*Implementation using Muller-C elements*

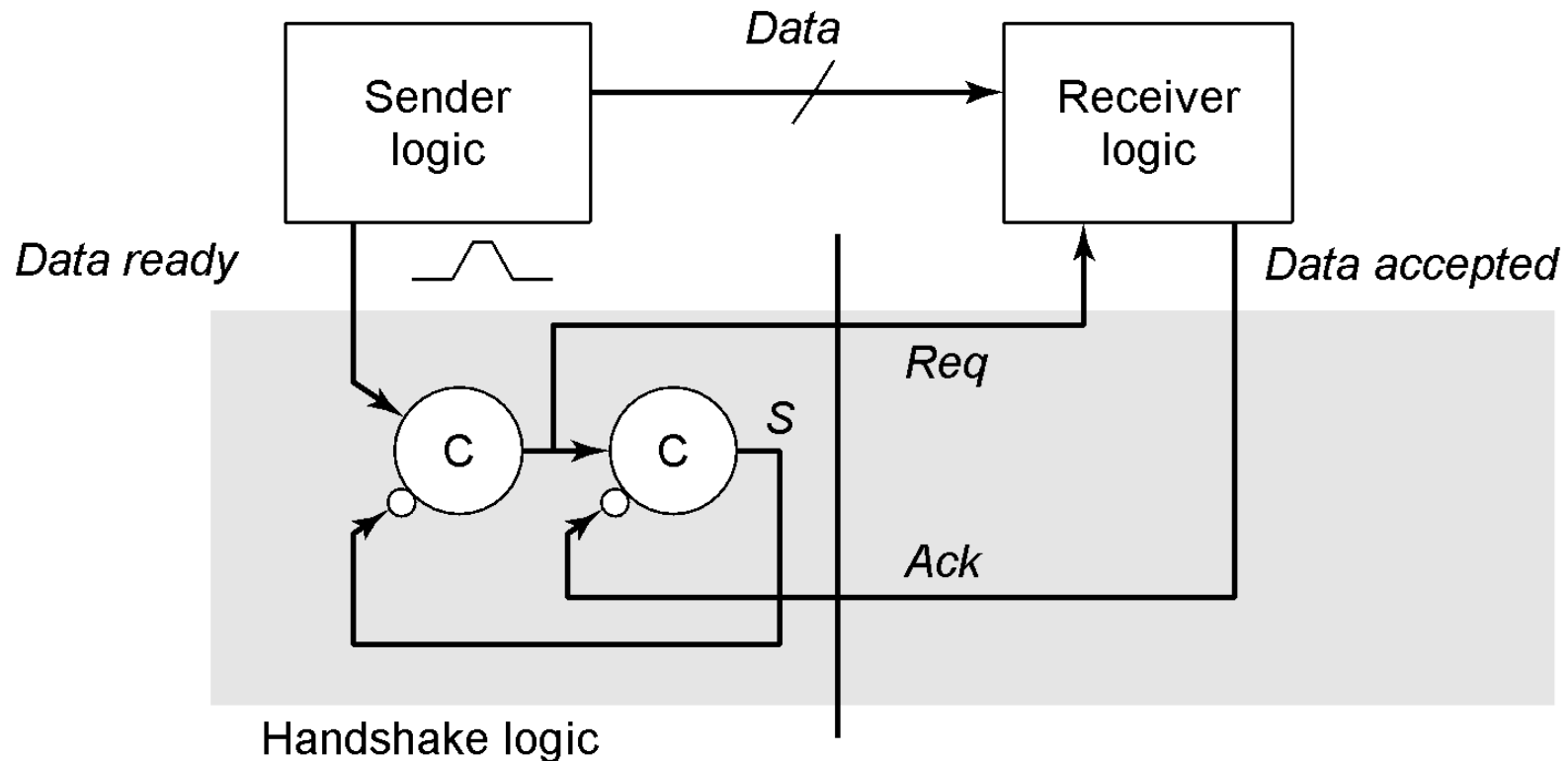


# Self-Resetting Logic

 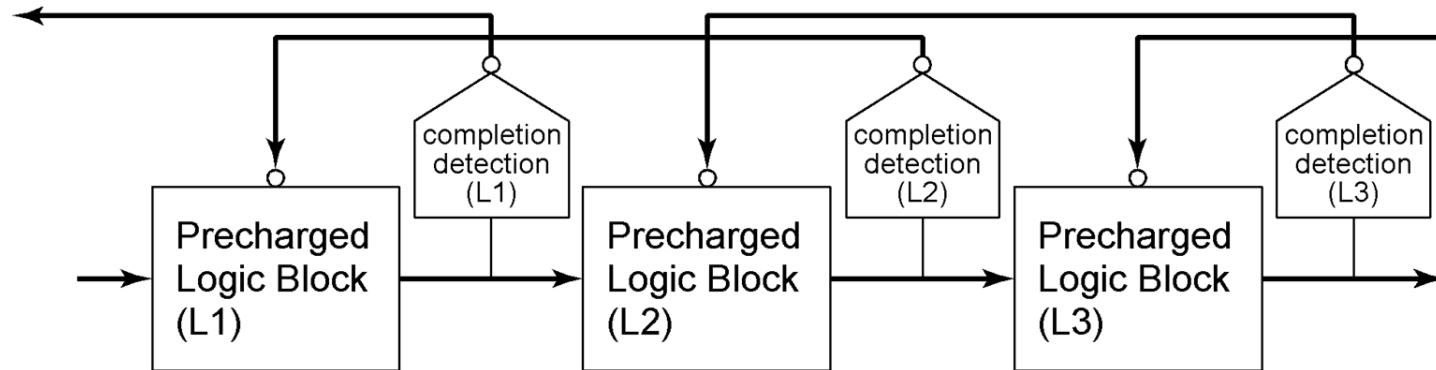


*Post-charge  
logic*

# Clock-Delayed Domino

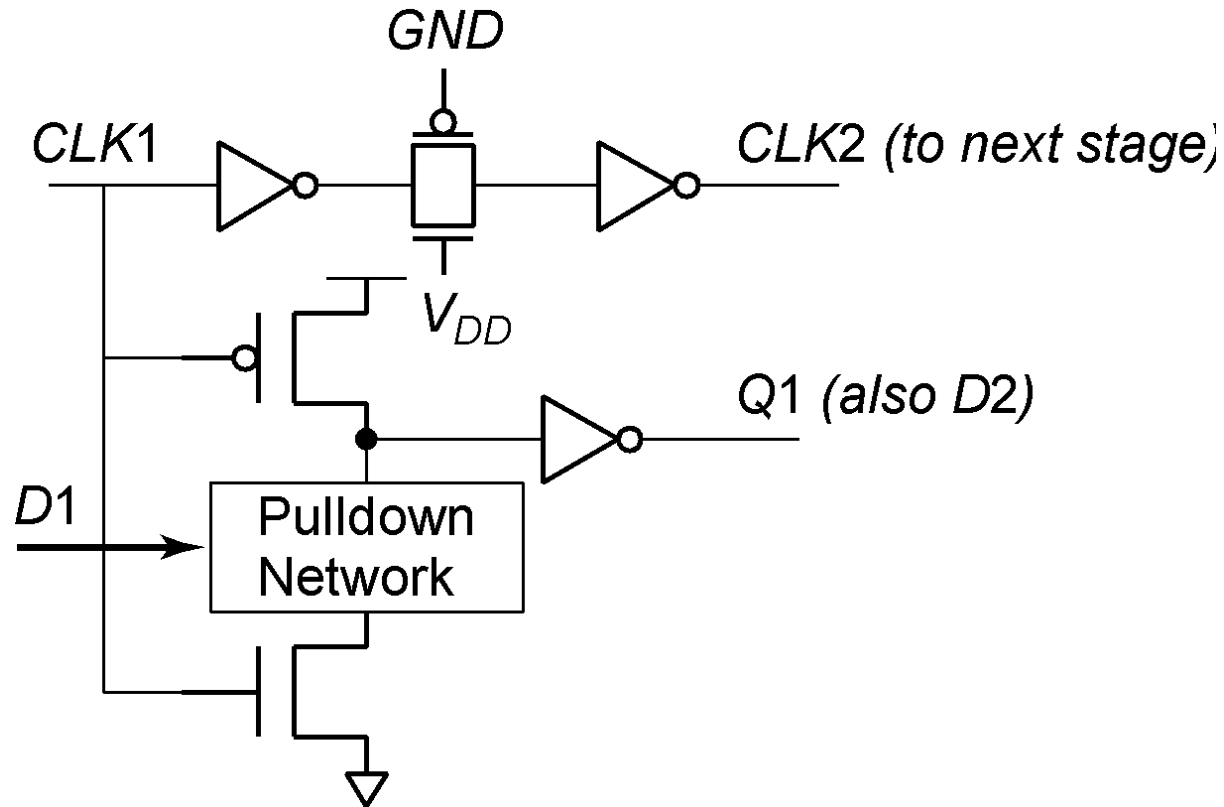


# Asynchronous-Synchronous Interface

 

# *Synchronizers and Arbiters*


- ❑ **Arbiter**: Circuit to decide which of 2 events occurred first
- ❑ **Synchronizer**: Arbiter with clock  $\varphi$  as one of the inputs
- ❑ **Problem**: Circuit HAS to make a decision in limited time - which decision is not important
- ❑ **Caveat**: It is impossible to ensure correct operation
- ❑ But, we can decrease the error probability at the expense of delay

# A Simple Synchronizer

 

- Data sampled on rising edge of the clock
- Latch will eventually resolve the signal value, but ... this might take infinite time!


# Synchronizer: Output Trajectories

 

**Single-pole model for a flip-**

$$v(t) = V_{MS} + (v(0) - V_{MS})e^{t/\tau}$$

# Mean Time to Failure

 

$$N_{sync}(0) = \frac{P_{init}}{T_{\phi}} = \frac{\left( \frac{V_{IH} - V_{IL}}{V_{swing}} \right) t_r}{T_{signal}} \frac{1}{T_{\phi}}$$

$$N_{sync}(T) = \frac{P_{init} e^{-T/\tau}}{T_{\phi}} = \frac{(V_{IH} - V_{IL}) e^{-T/\tau}}{V_{swing}} \frac{t_r}{T_{signal} T_{\phi}}$$



# Example

$$T_f = 10 \text{ nsec} = T$$

$$T_{\text{signal}} = 50 \text{ nsec}$$

$$t_r = 1 \text{ nsec}$$

$$t = 310 \text{ psec}$$


$$V_{IH} - V_{IL} = 1 \text{ V} \quad (V_{DD} = 5 \text{ V})$$

$$N(T) = 3.9 \cdot 10^{-9} \text{ errors/sec}$$

$$\text{MTF}(T) = 2.6 \cdot 10^8 \text{ sec} = 8.3 \text{ years}$$

$$\text{MTF}(0) = 2.5 \mu\text{sec}$$


# *Influence of Noise*

 


Low amplitude noise does not influence synchronization behavior

# Typical Synchronizers


## 2 phase clocking circuit

 


## Using delay line

 


# Cascaded Synchronizers Reduce MTF

 


# Arbiters

 

(a) Schematic symbol

 


(b) Implementation

 


(c) Timing diagram


# PLL-Based Synchronization

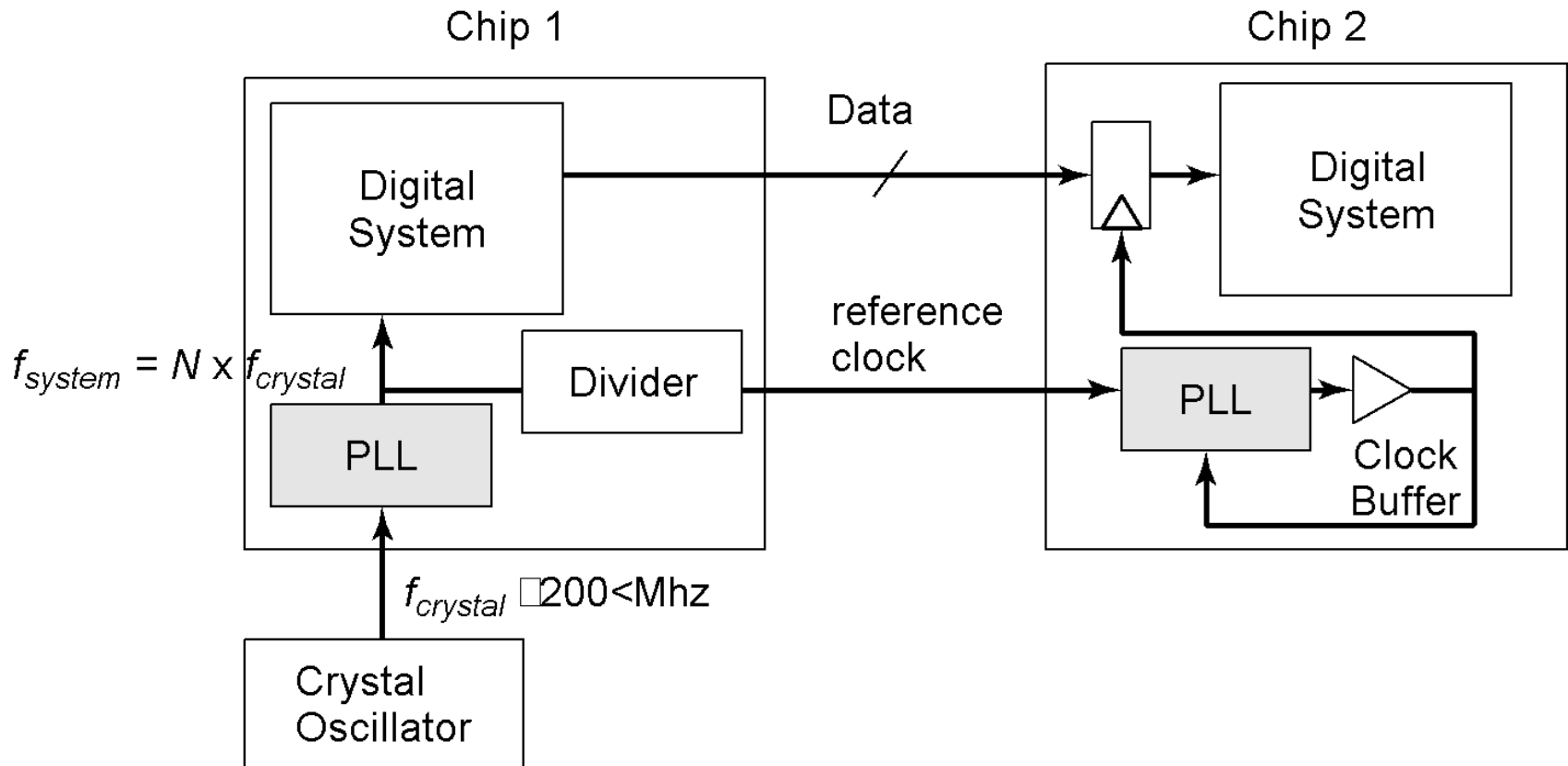

# PLL Block Diagram

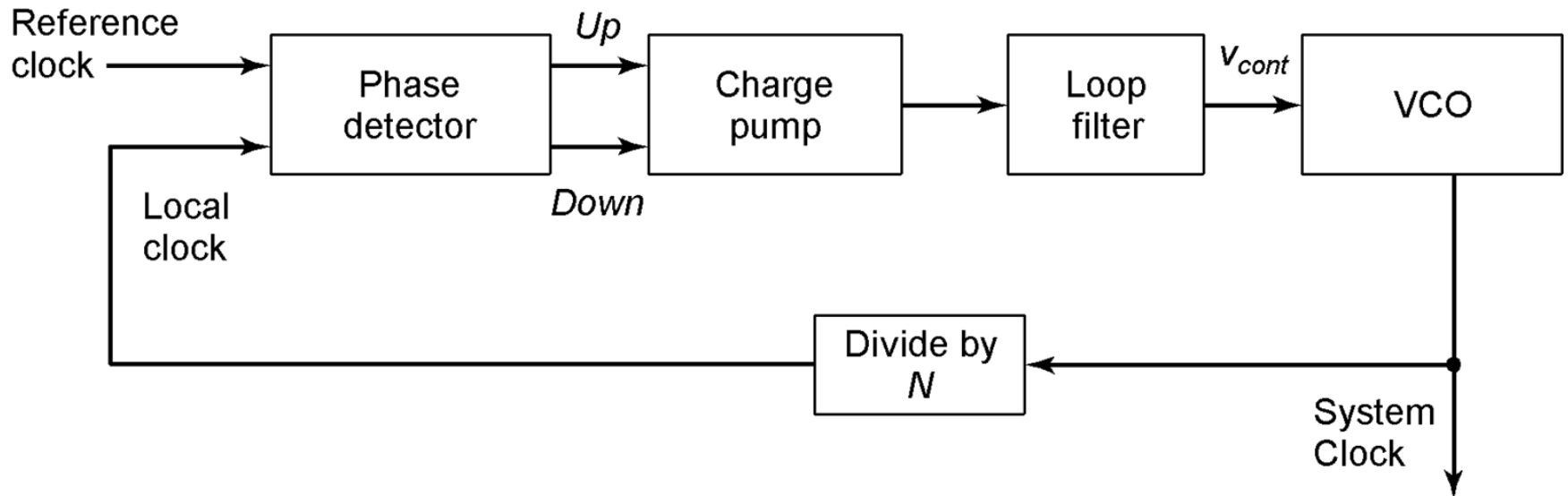


# Phase Detector

 


(a)

*Output before filtering*

 

(b)

 


(c)


*Transfer characteristic*





# Phase-Frequency Detector

 

(a) schematic

 


(b) state transition diagram

  


(c) Timing waveforms


# *PFD Response to Frequency*

 


# *PFD Phase Transfer Characteristic*

 

# Charge Pump

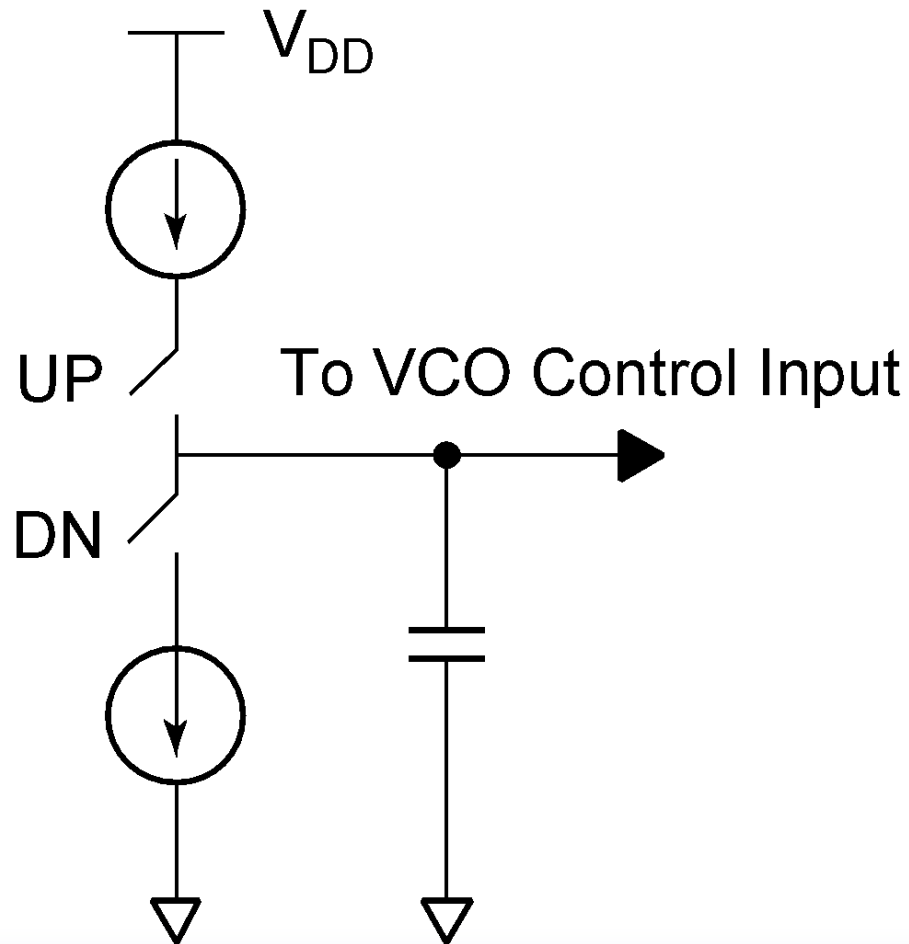


# PLL Simulation

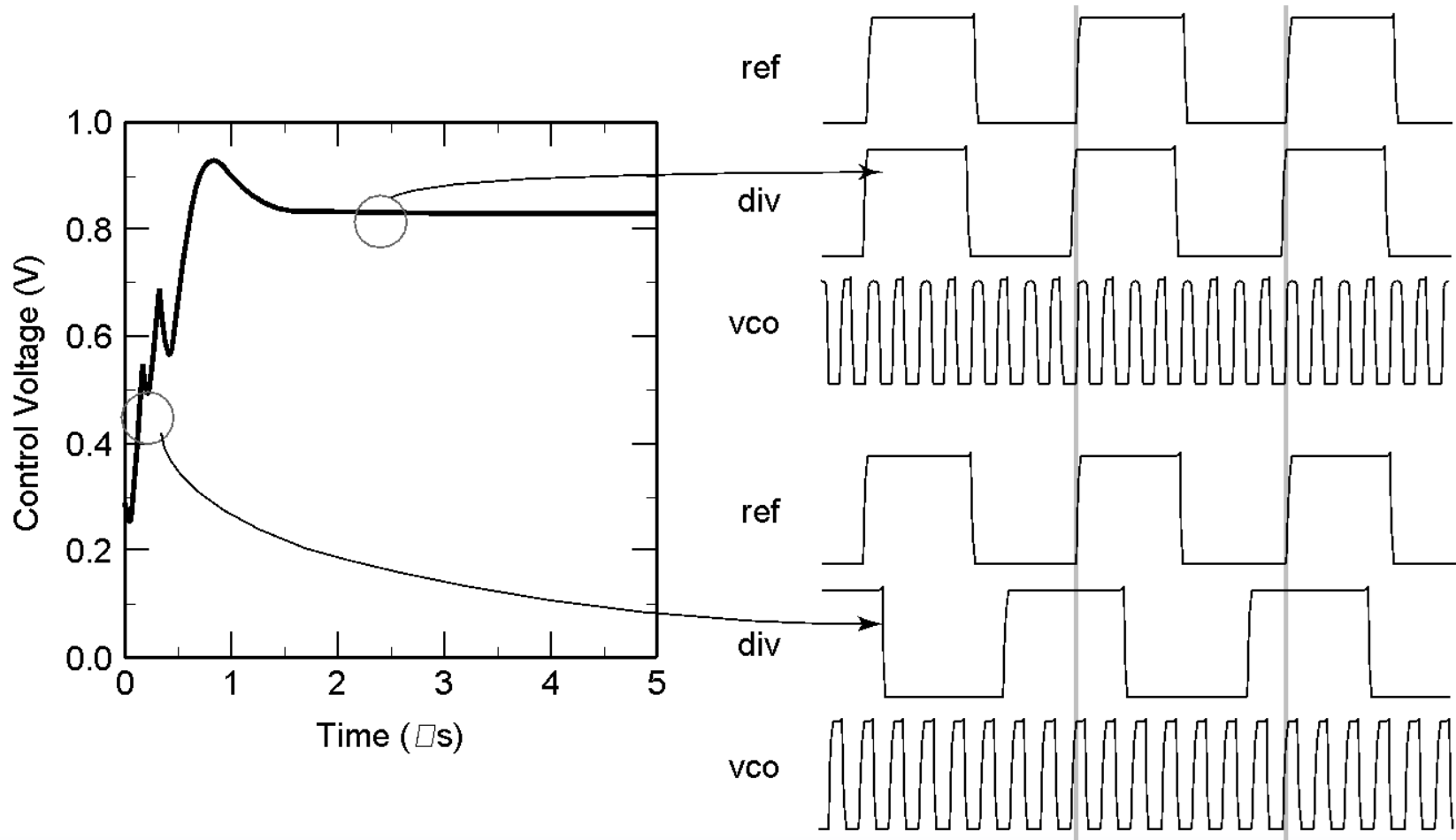


# Clock Generation using DLLs


Delay-Locked Loop (Delay Line Based)

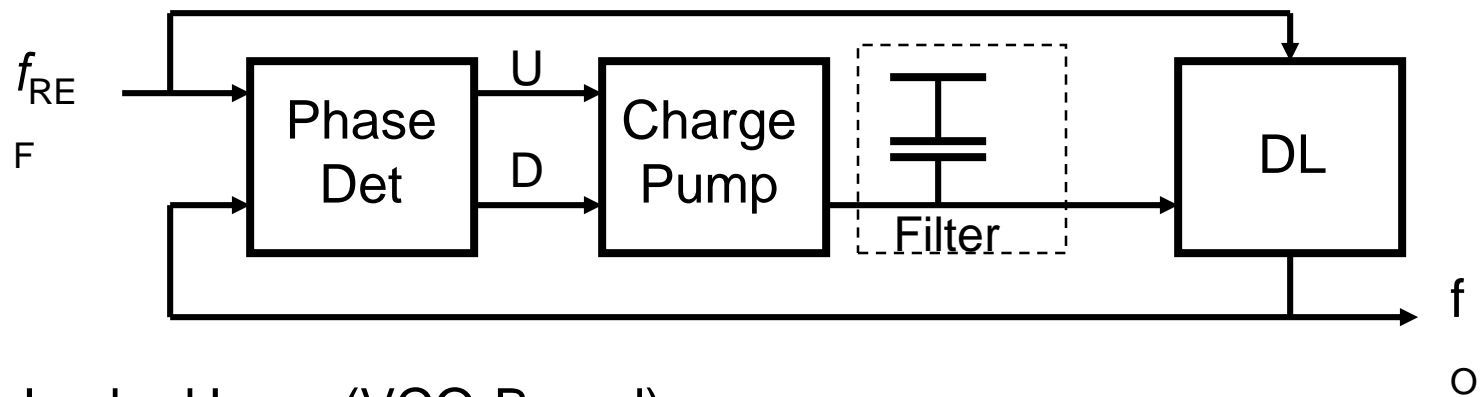


Phase-Locked Loop (VCO-Based)

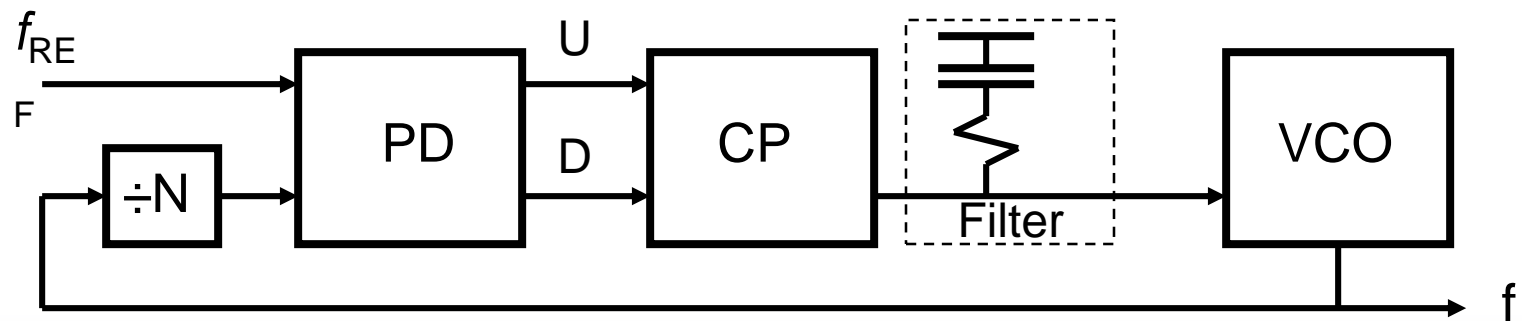


# Delay Locked Loop

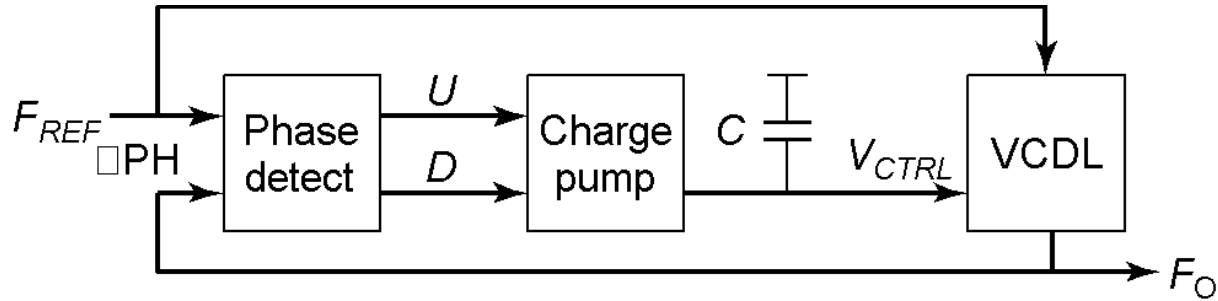

(a)

 

(b)

 

(c)

# *DLL-Based Clock Distribution*

